
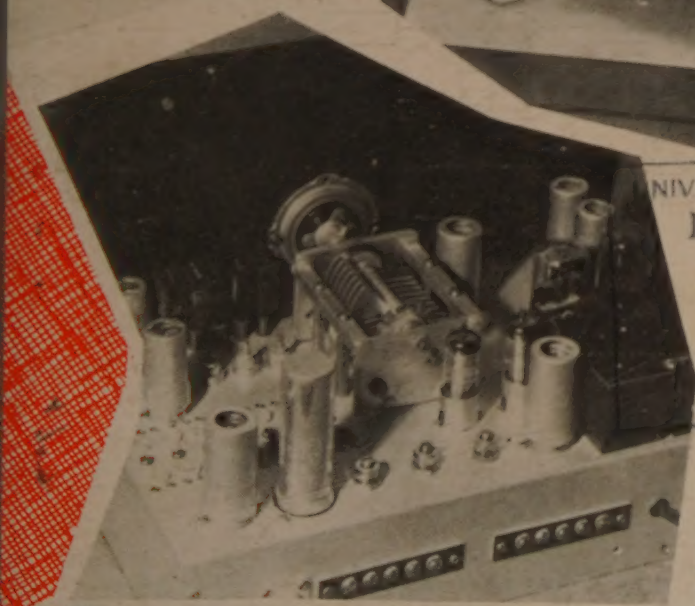


# CQ

October 1958

50c

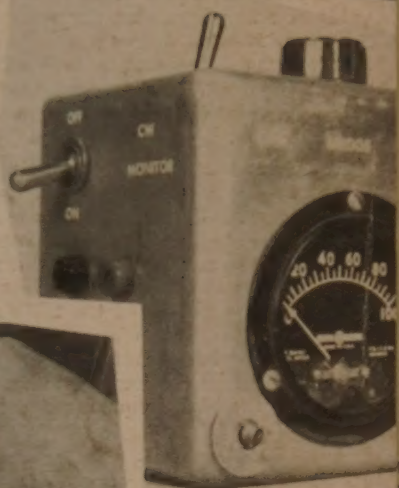

UNIVERSITY OF ILLINOIS  
LIBRARY

SEP 22 1958

CHICAGO



The Radio Amateur's Journal



# Double Conversion Double Talk

The single conversion superheterodyne is probably the most used piece of electronic equipment in the world today as the basis of almost every broadcast receiver. On the broadcast band, it does an excellent job of receiving where stations are separated by huge voids of empty spectrum (by amateur standards) so selectivity is not a serious problem. The frequency is low enough that low drift or good stability is not much of a requirement. This low frequency also allows adequate image and spurious rejection with very simple tuned circuits.

But try to use a single conversion receiver on the higher frequency ham bands and its deficiencies are greatly magnified. You first notice that you have your choice of two ten meter bands — one (the image) is a little weaker than the other, but still strong enough to create a problem when the band is crowded. You also notice that a slight jar of the table causes signals to disappear like magic. Warm-up drift becomes quite objectionable when the set is used on higher frequency bands, caused by the local oscillator which must operate near the high frequency signal in this type of circuit.

What can be done to cure these inherent faults of the single super? Assuming the same number of front end circuits, the only way to secure better image rejection is to use a higher IF frequency. But since a high IF frequency and good selectivity are not compatible, it is necessary to again convert this high IF to a lower frequency for selectivity purposes. This is



double conversion. Frequently this 2nd conversion is done with a crystal oscillator, but the main source of drift, the tuneable oscillator, is still required to operate at a high frequency. (See Block Diagram #1.)

We have now cured one of the faults, poor image rejection. If carried no further — which often happens — the double conversion superheterodyne still does and its signals still warble.

At Collins, we believe there is only one right way to build a double conversion super. That is to first convert the high frequency signal to a lower frequency signal by means of a stable crystal oscillator, providing good image rejection without introducing drift. Then tune this low frequency signal with a very stable linear oscillator, and since this oscillator is operating at a much lower frequency than the original signal, drift and mechanical instability become almost negligible. A Mechanical Filter is then used for securing the best possible selectivity. This is not the easiest nor the least expensive way to build a receiver, but we have found it the only effective method of producing maximum performance. So look at the block diagram before you buy. Is it done the easy way or the right way?

*Engene C. Senti*

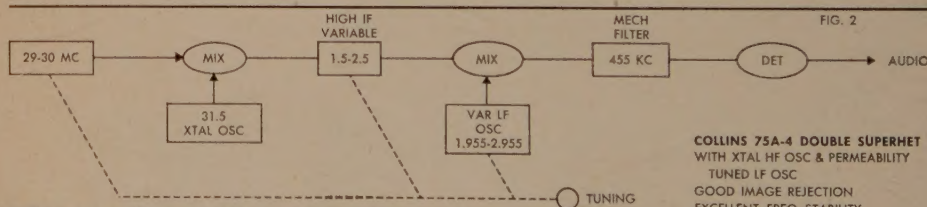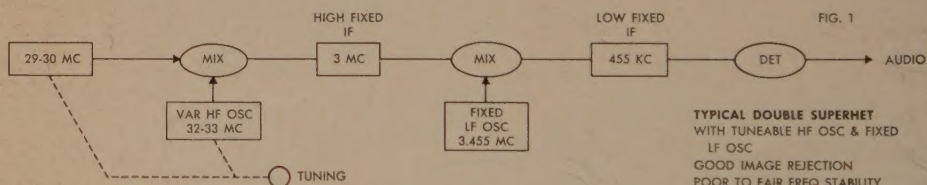
WØROW  
Design Engineer  
Amateur Section



For further information, check number 1 on page 126.

*Collins*

CREATIVE LEADER IN COMMUNICATION

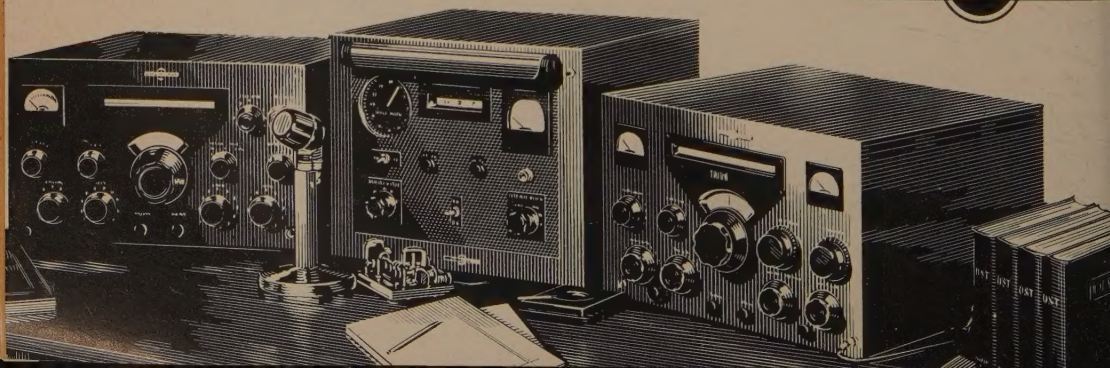



# Q—The Radio Amateur's Journal

October, 1958

vol. 14 no. 10

0 West 43rd Street, New York 36, N. Y.

Next Month: Parametric Amplifier construction details! (1 db noise figure on 2M)  
First one in the world on the air!

All Band Conversion Exciter	E. D. Crawfis, W7ATV	28
Mobiling	H. T. Orr, W0WET	31
DX-Pedition To Austin Pass	Ken Bale, W7VCB	32
9,641 FCC Citations	Maurice J. Hinden, W6EUV	35
Build Equipment On A Kitchen Table	A. D. Mayo, W5DF	36
Sixing the AF-67	James Frederick, Jr., K4ELB	38
A Quick Attachable Noise Limiter	E. H. Sommerfield, W2QUB	39
A Tunable Audio Filter	Thomas Beling, W9AEI	40
The "Macy's Special" Patch: \$2.98	Will Connelly, W6QID	42
All (Almost) Band Mobile	L. L. Chilton, W5THI	45
Stop Those Harmonics	E. H. Marriner, W6BLZ	46
The Vox-Break	R. F. Biloon, K2ECY	47
The Monomatic	A. L. Williamson, W8JVD	48
The 6AU8 Driver	Albert Newland, W2IHW	49
Water Cooled Rigs	Paul Barton, W6JAT	50
The Power Saving Voltage Dropper	Howard Felperin, K2KVG	52
Mercury Rectifier Tests	Paul M. Barton, W6JAT	54
Simple Vox For Sane Mobile Operation	Stan Bell, K6ESZ	56
All In A Name	Al Edwards, W2BOH	57
BC and Sputnik, Too!	Karl Thurber, K2KIZ	94
DB's	Cloice Proctor, W8PMD	95

## Departments

de W2NSD	9	RTTY	62	Contest Calendar	83
Scratchi	12	SB	64	Mars Broadcasts	83
Letters	14	Propagation	67	YL	84
QSL Contest	20	DX	71	Surplus Conversions	86
Club Bulletins	22	Overseas Echoes	79	Novice	89
Semiconductors	60	VHF	80	Ham Clinic	92
				Hamfest	109

## Branch Advertising Offices:

Ted E. Schell, 2700 West 3rd Street, Los Angeles 57, Calif. DUmkirk 2-4889.

Charles W. Hoefer, 1654 Emerson Street, Palo Alto, Calif. DAvenport 4-2661.

*publisher* S. R. Cowan  
*production manager* Bill Gardner, Jr.  
*circulation manager* Harold Weisner  
*editorial production* David Fish  
*advertising representative* Jack Schneider  
*advertising representative* Dick Cowan  
*classified advertising* Kate Gerace

(title registered U.S. Post Office) is published monthly by Cowan Publishing Corporation. Executive and editorial offices at 300 West 43rd Street, New York 36, N. Y. Telephone JUdson 2-4460. Second Class Mail privileges authorized at New York, N. Y.

SCRIPTION RATES: U.S.A. and Possessions, APO, FPO, Canada and Mexico: one year \$4.00; two years \$7.00; three years \$10.00. American and foreign: one year \$6.00; two years \$11.00; three years \$16.00.

IGN SUBSCRIPTIONS: Great Britain: RSGB, New Ruskin House, Little Russell St; London WC 1, England. Australia: Technical Co., 297 Swanston St., Melbourne C 1, Victoria, Australia.

ed in U.S.A. Entire contents copyright 1958 by Cowan Publishing Corporation. CQ does not assume responsibility for unsolicited manuscripts.

master: Send Form 3579 to CQ, 300 West 43rd Street, New York, N. Y.





CLELL K8DKY



DAR K8ADS



DICK K9EMJ/8



DOUG K8GNA



AL W8HTX




REX K8GND



FRED K8GMY



ERNIE W8VFN

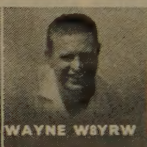

WAYNE W8YRW



FRANK W8WUN



AL K8BLI

All of these licensed radio amateurs make important contributions to the Heath line of fine ham kits. In a sense, they are your personal representatives within the company, because their design ideas and performance preferences reflect not only their own "on-the-air" experiences, but those of the amateur fraternity with which they are in constant contact. With this kind of representation in Benton Harbor, you can continue to rely on high-performance Heathkit amateur radio equipment designed by hams, for hams!

# HEATH *hams work to bring you*



CHUCK K9CJI



ROGER MACE (W8MWZ)  
SENIOR HAM ENGINEER  
HEATH COMPANY

## HEATHKIT 50-WATT CW TRANSMITTER KIT

MODEL DX-20

\$35<sup>95</sup>



If high efficiency at low cost in a CW transmitter interests you, you should be using a DX-20! It employs a single 6DQ6A tube in the final Amplifier stage for plate power input of 50 watts. The oscillator stage is a 6CL6, and the rectifier is a 5U4GB. Single knob band-switching is featured to cover 80, 40, 20, 15, 11 and 10 meters, and a pi network output circuit matches antenna impedances between 50 and 1000 ohms to reduce harmonic output. Designed for the novice as well as the advanced CW operator. The transmitter is actually fun to build, even for a beginner, with complete step-by-step instructions and pictorial diagrams. All the parts are top-quality and well rated for their application. "Potted" transformers, copper-plated chassis, and ceramic switch insulation are typical. Mechanical and electrical construction is such that TVI problems are minimized. If you desire a good clean CW signal, this is the transmitter for you. Shpg. Wt. 19 lbs.





## ...de W2NSD

never say die

## The National Convention

Everybody I talked to had a good time. I had a good time too. We sold a few subscriptions to the magazine and met a lot of old friends. I've been to so many conventions now that I'll bet I had met about half of the fellows at the convention at least twice before. It seems like there is a hard core of conventioners. They came by saying, "Glad to see you again, we met at San Francisco," etc.

The event was quite well organized and top notch. It was on tap for all of the lectures and forums. There were tours to just about every point of interest in the D.C. area, including the one that made my eyes pop out: open house aboard the submarine USS Drum. What memories it brought back. I'd spent almost two years aboard that boat during the war.

At the first opportunity I rushed down to the museum, which is now a school boat rather permanently tied up at the Navy Yard in Washington. There wasn't anyone around to guide the visitors from the convention through the boat so I set myself up as the guide and gave them the old spiel, "This is the After Engine Room, these are two Fairbanks Morse nine cylinder single acting opposed piston-1600 horsepower diesel engines, each driving a 1120 kilowatt generator," etc.

They had a rig set up in the Dinette operating on 20 SSB, just to top things off. Several other Naval ships have been active on the ham bands, but this is the first submarine.

## Eleven Meters . . . R.I.P.

For the benefit of that one chap who never uses the word . . . as of September 11, 1958 there was no more Eleven Meter amateur band. Just thought I'd mention it. You won't miss it since you've never used it. Too bad you didn't give it a try now and then. The FCC hinted out in their note that the big reason they were taking it away and giving it to the Citizens Radio Service was that their monitors didn't heard much of you on the band. Guess you left it for Charlie to do once too often, eh? The FCC stated, "It was particularly noted that most of the reasons presented for the opposition to the reallocation of the 11-meter band were based upon potential use of this band in the future instead of on actual need or existing use of the band. Monitoring reports

indicate that this band is not heavily used by the amateur service."

Let's see now, what have we left . . . ?

## On The Reciprocity Front

There has been a major breakthrough on the reciprocity problem. Late word is that the AOPA (Aircraft Owners and Pilots Association) members in Congress were able to get a bill passed through the House and Senate which makes it possible for alien pilots to operate their aircraft radios while flying in the United States in private aircraft. The prerequisite for this radio license from the FCC is a valid pilot's license from their own country.

If only we had a few hams in Congress so we could further amend the 1934 Communications Act to encompass aliens with valid amateur radio licenses we would go a long way towards creating friendship in foreign countries which would pay off come the frequency allocation conferences next year and in making it easier to get special licenses for DXpeditions.

## CW on Two

Several (seven) quite active VHF cw-men took me to task with a dash of vitriol for my one-sided presentation re the proposed setting aside of the lower 100 kc of both two and six meters for cw exclusively.

Since this was an ARRL proposal I theorized (correctly) that the pro side of the proposal would be well stated in QST. It thus seemed that a little attention should be placed on the negative aspects of the situation.

My question is this: granted that it is a good idea to encourage some cw operation on the VHF bands . . . why not agree on a segment for such a purpose which does not interfere with the bulk of the present activity on those bands? By establishing a DX segment up around 51 mc and 146 mc we would not have to have any FCC ruling to keep out the phone stations and we would also generate more activity in the relatively unused sections of the bands and give us a better chance of holding on to our frequencies when the next try is made to depose us. Remember, inactivity was given by the FCC as the reason for our losing Eleven Meters.

73, Wayne



**This is hallicrafters' SSB and V**

**MORE THAN  
\$14,000  
IN PRIZES!**

**5 GRAND  
PRIZES**

**plus more than**

**100 CERTIFICATES  
each worth  
\$100.00**

**ENTER  
BEFORE  
OCT. 31**

**1st  
PRIZE  
FPM-200**

**4th  
PRIZE  
SR-34**

**3rd  
PRIZE  
HT-32**

**2nd  
PRIZE  
HT-33A**

Hallicrafters' SSB-VHF Contest offers you another great opportunity to share in *more than \$14,000 worth of prizes!*

To enter this tremendous contest, simply visit one of the participating distributors and see a demon-

stration of Hallicrafters' latest SSB-VHF ment.

Enter today! You may win a gift certificate *\$100.00* as a local winner . . . plus a chance to win one of the five *grand prizes* illustrated above.

## **HERE'S HOW YOU ENTER—**

**1.** Go to one of the distributors listed here—any time during the month of October. See a demonstration of Hallicrafters' latest equipment.

**2.** Fill out the entry card which your distributor will supply you, including call letters and completion of, in 50 words or less, *either* of these two statements:

(a) *"I prefer Hallicrafters single sideband equipment because . . ."*

(b) *"I prefer Hallicrafters V.H.F. equipment because . . ."*

**3.** Turn in card to distributor—do not mail to Hallicrafters. Each distributor will judge his entries and select his local winner. More than 100 such local awards will be made to entrants submitting the best, most sincere and original statements in the opinion of the distributor or other individual(s) he may designate.

**4.** Each local winner will receive from this distributor a *Certificate worth \$100.00* for the purchase of any new Hallicrafters communication equipment. Decision of local winners' judges shall be final.


**5.** Local winners' names and entry statements will be forwarded to the Hallicrafters Company, where a panel of judges will select 1st, 2nd, 3rd, 4th and 5th place winners. Prizes to be



Best month!

You may win!

5th  
PRIZE  
SX-101

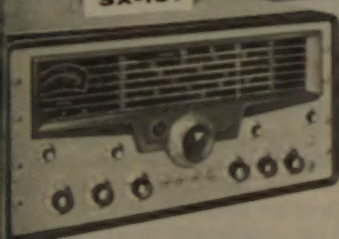

Peter A. Ricke,  
K8HHY  
Grand Winner,  
57 Hallicrafters  
SSB Contest

For more information, check  
page 6 on page 126.

Illustrated above.  
All decisions shall be

entries become the  
property of the Halli-  
crafters Company, and  
not be returned. Win-  
ning statements may be  
issued by the Halli-  
crafters Company  
winners identified.

Hallicrafters Co.  
Chicago 24, Illinois

## ENTER HERE!

Visit one of these distributors in October!

### ARIZONA

Phoenix: Southwest Wholesale Radio, Inc.

### CALIFORNIA

Berkeley: Electronics Suppliers  
Burbank: Valley Electronic Supply Co.  
Culver City: Bill Thompson's Radio Supply  
El Monte: Kimball & Stark, Inc.  
Inglewood: Universal Distributors, Inc.  
Long Beach: Larry Lynde Electronics  
Scott Radio Supply Co.  
Los Angeles: Henry Radio  
Radio Products Sales Co.  
Oakland: Elmer Electronics Inc.  
Palo Alto: Zack Radio Supply Co.  
Pasadena: Dow Radio Supply Co.  
Riverside: Mission Radio Ham Supplies  
San Diego:

Electronic Equipment Distributors  
Western Radio & Television Supply Co.  
San Francisco:  
Northern California Amateur Supply  
San Francisco Radio & Supply Co.  
Television Radio Supply Co.  
Zack Radio Supply Co.

San Jose: Frank Quement  
Santa Barbara: Channel Radio Supply Co.  
Van Nuys: Valley Electronic Supply Co.

### COLORADO

Denver: Radio Products Sales Co.  
Rogers Radio Co.

### CONNECTICUT

Hartford: Harty of Hartford, Inc.  
New Haven: Radio Shack

### DISTRICT OF COLUMBIA

Washington: Electronic Wholesalers, Inc.

### FLORIDA

Miami: Electronic Supply Co.  
Tampa: Kinkade Radio Supply

### ILLINOIS

Chicago: Allied Radio Corp.  
Green Mill Radio Supply Co.  
Newark Electric Co.  
Genoa: Crawford Electronics  
Moline: Lofgren Distributing Co.  
Peoria: Klaus Radio & Electric Co.  
Selectronic Supplies, Inc.

### INDIANA

Fort Wayne: Warren Radio  
Frankfort: M. H. Dossett Co.  
Indianapolis: Graham Electronics Sup. Inc.  
South Bend: Radio Distributing Co., Inc.

### IOWA

Council Bluffs:  
World Radio Laboratories, Inc.  
Des Moines: Bob & Jack's Store for Hams  
Fort Dodge: Ken-Els Radio Supply Co.

### KANSAS

Wichita: Molers Camera Clinic

### LOUISIANA

New Orleans: Radio Parts, Inc.

### MARYLAND

Baltimore: Amateur Radio Center  
Silver Springs:  
Uncle George's Radio Ham Shack

### MASSACHUSETTS

Boston: DeMambo Radio Supply Co.  
Radio Shack—Washington St.  
Radio Shack—Commonwealth Ave.  
Lawrence:  
Young & Young of Lawrence, Inc.  
Reading: Graham Co.  
Springfield:  
Young & Young of Springfield, Inc.  
Soundco Electronic Supply Co.

### MICHIGAN

Detroit: M. N. Duffy & Co.  
Reno Radio  
Grand Rapids: Radio Parts Co.

### MINNESOTA

Minneapolis: Electronic Center, Inc.

### MISSISSIPPI

Jackson: Swan Distributing Co., Inc.

### MISSOURI

Kansas City:  
Associated Electronic Supply Co.  
Radiolab

St. Louis: Walter Ashe Radio Co.

### NORTH CAROLINA

Asheville: Frack Radio & Supply

### NEW HAMPSHIRE

Concord: Evans Radio

### NEW JERSEY

Bloomfield: Variety Electronics Corp.  
Newark: Hudson Radio & T.V. Corp.  
Trenton: Almo Radio Co.

### NEW YORK

Albany:  
Fort Orange Radio Distributing Co., Inc.  
Bluepoint, L.I.: Standard Parts Corp.  
Hempstead: Standard Parts Corp.  
Jamaica: Harrison Radio Corp.  
Mineola: Arrow Electronics, Inc.  
New York: Harrison Radio Corp.  
Harvey Radio Co.  
Hudson Radio & Television Corp.  
Terminal Radio Corp.

White Plains: Melville Radio Corp.

### OHIO

Canton: Burroughs Radio, Inc.  
Cincinnati: Steinbergs, Inc.  
Cleveland:

Pioneer Electronic Supply Corp.  
Columbus: Universal Service  
Dayton: Custom Electronics, Inc.  
Marietta: Marietta Radio & Electric Co.  
Toledo: Selectronic Supplies, Inc.

### OKLAHOMA

Tulsa: Radio, Inc.

### OREGON

Portland: United Radio Supply, Inc.

### PENNSYLVANIA

Allentown: A. A. Peters, Inc.  
Elkins Park: A. G. Radio Parts Co.  
McKeesport: Barco Radio Co.  
Philadelphia: Almo Radio—Arch St.  
Almo Radio—Frankford Ave.  
Ham Buerger

Pittsburgh: Radio Parts Co., Inc.

### RHODE ISLAND

Providence: DeMambo Radio Supply  
W. H. Edwards Co.

### SOUTH DAKOTA

Watertown: Burghardt Radio Supply

### TEXAS

Amarillo: R & R Electronic Co.

Dallas: Central Electronics

Crabtree Wholesale Radio Co.

Fort Worth:

Electronic Equipment Co., Inc.  
Bill Sutton's Wholesale Electronics

Houston:

Busacker Electronic Equipment Co., Inc.  
R. C. & L. F. Hall, Inc.  
Lubbock: R & R Electronic Co.  
San Antonio: Modern Electronics Co.  
Texarkana: Lavender Radio Supply Co.  
Wichita Falls: R & R Electronic Co.

### VIRGINIA

Arlington: Key Electronics

### WASHINGTON

Seattle: Amateur Radio Supply Co.  
Pacific Electronics Sales Co.  
Seattle Radio Supply  
Tacoma: C & G Radio Supply




### WISCONSIN

Fond du Lac: Harris Radio Corp.  
Madison: Satterfield Electronics, Inc.  
Milwaukee: Amateur Electronic Supply
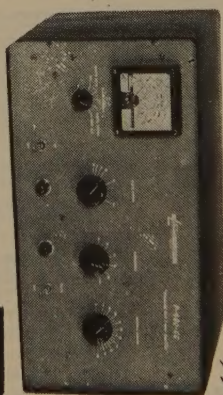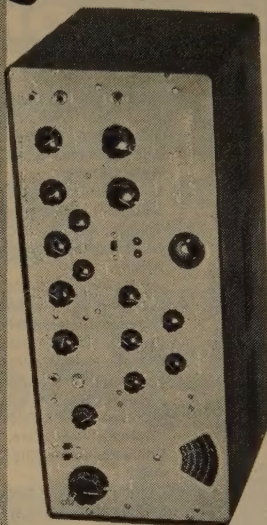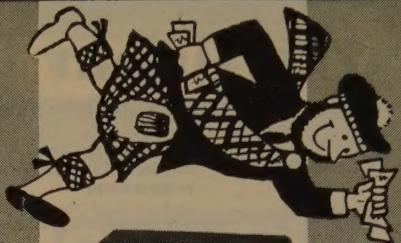
### HAWAII

Honolulu: Kaimuki Radio Co., Ltd.  
Precision Radio Limited





"Phasemaster II-B" +  
AMATEUR NET \$459.00

P-400 GC =  
AMATEUR NET \$269.50

**400**  
watts

**\$728.50**

COMPLETE WITH BUILT IN V.F.O.

See Your Dealer or Write Us....

**Lakeshore INDUSTRIES**  
MANTOWOC, WISCONSIN  
MANUFACTURERS OF PRECISION ELECTRONIC EQUIPMENT



Feenix, Ar

Deer Hon. Ed:

Sounding the Hon. Clarion Bell! Starting the Hon. Presses rolling! Warning all amchoor of the impending doom! Amchoor radio is not long for this world.

Yes indeedy, the rolling stone of doom is coming, Hon. Ed., and you knowing old sayings—A rolling stone are braking glass houses. And no time to losing. Are calling on you on account two heds are better than stitch in time.

Good old Seek-You will not failing the amchoors in there hour of peril. Your good old Hon. Rag will getting amchoors out there trouble.

What are the trubble? Hon. Ed., it are Extra Sensory Persepshun. You knowing what ESP are, I'm surely. Even having tellyvishun program on ESP. Peeples telling which card a which without seeing self-same card—peeples reeding other peoples mind.

All self-thinking amchoors must rising up and stamping out this threat to amchoor radio as we knowing it today. Can you imagine what happening if ESP catching hold? Arizona Kilowatts are doing no good. Not mattering how many beams feller are having. Could even taking toots out of reseever and making a difference.

Hon. Ed., here are what cue-ess-o of future being like. Amchoor first finding reel comfortable chair and sitting in it to getting relaxed. Leaning back, closing eyes, and making Hon. Mind a blank. (My XYL-to-be saying if this are important howcomes I not already expert on ESP).

Next, amchoor are tooning across band—mean looking—that is, thinking across the band. When coming across seek-you he wanting to answer, he answering by turning on men plate switch and talking to other amchoor.


Of course, if he having cue-are-em, may other amchoor not heering—that is, thinking him so maybe feller having to making men seek-you to seeing if he can getting someone to calling him.

If getting reel good at amchoor radio ESP they not saying he having nice fist. No indeed

[Continued on page 119]

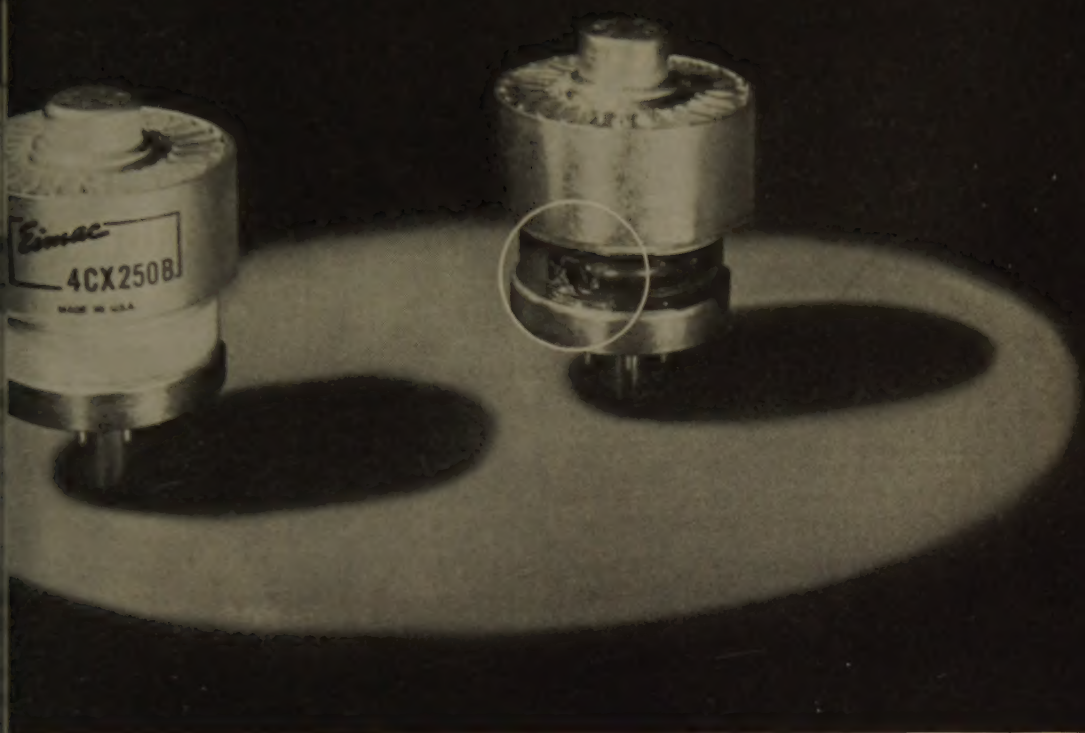For further information, check number 7 on page 126.





## Lower Dielectric Loss in an Eimac Ceramic Tube Extra

Fifth in a series describing the advantages of ceramics in electron tubes. Previously discussed: Impact, heat, vibration, compactness

Ceramic is considerably superior to glass in terms of dielectric loss at high frequencies. The ceramic envelope 4CX250B and the glass envelope 4X250B were operated in identical 500 megacycle RF amplifier circuits, under identical operating conditions. The glass envelope tube failed catastrophically within a few minutes due to RF heating and puncture of the glass envelope. Further testing of the 4CX250B at 500 Mc. with higher applied voltage showed no appreciable heating of the ceramic envelope material from dielectric loss effects.

Other tests compared glass envelope 2C39A tubes with 3CX100A5's, their ceramic envelope counterparts. These tubes were operated as oscillators at 100 Mc., under identical conditions. 3CX100A5

ceramic tubes consistently showed a 10% greater output power than the glass envelope type, due to the lower dielectric loss of the ceramic material.

These ceramic tubes are just two of more than 40 Eimac ceramic tube types whose compactness, and resistance to damage by impact, heat, and vibration make them ideal for use wherever exceptional reliability and high performance are demanded.

Write our Amateur Service Department for a copy of the booklet "Advantages of Ceramics in Electron Tubes"

**TEL-McCULLOUGH, INC.**  
SAN CARLOS, CALIFORNIA

*Eimac First with ceramic tubes that can take it*  
For further information, check number 8 on page 126.



### Products Designed and Manufactured by Eimac

Negative Grid Tubes

Reflex and Amplifier Klystrons

Ceramic Receiving Tubes

Traveling Wave Tubes

Vacuum Tube Accessories

Vacuum Switches

Vacuum Pumps

Includes an extensive line of ceramic electron tubes



# FREE



An FCC License can be Your  
Guarantee of Success in Electronics.

## Get your FCC Commercial License — or your money back

The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

### HERE'S PROOF:

Name and Address	License	Time
John H. Johnson, Boise City, Okla.....	1st	20 weeks
Prentice Harrison, Lewes, Del.....	1st	27 weeks
J. A. Niedeck, Bethlehem, Pa.....	2nd	8 weeks

WE CAN PROVIDE NAMES IN YOUR AREA ON REQUEST


### EMPLOYERS MAKE OFFERS LIKE THIS:

Letter from nationally-known Airlines: "Radio Operators and Radio Mechanics are needed for our company. Periodic wage increase with opportunity for advancement. Many company benefits."

### OUR TRAINEES GET JOBS LIKE THIS:

"Since enrolling with Cleveland Institute I have received my 1st class license, and am now Chief Engineer of Station WAIN. Thanks to the Institute for making this possible."

Lewis M. Owens, Columbia, Ky.

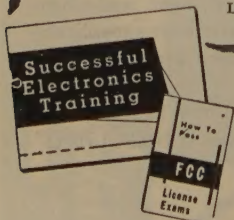

MAIL COUPON TODAY  
AND RECEIVE ALL  
2 BOOKLETS

## FREE

Accredited by National  
Home Study Council



Cleveland Institute of Radio Electronics  
Carl E. Smith, Consulting Engineer, President  
Desk CQ-45, 4900 Euclid Ave., Cleveland 3, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- |   |   |
|---|---|
| <input type="checkbox"/> Military           | <input type="checkbox"/> Broadcasting       |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home experimenting |
| <input type="checkbox"/> Manufacturing      | <input type="checkbox"/> Telephone Company  |
| <input type="checkbox"/> Amateur Radio      | <input type="checkbox"/> Others             |

In what kind of work are you now engaged?.....

In what branch of Electronics are you interested?.....

Name ..... Age.....

Address .....

City ..... Zone..... State.....

## Letters • • • to the editor

### CG Foul Up

Dear Wayne,

I am 18 years old and a 3rd class radioman in U.S. Coast Guard. I have been in the C.G. since July 1957 and I am currently on the C.G. Cutter Bram engaged in Arctic operations. You asked for info on Ham radio in the service so here is the situation I found it.

I went through boot camp at Alameda, Calif.—ham station. Next stop; radio school at Groton, Connecticut. They have a ham station there consisting of a 32V2,51J and a beat-up 20 meter beam. I was there for 5 months and spent the first 3 trying to get an officer-in-charge of radio school to get a club organized and get back on the air as the station, W1CGS, had been closed for several months and nobody seemed to have any interest in getting it back on the air. Finally I managed to make a weekly sked home for my 17 or 8 weeks there. From radio school I reported about the Bramble 3 weeks before departure from Mid Beach to the Arctic. A request had been sent in to operate ham radio on the trip. It was forwarded, proved all the way up to the Chief of Naval Operations who declined it. By the time we got his reply we were underway. I should explain that we had intended using the ship's transmitter for ham use and CNO said we could get some separate gear it would be approved. That was nice to know after we were a thousand miles from a radio store.

They have a ham station here at the Naval base in Argentina but it is inoperative.

Well, there it is. I have been in the service almost a year and ham radio has become nothing but a memory and a very fond one at that. I shudder to think of next 3 years. Will I lose my ham spirit?

I am fond of all phases of ham radio and especially enjoyed the 10 meter hidden transmitter hunts and chasing DX on ten meters during the winter of 56/57. I chalked up 112 countries during that time using DX-100, NC-125 and a 3 element beam. All I have now is an HQ-140X at home.

Louis J. Haake RM3  
USCGC Bramble WAGL-392  
c/o FPO New York, New York

### No Fairy Tale

W2NSD:

We are like the Old Woman in the Shoe . . . we read so many beam articles that we don't know what to do. Hi. PS: Like the July issue, my subscription is enclosed.

W8P

### Army Foul Up

Dear Wayne:

I'm replying to your inquiry in the June Editor concerning hams in the service.

I came into the Army (I'm sad to relate) last June. I had been in the Regular Reserves for two years as a radio operator. When I came in Active I was sent to Fort Knox, Kentucky, and went through a twelve week Radio operator's course. An interesting point is that even though I had been an operator in the Reserves I was still sent to school. The Army has a rule that they do not honor Reserve specialties and will send a guy to a school anyway. It was actually ridiculous, because I took all the tests the first week and sat around

[Continued on page 16]



# Quality...

## UNSURPASSED — ANYWHERE NEAR THE PRICE!



**HQ-170**

### HQ-170

For the amateur who wants the very finest in SSB receivers. Contains all the functions necessary for solid contact in today's crowded bands. 17-Tube superheterodyne. Dual and triple conversion. Separate vernier tuning. Adjustable 60 db notch filter. 6, 10, 15, 20, 40, 80 and 160 meter amateur bands.

**\$359<sup>00</sup>\***

### HQ-160

You could pay twice as much, and get no more than the general-coverage HQ-160 quality. Dual conversion. 540 KCS to 31 MCS. SSB. Q-Multiplier. Electrical bandspread. Separate stabilized BFO. Crystal calibrator. Adjustable 60 db notch filter. 13-Tube superheterodyne. Crystal-controlled 2nd IF.

**\$379<sup>00</sup>**



**HQ-160**

Here's the pair that's making history in amateur radio. Never before has so much genuine quality and performance been offered at such low prices. Now the amateur can choose the one he wants and be sure that he's getting the very best buy in either a straight ham band or general coverage receiver.

\*Telechron clock-timer. \$10 extra.



Established 1919

# HAMMARLUND


**HAMMARLUND MANUFACTURING COMPANY, INC.**  
460 West 34th Street, New York 1, N. Y.

For further information, check number 9 on page 126.



# NEW

## SUPER-12 CONVERTER

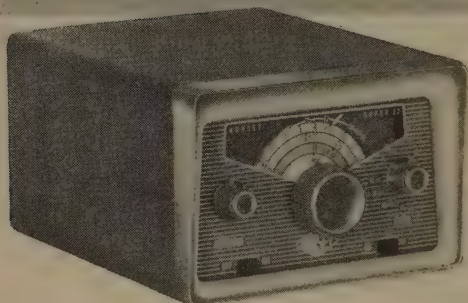

*Now...SUPER-12...a modernized  
version of Gonset's very well known  
SUPER-6 Converter.*

### features...

...direct 12 volt operation...the perfect SW converter  
for the new 12 volt "Hybrid" auto BC receivers.

### features...

...wide frequency coverage. 10-11, 15-20, 40 and 75 meter  
amateur bands. Also 19 and 49 meter international short  
wave bands for casual listening.

### features...

...high sensitivity and stability. Has panel antenna trimmer,  
BC-SW switch, calibrated, easy-to-read tuning dial  
with planetary drive for vernier tuning.


### features...

...compactness, easy mounting. Modern, attractive, blends  
with instrument panel of modern cars.

### features...

...simple, rapid installation. No alterations or internal  
connections to BC set. Converter merely plugs into antenna  
input of car radio. Operating power is obtained from battery  
connection post behind dash.

Model 3261 ————— 57.50

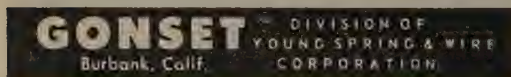

For further information, check number 10 on page 126.

## LETTERS [from page 14]

for eleven weeks with nothing to do.

Upon being graduated from the school I was  
signed to the Fort Knox Mars station as an operator.

A tip to any ham coming into service—it pays to  
it be known to the powers that you are a ham and  
terested in being assigned to a MARS station. This  
the best deal and practically the only one where you  
will do your intended job. I have corresponded with  
some of the guys from my class, and only one of five  
or six I know about is an operator. The rest are truck  
drivers, border guards (in Germany), clerk typists, etc.  
It seems that very few of the guys who go through  
radio school actually end up as an operator.

The job at the MARS station was really a good deal.  
I worked every other day and had every other week  
off. All I did was ham and meet a few MARS net.  
The rest of the time I spent any way I wanted, building,  
experimenting, etc.

When I first came in the Army I applied for Guided  
Missile School. Nothing ever happened until I had  
been assigned to the Station for a couple of months.  
Then, just like the Army, I suddenly received word  
that I had been accepted and was to report to Fort  
Monmouth, N. J., immediately. I hated to leave such  
a good deal, but this way I am getting into my chosen  
field. I spend 12 weeks at Monmouth and am now in  
my 10th week of a 26 week course in testing, maintenance  
and repair of the Nike Ajax—Hercules Acquisition  
Radar and Computer, here at Redstone Arsenal, Ala.

Having taken Electrical Engineering in college and  
wanting to work with missiles when I get out of the  
Army, this is the best deal for me.

I did enjoy my stint as a MARS operator and remind  
any ham to let himself be known as a ham and wanting  
to operate MARS. They certainly don't ask him.

The Army is generally terrible, but can be made  
livable by getting something you want. But you have  
to work a little to get it.

Hope this will help you with the overall picture.  
Wayne, and will be glad to offer any other information.  
Sure wish I were a civilian again, because that job  
CQ sure sounds inviting. Thanks for the nice job you  
are doing at CQ. It certainly is a pleasure to read CQ  
every month.

Am 10 meter mobile in my 1958 Fiat 600. The small  
cars are Great! Would also go for a Fly-In Hamfest.  
Let's have one!

Donald L. Schliesser, W8KA

### Oops

Dear Mr. Editor,

We have just received the June issue of your well  
known CQ Magazine and sorry we read on page 56  
very great mistake about our PACC-Certificate.

This PACC Certificate is namely our own Certificate  
and of course it is only available by our Society.

Cards should be submitted direct to the Traffic Manager  
of our Society, the V.E.R.O.N. (Netherlands Section  
of the I.A.R.U.), Postbox 6011, The Hague, the  
Netherlands.

We have asked our Traffic Manager, Mr. Louis van  
Nadort, PAØLOU, to send you as soon as possible some  
interesting information about our Certificates.

We suppose you will be kind enough to correct your  
message in the next issue, because it is of international  
importance to have the disposal of right information  
especially for the dx-hams.

We thank you in anticipation and remain with good  
luck,

sincerely yours,

H. M. Udtöolen, PAØN  
President

### Circulating Library

Dear Sirs:

My subscription to your magazine was a gift from  
the XYL and I must say that I enjoy each and every  
[Continued on page 18]



# ROOF OF THE PUDDING...



## ON-THE-AIR REPORTS

"... miraculously reduced the effort required in sending."

"... increased my percentage of successful CQ's."

"In a traffic net, I now have far less requests for repeats."

"Though I'm a novice, the old timers compliment me on my sending—thanks to the EE-3A."

"Friends on the air say it's the best phone patch they've heard."

"My mother, who knows practically nothing about ham radio, didn't realize she was talking thru a patch."

"From start to finish, I never touch a knob."

"The Antarctic gang really approves of and uses my new TFP-1."

For further information  
see your dealer,  
or write  
ELDICO direct.




**ELDICO**  
ELECTRONICS

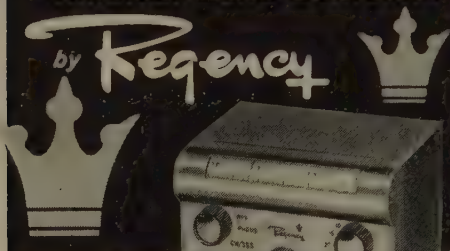29-01 BORDEN AVENUE, LONG ISLAND CITY, NEW YORK


A Division of Radio Engineering Laboratories, Inc.



Receive "Ham" signals  
anywhere, on any set with  
Model ATC-1 Transistorized  
Amateur Band Converter



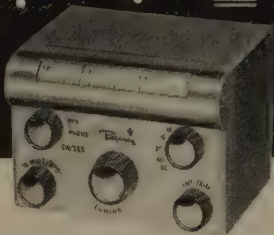WORLD'S  
ONLY  
SPECIALIST  
IN TRANSISTORIZED EQUIPMENT



THE ONLY CONVERTER  
FOR AMATEUR RECEPTION  
ON NEW 12 VOLT  
AUTO RADIOS...

because Model ATC-1 is self-powered (3 pen-light batteries, shelf life expectancy) and does not require a power supply. Its own power supply guarantees frequency stability—voltage fluctuations in car's electrical system will not affect it.

Simple to connect—one connection to antenna, other to receiver antenna input; only  $4\frac{3}{4}$ " x  $3\frac{1}{4}$ " x  $4\frac{1}{16}$ "—30 ounces—small and light enough to be carried easily, mounted in any convenient spot in car; adaptable to any receiver—receives AM, CW and SSB on the 80, 40, 20, 15 and 10 meter amateur bands; the answer to mobile SSB listening—built in BFO plus a high degree of stability make the tuning of SSB, DSB, or CW signals a pleasure; provided with outstanding selectivity on AM phone by the modified "Q" multiplier circuit.

Model ATC-1, \$79.50

See your Electric Parts Distributor for full information on Transistor complement, Diode clamp protection, Controls, Sensitivity, etc., or write

Burton Browne Advertising

Regency

Division I.D.E.A., Inc.

7900 Pendleton Pike, Indianapolis 26, Ind.

## LETTERS [from page 16]

issue. It does the rounds at my office where we have four other active hams. I particularly enjoy your V7 news and articles, your tongue-in-the-cheek presentation and the fact that your staff is largely composed of sportscar driving night-people. Obviously fine chaps.

Perhaps you would allow me to forward my thanks to the Manitoba Phone Net through your letters to the editor column. During a two month stay in the bush I operated portable VE4. My transmitter was a battery operated rig working up to a mighty five watts times. The members of the net stood by for me every night and made every effort to copy my signal. During my operation there I passed personal messages, a forest fire report, a report on a lost aircraft and a request for food when our camp communications broke down. My special thanks to VE4PA, 4FF and 4RR.

Jas. B. Bremner, VE3AL

Quebec

This lending of CQ to fellow employees must stop immediately or we will have to terminate your subscription.—ed.

### Oh, for the life of a bachelor

Dear Wayne:

My curiosity has gotten the better of me. Five or six years ago you were on twenty meters requesting anyone listening to send a card to a friend who was getting married. This card was to be signed by a make-believe girl friend of your pal to get him in dutch with his wife. No doubt he did receive several cards for his sister-in-law VE3BVT sent him one as did some other locally. How many cards did he receive? Are you his friend? What happened?

Bert, VE3AL

Well, Bert, that hoax worked out splendidly. You see here is what happened. This friend of mine, 75 years old and living in a small town in New Hampshire (a home town), was about to get married to a gal from a small Vermont town. I got on the air and got fellows from all over the world to send post cards to him both his address and her address, all signed by supposed girl friends and all disappointed that he was getting married and thus going out of circulation. The dozen so fellows that I talked to on twenty meters spread on all bands and several hundred cards came pouring to the two small post offices from Alaska, Germany, Scotland, South Africa, all over South America, Canada, etc. Plus just about every state. This natural caused quite a stir in the post offices, which aren't kept pretty good track of post cards.

My friend had no inkling as to how such a thing happened to him. He had no notion of my interest in ham radio and it was completely bewildering... impossible to explain. I finally told him about several months later and he turned a few of the cards that got by his wife over to me. I don't think she appreciated the humor of it, hi!

### Another First

Dear Wayne:

The first meeting of a group of amateurs to reactivate the NARC was held in the Town Hall, Broadway Heights, Ohio, on June 14, 1958. W8UDN, Edward "J" Kopp was elected Chairman, and past secretary W8R. Harry Steffan was elected Advisor.

Quite a number of local Hams were in attendance and the meeting was considered a success by those who organized it and arranged for use of the Town Hall.

Let's all get behind the only organization responsible for the use of the 40 meter 'fone band and the meter band as of this date.

James R. Jansic, W8

Publicity NA

RFD #6 County Rd.

Brunswick, O


For further information, check number 12 on page 126.



# ANNOUNCING THE NEW
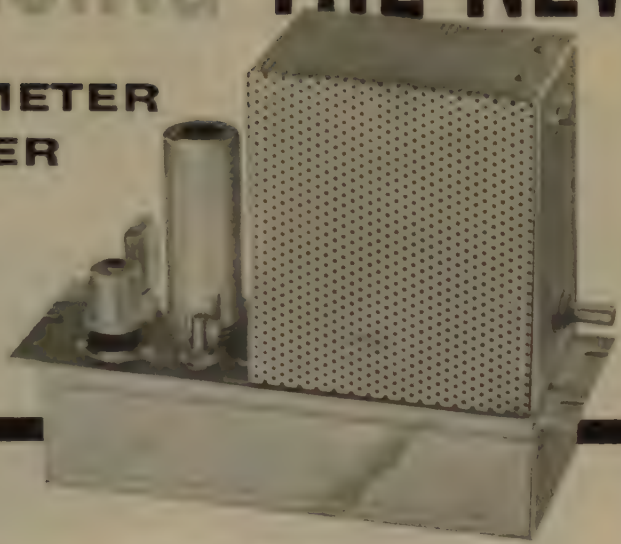
## STP-50, 6 METER TRANSMITTER

THIS TRANSMITTER IS  
THE FIRST OF SEVERAL  
STRIP TYPE UNITS TO BE  
MANUFACTURED BY  
INTERNATIONAL



### SPECIFICATIONS

Power Input: Maximum 30 watts  
 Tube Line-Up: Oscillator-Buffer 12BY7  
 Final: 2E26  
 Heater Power: 6 Volts  
 Plate Power: 300 to 500 Volts  
 Crystal: 12MC Fundamental (8MC Fundamental  
                     Crystal may be used)  
 Size: 3" x 6" x 6"

### PRICES

Kit, less tubes and crystal .....\$21.50  
 Kit, with tubes less crystal ..... 26.50  
 Wired, with tubes but less crystal ..... 32.50  
 Crystal, FA-5 12MC ..... 4.00

The STP-50 transmitter doubles in the first stage and doubles in the final. By doubling in the final we will eliminate neutralization problems and we gain the ease of alignment.

**AVAILABLE OCTOBER 1, 1958**

### HOW TO ORDER

Please supply sufficient information with order to facilitate accurate processing. Shipments are made on open account F.O.B. Oklahoma City when credit has been approved. On C.O.D. orders of \$25.00 or over, 1/3 down payment with order is required. Please include in check or money order sufficient postage and insurance for your Parcel Post Zone. Shipping weight, 5 lbs.

*International*  
 CRYSTAL MFG. CO., INC.

18 N. LEE • PHONE RE 6-3741 • OKLA. CITY, OKLA.

For further information, check number 13 on page 126.





## CM3 CONELRAD MONITOR and BROADCAST RECEIVER




*Complete Unit*

**NO INTERFERENCE  
WITH PRESENT EQUIPMENT**

Gives immediate warning as soon as your Conelrad station breaks its carrier—without the slightest interference with your transmitter. The Moradco CM3 Conelrad Monitor receives the entire AM broadcast band (550 to 1750 Kc), is complete in itself. Pre-set alert switch maintains constant vigil, sounds penetrating signal. Compact metal cabinet: 5 $\frac{7}{8}$ " wide, 4 $\frac{1}{8}$ " high, 7 $\frac{3}{8}$ " front to back, weighs only 4 $\frac{1}{2}$  lbs. packed for shipping. Standard 5-tube superheterodyne with added alarm circuit (6 tubes incl. rectifier).

*Plug it in Anywhere*

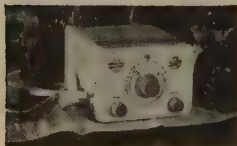

WRITE for  
descriptive folder.

Plugs into 110-volt line in your ham shack, living room, or bedroom. Loud, 1000-cycle tone will wake you out of a sound sleep if an emergency warning comes through. Choice of colors: Russet mahogany, African ivory, or gray hammertone.

**PRICE... \$39.95**

**MORROW** radio manufacturing company

P. O. BOX 1627

SALEM, OREGON

For further information, check number 14 on page 126.


**QSL** contest

WINNER



A one year subscription to CQ goes to this month's winner VE3MR for his beautiful and carefully planned card. The effect is magnificent with the bright red sine wave, the yellow circuit diagram and the blue background. Runners up win mainly our applause for excellent cards and an extra copy of CQ to flash at their friends.

LOSER

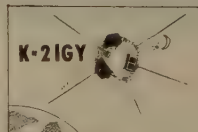



# New MORADCO

## SINGLE SIDEBAND MINIATURIZED 50 WATT TRANSMITTER 4 1/8" x 11-7/8" x 7 1/4"

### Model SBT for Fixed or Mobile Use




**Coverage:** 3.8-4.0, 7.1-7.3, 14.1-14.3, 21.200-21.400, 28.5-28.7 MC.

**Calibration:** VFO Calibrated, 0-200 Kc (add to frequency shown on band switch).

**Filter:** Uses a Mechanical Filter for Long Term Maximum Suppression of Unwanted Sideband.

**Emission:** Upper or Lower Sideband. CW-AM (SSB with Carrier Added).
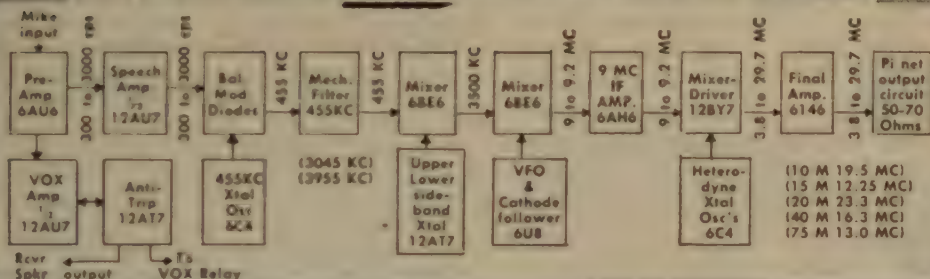
#### STREAMLINE DESIGN PROVES MONTHS OF MORROW RESEARCH



- Change bands, set drive and peak final, null carrier in about 30 seconds.
- Excellent voice-operated control system (VOX). Anti-trip of new, improved design, plus push-to-talk.
- Semi-automatic loading when changing bands designed for 50-70 ohms.
- Antenna (VOX) relay built in.

- By changing plugs in the universal power supply unit, the SBT operates as an exciter at about 10 watts output, or as a barefoot transmitter at about 50 watts output.
- Controls grouped for ease of operation.
- Same cabinet dimensions as MB6 and MB565: 4 1/8" x 11 7/8" x 7 1/4".
- Plug-in connections for easy removal from car.


## NEW

Power Supply Unit designed especially for the SBT Transmitter; regulates all the important voltages. Also supplies voltages for the receiver. This unit operates from 6 or 12 volts DC, or from 117 volts, 60 cycles. One cable and plug makes all the connections and changes from 6 to 12 volts.

SEE YOUR DEALER . . . or write Morrow Radio Mfg. Co. for full information on the SBT Transmitter.

**MORROW** radio manufacturing company  
P. O. Box 1627 Salem, Oregon




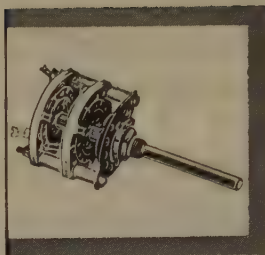
The  
**SWITCH**  
you need  
is carried  
by your



# Centralab

®

## DISTRIBUTOR

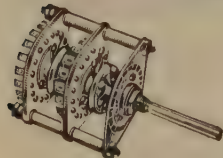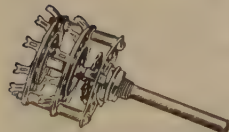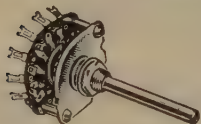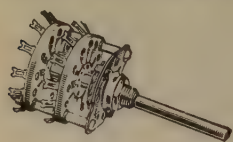

• The extensive CENTRALAB line of high reliability switches includes the unit you need. For ham applications, as well as industrial and military uses, you can depend on CENTRALAB switches. Sub-miniature, miniature, standard and heavy duty; rotary and lever action; ceramic and phenolic—your CENTRALAB distributor has them all. You'll find them listed in CENTRALAB's Catalog 30. If you don't have this catalog, write us or ask your distributor for a free copy.

# Centralab

®

A DIVISION OF GLOBE-UNION, INC.  
954K E. KEEFE AVE. • MILWAUKEE 1, WIS.

In Canada: 804 Mt. Pleasant Rd., Toronto, Ont.

SWITCHES • CERAMIC CAPACITORS • PACKAGED ELECTRONIC CIRCUITS  
CONTROLS • ENGINEERED CERAMICS • SEMI-CONDUCTOR PRODUCTS

For further information, check number 16 on page 126.

22 • CQ • October, 1958

## CLUB BULLETINS

Marvin D. Lipton, VE3DQX,

311 Rosemary Road, Toronto 10, Ontario, Canada.

A free CQ subscription will be sent each month to the individual submitting the best news item to this Department. The entire story should not exceed 2 or 3 sentences. News items, inventions, outstanding accomplishments, coincidences, extraordinary DX contacts, accident reports, new operating records, etc., is what we are after. All news accounts will be used to supplement CQ NEWS. The monthly winner's name will appear in this column, and in addition to the one year free subscription to CQ NEWS, he will receive a complimentary copy of the CQ news release carrying the winning episode. Send your news to the address above, not to the New York office.

The BISON, paper of the Indiana Radio Club Council, recently ran a paragraph about the "promote Indiana on the air" campaign. Indiana Hams are requested to interest out-of-state contacts in that W9 state. Indiana Amateurs forward the names and addresses of contacted Hams residing in "foreign states" to the Indiana Department of Conservation, on post cards supplied by that Department. The Conservation people take things from them. Here is a way to get on friendly terms with your State or Provincial Government; the Government that issues auto license plates.

Publications of all kinds comprise the membership of our news service. Radio Club bulletins, Mobile Clubs, Traffic Nets, Manufacturer's Wholesalers, DX ers, and SWL groups publish the 128 papers reaching us monthly. DX Hounds and SWL's not presently receiving one of these smaller bulletins are passing up a wealth of valuable information. If you fall in this category and if you would like to share the contents of a small DX or SWL bulletin, drop me a line and I'll refer you to an editor in your neighborhood. In most cases there is little or no subscription fee.

In the past month it was our pleasure to add the names of the papers noted below to the ever-increasing list of publications in the CQ news service. Welcome, HARMONICS, South Jersey R.A., THE SIDEBANDER, SSB.A.R., ATHENS JR. A.R.C., Assoc. member, THE YANKEE R.C. NEWS, Yankee R.C., PAHANDLE A.R.C., Assoc. member, LAKELAND GRAM, Lakeland A.R.Soc., RAGCHESTER, Nevada, A.R.A., and SKIP, Fresno A.R.C. I

73, Marv. VE3DQX

CQ NEWS, the official news release of the Club Bulletin Department, is issued monthly to full and associated members of the CQ News Service. Editors of Amateur Radio Club Publications are invited to join the News Service gratis. Amateur Radio Clubs not publishing bulletins may become associated members free of charge by notifying this Department. Contents of CQ NEWS are extracted from affiliated club bulletins. Associated members are granted full membership upon publication of a club paper.



# Match transmission line impedance— reduce SWR!

## they're new!

### Viking "MATCHBOXES"

- Provides more than 20 db of additional TVI harmonic suppression!
- Self-contained—complete with built-in directional coupler and indicator!
- Bandswitching—no plug-in coils!

put more useful  
RF into your antenna

These new Viking "Matchboxes" provide completely integrated antenna matching and switching systems for kilowatt or 275-watt transmitters. Units are complete with built-in directional coupler and indicator providing continuous monitoring of either incident or reflected transmission line power. Bandswitching 80, 40, 20, 15, and 11-10 meters and completely front panel controlled, these versatile "Matchboxes" quickly and easily match the transmitter to balanced or unbalanced lines over a wide range of antenna impedances. In addition, units are capable of tuning out large amounts of capacitive or inductive reactance. Revolutionary circuit design does away with the annoying use of "plug-in" coils and completely eliminates "load-tapping" necessary in other antenna couplers.

"Matchboxes" are also designed to provide separate matching of the antenna system to receiver. Self-contained, heavy duty change-over relay switches antenna from receiver to transmitter, grounding the receiver antenna terminal and muting the receiver while transmitting. Units are supplied wired and pre-tested only—complete instructions included.

CAT. NO.	POWER RATING IN WATTS	TRANSMISSION LINE IMPEDANCE IN OHMS	
		Balanced Line	Unbalanced Line
250-23 250-23-3	275	25 to 1500	25 to 3000
250-30 250-30-3	1000	50 to 1500	50 to 2000

**275 WATT "MATCHBOX"**—For transmitters with a maximum power input of 275 watts.

Cat. No. **Amateur Net**  
250-23-3 With built-in Directional Coupler & Indicator \$86.50  
250-23 Less built-in Directional Coupler & Indicator \$54.95

**KILOWATT "MATCHBOX"**—For transmitters with a maximum power input of 1000 watts. Antenna change-over system includes time delay circuit for relay, providing "fast make—slow break" action.

Cat. No. **Amateur Net**  
250-30-3 With built-in Directional Coupler & Indicator \$149.50  
250-30 Less built-in Directional Coupler & Indicator \$124.50


Write for your  
free copy of our big  
amateur catalog



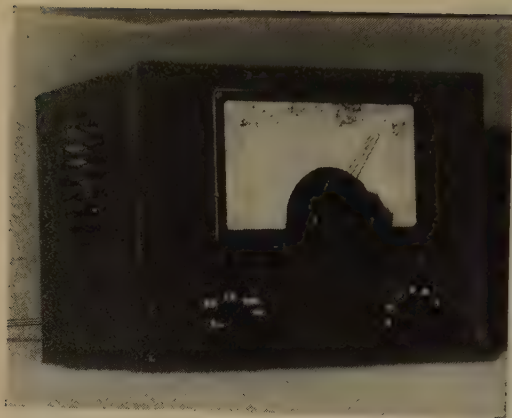**E. F. Johnson Company**

2931 SECOND AVENUE S.W. • WASECA, MINNESOTA

For further information, check number 21 on page 126.



# All-Band Conversion Exciter

**E. D. Crawfis, W7ATV**

RFD #2, Box 796

Phoenix, Ariz.

The idea of a conversion exciter certainly is not new. The writer first saw an article describing one in the February, 1938 issue of *Radio*. Since then, numerous similar articles have appeared, all describing some variation of the basic idea. The fundamental principle of such a device is quite simple. A stable variable frequency is obtained by beating a relatively low-frequency vfo against a high-frequency crystal and using either the sum or difference as the output frequency.

The writer has long thought that the designers of these exciters were overlooking an excellent opportunity by restricting their output to one band. By proper selection of frequencies, direct output may be obtained on several bands simply by switching crystals and tank circuits. Two models of such exciters have been built and used by the writer in the last few years, with very satisfying results.

The principal reason for using a band-switching conversion exciter is to eliminate the string of frequency multipliers usually associated with a multi-band exciter. Output may be obtained directly on any band by switching the crystal oscillator frequency and the mixer tank circuit. Other general advantages of a conversion exciter are: much better frequency stability on the higher-frequency bands, and break-in operation with continuously running oscillators, by keying the mixer.

Naturally, things are not as rosy as they seem with this scheme. Probably the most obnoxious fly in the ointment is the generation of undesired mixer products. The book says that if two frequencies are combined in a mixer stage, the output will contain the two original frequencies, and also their sum and difference frequencies. While this is true, it does not begin to tell the whole story. In practice, there are also an infinite number of other frequencies, including harmonics of the original frequencies, and such combinations as three times one frequency minus twice the other. While this is not a hopeless case, it does present a problem if one is to refrain from filling the radio-frequency spectrum with "birdies."

There are several angles of attack to this problem, all of which should be exploited to the fullest extent possible. These approaches are as follows:

- (1) Selection of a mixer whose characteristics approach square-law operation as closely as possible, to keep the relative amplitude of the higher-order mixer products as low as possible.
- (2) The use of as many good tuned circuits as possible between the mixer and the antenna, to further attenuate frequencies which fall near the desired pass-band.
- (3) Proper selection of the two oscillator frequencies to prevent as many undesired



To illustrate the use of the table, an example will be carried through. Suppose we want our mixer output to cover the range 7.0 to 7.3 mc. We choose 5.85 mc for our crystal frequency, because we happen to have a 5.85 mc crystal on hand. This calls for a vfo tuning range of 1.15 to 1.45 mc. We divide the extremes of the vfo tuning range by the crystal oscillator frequency and get approximately 0.20 to 0.25 for the range of oscillator frequency ratios. Examination of the table in this range shows us that we will get 5th, 6th, and 10th order products

This requires a vfo range of 3.8 to 4.1 mc. Now we divide the crystal oscillator frequency by the extremes of the vfo tuning range (because the table is set up to use the smaller of


Fig. 1

the two possible quotients), and come up with approximately 0.12 to 0.13 for the frequency ratio. Examining the table in this range shows that only 9th order products will fall in the desired pass-band. We conclude that we have picked a fairly good set of frequencies for our purpose this time.

This is not intended to be a how-to-build-it article, but rather to put across a few ideas which the experienced and progressive ham can use in designing a band-switching conversion exciter to meet his own requirements. This will be done by describing an actual exciter without going into all the constructional details. A block diagram of the exciter is shown in fig 2.

The vfo tunes over the range 3.5 to 4.5 mc. A low-pass filter is placed between the vfo and mixer to attenuate any harmonics which might be present in the output of the vfo. The cathode follower after the vfo provides isolation. The crystal oscillator uses a harmonic circuit because crystal harmonics are used on the higher-frequency bands to avoid using high-frequency crystals. The output stage is a cathode follower in order to provide a low output impedance to work into a matched coax cable of any length. On the 3.5 mc band, the frequency of the vfo is used directly, and the crystal oscillator is inoperative. A conventional pentagrid mixer is employed, and its plate circuit is tuned to the sum of the vfo and crystal oscillator frequencies.

Since the stability of the output frequency can never be any better than that of the vfo, a little care in the design and construction of this important stage will pay dividends. The author's vfo makes use of a modified Colpitts circuit in which the tube is effectively tapped down on the tank circuit. This circuit has one advantage over the Clapp circuit, in that it will tune over a wider range with less variation in output. The plate supply of the vfo should, of course, be regulated. Silver mica capacitors or their equivalent should be used in the tank circuit, which must be solidly constructed. The author used a

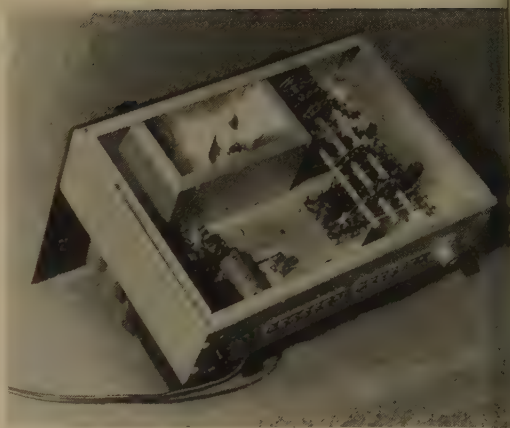

rugged double-spaced transmitting capacitor to tune his vfo, and the coil was wound on a grooved ceramic form. The entire tank circuit was shielded.

A cathode follower serves to isolate the vfo and also to provide impedance transformation to a level at which a practical low-pass filter can be constructed. The two-section filter, of the constant-k variety, has a cut-off frequency of about 6 mc. Its purpose is to remove harmonics from the vfo output.

The crystal oscillator is a conventional harmonic type. Since it is not used on the 3.5 mc band, the grid is grounded in this position. When operating the exciter on the 7 mc band, the crystal oscillator operates straight through on the crystal frequency. On the higher-frequency bands, the plate circuit is tuned to a harmonic of the crystal frequency. Coupling from the crystal oscillator to the mixer is adjusted to give proper injection grid current.

The mixer is coupled to the cathode follower output stage by means of over-coupled band-pass circuits. These circuits are carefully tuned and adjusted to provide reasonably flat response over each band, and to fall off sharply just outside the band edges. On the wider bands, resistance loading of the secondaries is necessary to achieve the desired characteristics. Probably a more satisfactory method of coupling would be to use single-tuned circuits ganged with the vfo tuning control.

The cathode follower output stage is simply an impedance transformer designed to couple into a terminated 70-ohm coax line of any length. Since the output of the exciter is quite low (in the order of one to two volts), a high-gain class-A amplifier must be hung on the other end of the coax. The author's transmitter has a 6AG7, which supplies enough power to drive a 6L6, either as a straight amplifier or as a doubler.

The design and construction of a conversion exciter, following the principles outlined above, should repay the experienced ham in endless hours of pleasant operating.





# MOBILING

H. T. (Tom) Orr, WØWET, K5HLG

5107 Junius St.  
Dallas 14, Texas

Sooner or later every amateur owns a means of transportation other than his two feet desires to place his hobby, or a portion of it, in the "wheel", whether it be automobile, truck, motorcycle, motor scooter, airplane, motorcycle or idie car.

The purpose of this article is not to describe how to eliminate ignition interference, build a new transmitter, or design a new mobile receiver but to point out some of the non-technical problems of being mobile.

Probably the most characteristic sign of the mobile amateur is the whip antenna. The big problem with whips is not loading coil losses but the fact that the American public believes that any person with a whip on his car is a law-enforcement officer. Many amateurs driving on a highway find themselves followed by a string of traffic afraid to pass. Just the sight of that whip at the rear of the favorite lovers' lanes makes everyone else drive away. Oh, well, there's nothing like privacy. On one occasion when other cars were being detoured around a block where firemen were fighting fire, I was directed into the block by a policeman who waved as I went by. It wasn't until I was surrounded by fire hoses that I realized that even the policeman thought I was part of the show.

The height of the whip is another problem. The amateur must adjust his driving habits to avoid the low telephone lines, tree limbs, underpass and drive-in banks. Some of the more popular arguments for the whip are overhanging light bulbs at service stations. I also have to my credit one overexposed light which was broken at the entrance to a drive-in movie. One amateur has a sway in his whip because of a heavy loading coil that when making a sharp turn, he occasionally is able to knock the hat off a pedestrian.

Those who drive to and from work or school usually find mobiling to be really great. Usually they talk with other amateurs in the same town doing the same thing. This is particularly good

for those who must drive through heavy traffic; the time spent is not all lost transit time, but just that much more hamming time. While others are cursing the long lines of traffic, the mobile amateur is enjoying his hobby.

Cross-country mobiling is usually somewhat different from the "in-town" type of mobiling. The attenuation of buildings and other objects is eliminated and distances worked increase. One of the problems of mobiling on any frequency below 10 meters is that usually a loading coil of some sort is necessary. While the airplanes have been using trailing antennas for years, few amateurs even consider such a thing. Just add enough wire to the end of the whip to make the antenna a quarter wave length on the desired band and drive away. On 15, 20 and 40 this is no problem, but generally cannot be used on 80 meters as a 50-foot wire hanging from a whip causes quite a stir among some local authorities. A piece of paper or cloth tied to the free end of the wire keeps it in the air as you drive along. Of course, many motorists will spot this wire and take it upon themselves to inform you that "some piece of wire" is hanging on your aerial. When they honk, shout and scream, just wave at them and smile; they'll soon get tired and go away. It's possible to use a different color of wire for each band and solder an alligator clip on one end for rapid connection. With this system the mobile signal compares with those of fixed stations.

CW mobile is very good in cross-country mobiling and can even be used in town with some success. In a car with automatic transmission CW mobile can be used almost anywhere. Those extra db really make the difference and operation is almost as good as at the home QTH. A key can be mounted on one end of a piece of board and the other end placed under the driver's right leg. With a little practice the sending can be as good as at the home QTH. A speed key can be used in cross-country mobiling with very good results.

Power seems to always be a problem in  
[Continued on page 125]



We arrive at the end of the road in Austin Pass,  
car crammed full of radio gear.

# DX-PEDITION TO AUSTIN PASS

**Ken Bale, W7VCB**

13427 7th Ave. So.  
Seattle 88, Wash.

Hanging up the sky wire. That's beautiful Mt. Shuksan behind.





forthwith comes the saga of a short range DX-Pedition to Austin Pass in the Mt. Baker National Forest area of North Western Washington State.

Austin Pass is literally the end of the road so peak high in the Cascade Mountain range between Mt. Baker and Mt. Shuksan. We went to DX-Pedition there for two main reasons. First the area is known for its phenomenal propagation characteristics and secondly it is open to access by car about two months during the late summer. The remainder of the year it is a very fine ski area covered with deep snow. Getting back to the extra-super propagation, the author and many others have experienced hearing such things as broadcast stations back in the east and middle west coming in loud and clear on the automobile



The author and photog Ken W7VCB. Timer clock perched on the antenna coupler reminds us to gas the putt putt generator. (Notice our favorite radio magazine on the table. CQ RADIO no less.)

receivers during the middle of the day. On the 160m bands, it is possible to get "loudest signals in the band" reports with just a few watts of power. In the past it has been likened to operating from an Aeromobile over a good salt flat location but with the added pleasure of being on the very solid ground.

We who made the trip were Don, W7LAN, Ken, extra-ordinaire, and myself Ken, W7VCB, just another ham. Plans called for the trip to be made Labor Day weekend when the snow would surely be melted away and plenty



W7LAN pounding brass on Kens rig. Most visitors thought we were really nuts. It helps to be half nuts on a DX-Pedition!

of fellows should be on the air.

Don planned to use his all Elmac mobile gear with A.C. power supplies, and I my Ranger-NC183D combo. Power by my 700 watt Kato-Lite. Rounding out the gear was assorted test gear, antenna couplers, spare tubes, and the usual tripe.

After dumping my XYI and harmonics with Dons XYI in Anacortes, we crammed everything into Don's Kaisermobile, and headed for the hills. As we moved out of the driveway, XYIs and Harmonics were shaking their heads and giving us that look so familiar to parting DX-Peditioners.

After getting well gassed up (on gasoline of course) we started climbing up the long long trail to our 6,000 foot camp. On the way we were able to keep in almost constant mobile contact on 75 meters with other fixed stations through out the Northwest. Many of the stations promised to look for us later in the day and to tell others to listen for us. A dead battery from too much mobiling didn't pose any problem. Should the battery be flat we could always coast down the 20 miles or more of hairpin turns charging the battery on the way.

Upon arriving up in the pass, we took a good

look around and decided to set up camp where we could view both Mt. Baker and Mt. Shuksan and still get perches for our antennas. If the bands should be dead or if the gear should fail, we could always enjoy the scenery. (See photos.) As it turned out we actually did experience a little bit of each. Band conditions were very poor and on the second day an eager bystander did put my rig off the air temporarily by hitting the key when I wasn't looking. I had been off pruning an antenna and the rig was not resonant.

Our QTH was laid out around the car, as there were snow banks on three sides. Don used his mobile gear as mounted in the car, but on A.C. power packs and I had my rig on a light card table to the rear of the car. The putt putt generator was put out in front of the car as far away as the power cables would permit. The exhaust pipe was aimed the opposite direction too and its putt putt putting could be heard echoing up the valleys for miles around.

For antennas, Don made up a multi-band dipole and strung it from a snow bank to a high rock pile. I used an end fed long wire running up to a stunted tree and of course at right angles to Don's dipole. Because of the close proximity of the two 60 watt stations, it was arranged that Don would operate 10-15-20 C.W. and I would use 40-80 fone. It worked out fine and at no time did we interfere with each other, although only about 15 feet apart.

Bad QRM from atmospherics and poor band conditions took away the chances of working any real DX. The best I could do on the low frequency bands was a good collection of western states and British Columbia. Don couldn't get out of the USA either but did hear some good ones.


Our only difficulties were some irate campers and a sudden rain storm. No it wasn't BCI-TVI trouble with the campers. They didn't like to listen to our putt-putt rattling up the hills and demanded we shut it off and leave it off. We tried to explain why we had to have the generator and why we were there but only a ham can understand those things. About an hour later one of them came stomping down out of the hills and moved his car over directly behind ours so its bumper almost touched my operating table. Then he tied down the horn ring, locked his car, and headed back up into the hills. He was back again in a few minutes and on the run because clouds of smoke were beginning to roll out of an overworked horn. A rain storm came up suddenly in the late afternoon that nearly erased my log-book and threatened to float me down the valley marine mobile style.

Because of very bad QRM and really lousy band conditions we secured early the first day with hopes of an early start the next day and better conditions.

At 0500 next morning we started the day with W6s for breakfast and VE7 for dessert.



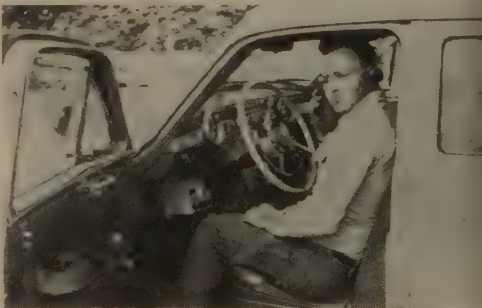Don checking the gas supply. Generator did wonderful job running two rigs together on full power. Mt. Baker 10,000 ft. plus in background.



Don W7LAN checking out the mobile to see how conditions would be.

A very FB QSO with VE7Itchy Monkey was one of the nicest of our entire trip. The campers were up early too and glaring down at us from above our own camp. Lucky they didn't think of starting an accidental landslide. They finally packed up and moved out later that morning.

Pickings were pretty slim and so we decided to secure after dinner. Conditions were at all time low and more and more tourists and hikers were heckling us. We spent so much time...

[Continued on page 125]



# 9,641 FCC Citations

Maurice J. Hindin, W6EUV

Amateur radio publications have recently been alerting the amateur fraternity to the coming of the international radio conferences. The international meetings always present the spectacle of various attacks on amateur bands from agencies which are covetous of the amateur frequencies. Amateur radio in the United States is well-established and is recognized as being a service to the public interest, convenience and necessity. Amateur radio likewise has received favorable recognition and support from the Federal Communications Commission. One of the reasons why it has received official support is the fact that regulating the amateur service has not imposed excessive burdens on the FCC administration. Likewise, a basic reason for regulation has not been a serious problem because of the historic effectiveness of the amateurs' self-policing activity. The term "self-policing", of course, is not literally correct. Under the laws of the United States, as they now stand, only the Federal Communications Commission has legal authority to regulate the amateur's activity. No amateur body has any disciplinary control over any individual amateur, and the weight and influence of amateur fraternal approval is a very strong element in keeping the amateur in line. Basically, the less governmental policing that is required of amateur activity the more favorable will be the amateur's position in official circles. Since it, therefore, becomes a matter of vital self-preservation that the amateur be a law-abiding citizen in the operation of his hobby, the author undertook a limited survey to ascertain the results as to just how effective amateur self-policing has been during the last five years.

The Federal Communications Commission operates on a fiscal year basis of July 1st to the 30th; hence, all statistics quoted in this report will be on that basis.

The 9,641 amateur violations were observed and reported by the Federal Communications Commission in the four-year period commencing July 1, 1952, and ending June 30, 1956. Each of the foregoing instances of observed amateur regulation violation resulted in a violation notice being sent to the amateur involved.

The Federal Communications Commission violation notices fall into three main categories. The first category is the form 790 which is an advisory notice of an unsatisfactory operating condition. This form of notice is used to advise amateurs of observed harmonic radiation, key clicks or other types of objectionable operating practices. The second cate-

gory is the form 792A Notice. This is an out-of-band notice and is used when the fundamental frequency of the transmitted signal is measured outside the limits of the amateur band. The third category is the form 793 Notice. This is a general citation form to notify the amateur of noncompliance with any of the rules and regulations except out-of-band operation. An analysis of the violations reported during the four years ending with June 30, 1956, is shown, as follows:

Year	Form 790	792A	793	Total
1953	526	79	487	1092
1954	629	90	524	1243
1955	1077	115	866	2058
1956	3308	159	1781	5248

From the foregoing statistics, it would appear that the year ending June 30, 1956, showed a sharp increase in violations over the immediately prior years. As a matter of fact, more than six times the number of 790 notices were given to amateurs in 1956 as were given in 1953. 1956 produced over twice as many form 792a notices as were issued in the year 1953. 1956 produced approximately four and a half times more citations of the form 793 variety as did the year 1953.

On the face of it, it would appear the amateur's violations are increasing at an alarming rate. These figures, however, may not necessarily reflect the true status of amateur activities. The increase in violations noted may well be the result of two factors. The first factor is the increased activity of monitoring stations operated by the commission. The second factor is the increase in amateur licensees.


Let us examine both of these possible causes. The Federal Communication monitoring stations do not devote their activities exclusively to monitoring amateur bands. The amount of time and the occasions upon which they do monitor the amateur bands depends upon the priority specified for such activity. The priority may change from time to time and depends upon many factors. If the priority given to monitoring amateur frequencies is raised, then more time is devoted by the monitoring station to amateur frequencies. More observation time and more stations engaged in monitoring services are bound to disclose more violations than would be discovered if less time and fewer stations were devoted to such work. It could not be determined if more monitoring time or more monitoring stations were used on amateur frequencies in 1956 than in prior years or if more violations were simply observed in the same monitoring time devoted.

*[Continued on page 115]*




Locate the hole by scribing cross lines. These not only tell you where to start the small hole, but are useful later in checking to see that a large hole is correctly centered.

*(Read across)*

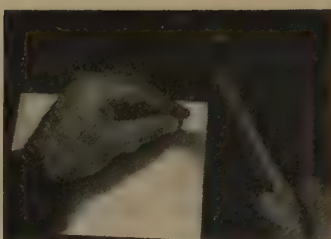

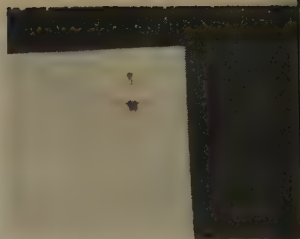
A hammer and nail will easily make a hole in an aluminum chassis.




The chassis bent down slightly around hole. If the chassis had been placed on a block of wood and supported from underneath at the time hole was punched it would not have bent down. Also, the hole is not centered to the cross scribed lines.

# BUILD EQUIPMENT ON KITCHEN TABLE? YES!

Nothing to it. Pictures show how.

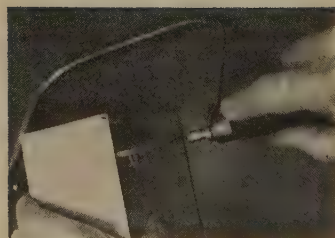

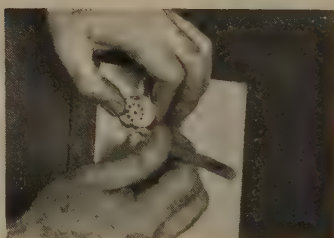To cut socket hole, coping saw is simple, easy and cheap tool.




To locate screw mounting hole for socket, put socket in place and scribe through mounting hole.

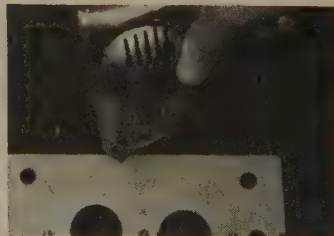
**A. D. Mayo, W5DF**  
209 Conti St., Jackson, Miss.



1/2 inch drill bit with 1/4 inch shank for use in small drills to make larger holes.



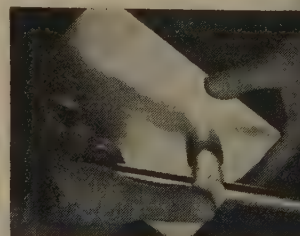Drifting, or elongating hole in cover plate with rotary file point in electric drill.



Screw type chassis punch makes socket holes easy.





Enter punching before making hole will minimize the chance of getting hole off center.




Small, round file will enlarge hole. Hole can be drifted to one side during this process if needed.



Simple drill makes holes easily in aluminum or steel. Examine drill point. If it is chipped or rounded have someone sharpen it for easy cutting.

**T**HOUSANDS of kits successfully assembled by hams testify to the soundness of home construction. Maybe you have an idea for a new device. Maybe you have only a magazine article and some parts. What's the difference between this and a kit? Seems to be mainly the fact that a new chassis has no holes where you want them. Photos show how to get holes in chassis with hand tools. Motorized tools merely make things easier.

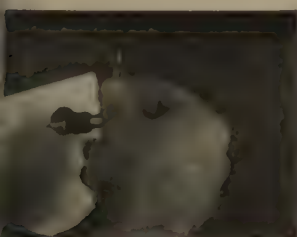


Machine screw and nut can be used to hold socket in place. This requires fumbling underneath with small nut. An easier method is to tap hole in chassis. Then threads are in chassis and no nut is needed.




A holder type screw driver starts screw in hole easily.



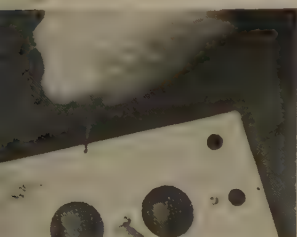
To make a ground connection to aluminum chassis, screw a lug to chassis and solder to lug.



Elongating hole with hand file.

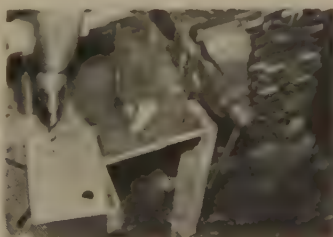

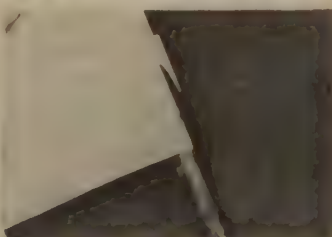Deluxe items for ham workshop. Drill press, heavy vice, work bench, and storage cabinet so something can be found when needed.



Aluminum roofing stock cut to size with tin snips. Roofing is a good source for aluminum stock. Most of it is thin but suitable for covers, shields, and small chassis. Sears Roebuck catalog number 13D M9682F.

# PUTTING THE AF-67 ON SIX

James Frederick, Jr., K4ELB

451 Ave. B. N.E.  
Winter Haven, Fla.

The migration to six meters in Central Florida led to an investigation of my brand new Multi-Products AF-67 for a possible conversion to six meters. This proved to be the perfect solution to the transmitter problem, as it eliminated the need for a separate transmitter for six meter operation.

An investigation of the Elmac circuit revealed several interesting facts. In the Elmac both the final plate and loading condensers are dual section units, one section of each is used for the higher frequency bands, and both sections for the lower frequency bands. This meant a better lc ratio would be possible for six meters. Also, because the Elmac had four tubes in the rf strip, it seemed possible to avoid doubling in the final amplifier. Last, but not least, the 160 meter position of the band switch could be used for the new six meter position, since there is no 160 meter operation permitted in this area.

Conversion to six meters was started with the final stage, working back to the oscillator. Everything went smoothly until the problem of a tuned circuit for the crystal oscillator came up. This at first seemed to be a major problem, since it must be switched out for the other bands. To complicate matters the oscillator band switch was inside the VFO housing.

The simple solution which resulted was to put the tuned circuit from the plate side of the crystal socket to ground. Since there were two crystal sockets in the Elmac, the coil could be switched out of the circuit by using crystal socket "X2" for six meters only, and crystal socket "X1" for all other bands. VFO operation was not considered because the VFO did not cover the frequency necessary for multiplying to six meters without modifications, and crystal operation was considered satisfactory. The oscillator plate coil was first grid-dipped to 8.3 mc, but proved to work better when resonated about 7.6 mc, as the stage had a tendency to cut out of oscillation when the coil was tuned too close to the crystal frequency. This coil must be grid-dipped only with the crystal switch in the "X2" position.

After final checking, the rig was fired up and adjusted for maximum grid drive with the final

high voltage off. To my surprise I had only three mils grid drive. High voltage was applied to the final and it dipped sharply into resonance. Power output on six was compared with the output on ten, and proved to be about the same.

Several other Elmacs have been converted in the same manner and all work equally well. It is a real potent signal squirter, accounting for 27 states, Canada, and Sweden to date on six meters. Assuming you are sold, proceed as follows:

Locate the crystal socket "X2" and connect coil L-a from the plate side to ground. (This is the top lug on this socket)

Next clip out resistor R-34, and install coil L-b, with condenser C-a in parallel with it from the terminal of switch SW-31 from which the resistor was removed to the junction of R-33 and C-35.

Remove the 160 meter coil, L-41, and use the form to wind new coil L-c. Reinstall the coil.

Note: in referring to switch terminals on switches SW-51 a, b, and c, terminals are counted from counter-clockwise to clockwise as viewed on the schematic diagram of the AF-67. As viewed from the rear of the transmitter terminal 6 on each wafer is just to the right of the mounting screw which passes through the three sections of the band switch. Section a is the wafer on top, b in the middle, and c on the bottom.

Next clip out the wire connecting switch terminals 4 & 5 to 6 on switch SW-51A. In the same manner, remove the wire connecting terminals 4 & 5 to 6 on switch SW-51C.

Next locate the 80-160 meter tank coil, L-53. Clip the wire which connects one end of L-53 to terminal 6 of switch SW-51B. Very carefully cut coil L-54 at the center tap, and remove the half which was used only for 160 meters. Do not remove the wire from the center of the coil which connects to terminal 5 of switch SW-51B. Disconnect the remaining wire on terminal 6 of SW-51B, and re-connect terminal 5 of SW-51B. Install the new 6 meter coil, L-d, from terminal 6 on switch SW-51B.

*[Continued on page 114]*



# A Quick Attachable Noise Limiter

E. H. Sommerfield, W2UQB

408 Day Hollow Road  
Lindcott, New York

Most automobile broadcast receivers are mounted in locations convenient for removal of tubes rather than for the addition of accessory circuitry. It was felt that any limiting device must be designed to be placed at the speaker terminal, which is easily accessible. The greatest service the limiter can perform is to prevent noise pulses from "ringing" the speaker cone. Though the noise pulses are usually short compared to the audio, accompanying ringing can mask the incoming audio. There is nothing new in this idea nor in the use of back-to-back diodes to limit these peaks. The variations of this circuit are in the use of a particular class of diode and the transformer. The diode is of the avalanche classification. Reference to fig 1, essentially no conduction takes place until a threshold of .25 volts for average diode. This is a power level of 15 watts across a 4 ohm voice coil. Strange as it may seem, this low value is ample audio in a car. Maximum voltage drop across the diode centers around .5 volts or 60 milliwatts of noise peaks, which is not enough to cause ringing in the "speaker". An auto transformer added to reduce this maximum level. By putting a resistance in series with the diode, the maximum level can be given a range of adjustment up to 60 milliwatts.

One of the disadvantages is a loss in audio level and low frequency response due to the transformer. This can be compensated for by boosting the volume control. There is also a certain amount of distortion on extra loud signals but the amount observed is tolerable. Reference to fig 2, it will be noticed that components have been added to permit silencing the receiver during transmission. With a 30 watt transmitter, it is improbable that the receiver will be damaged. I have operated a 100 watt sideband transmitter with the receiver connected identically with fig 3 for many years with no noticeable effects. Although I haven't tried other transformers, there should be no reason why any universal output transformer could not be used with approximately 1:1 "Z" ratio between the diode's tap and speaker tap both referenced to ground. For simplicity in construction and installation this circuit would be difficult to beat. ■


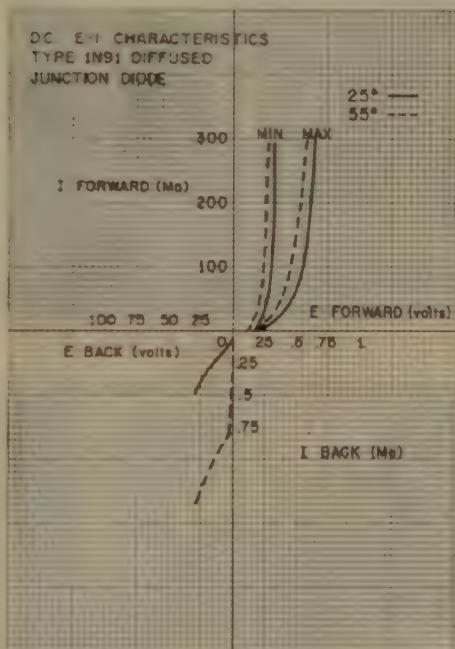


Fig. 1—DC E-I characteristics of Type 1N91 diffused junction diode used on quick-attachable noise limiter.




Fig. 2—Circuit diagram for quick-attachable noise limiter.

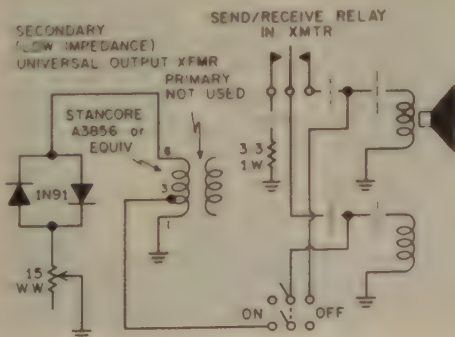
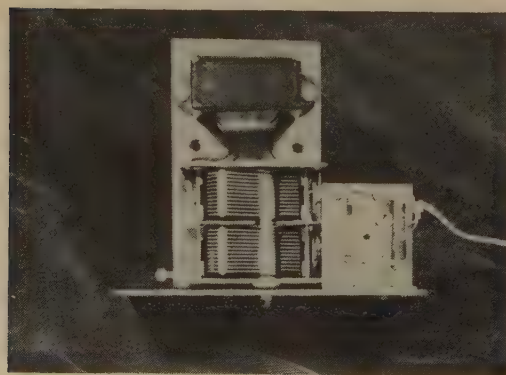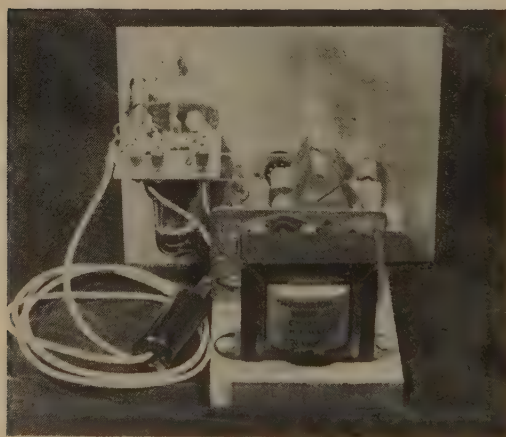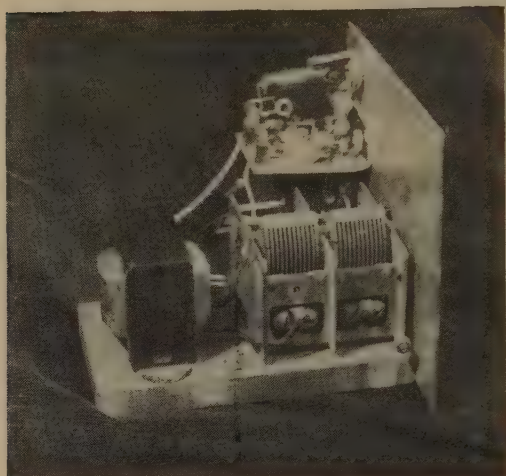
# A Tunable Audio Filter

Thomas E. Beling, W9AEI,

4619 Alexander Drive,  
Fort Wayne, Indiana



Probably the most congested portions of the entire radio spectrum are the 40 and 80 meter Novice cw bands. The number of stations per kilocycle is difficult to estimate, but, when propagation conditions are good, the situation can best be described as bedlam. From the viewpoint of the average Novice, reception is even more difficult than the number of stations would indicate. Most Novices cannot afford receivers with the extreme selectivity required to discriminate against interference only a few hundred cycles from the desired station. Since an outboard unit of some sort is indicated, an audio filter appears to be the logical choice. Selectivity can be made very good, although the high-Q chokes usually required are expensive. Also, most audio filters are limited to a single frequency, so that any tuning change required to compensate for transmitter or receiver drift must be made with either the main tuning knob of the receiver or the bfo pitch control. Usually, neither control provides the really fine tuning that is necessary if very high audio selectivity is used.

The little filter described here overcomes most of the disadvantages of conventional filters by employing a high inductance audio choke which is tuned at audio frequencies by a two-gang TRF broadcast capacitor. The filter network, consisting of  $L_1$ ,  $C_2$ , and  $R_3$ , is connected in a "bridged-T" circuit. The bridged-T has a response curve as shown in fig. 1. When correctly balanced it will not pass the frequency to which it is tuned. Theoretically, the rejection is infinite, but actually a small amount of voltage will get through due to capacity across the choke. The theory of the filter is this: at the null frequency of the bridged-T,  $V_{1A}$  operates as a cathode driven amplifier with a high gain.

At all other frequencies, there is a voltage on the grid of  $V_{1A}$  which reduces the gain through negative feedback. If the bridged-T is unbalanced by decreasing  $R_3$  to a too low value, regeneration and oscillation will occur. However, if the value of  $R_3$  is made higher than the correct value for balance, the effective selectivity will be reduced. This provides



easy way of reducing the filter selectivity under interference conditions are not too rare.

With the values shown, the filter is useful for the best notes in the range of 800-1100 cycles. The selectivity is poor at small values of  $f$  due to the shunt capacity of the choke. In operation, the control  $R$  is adjusted to a point considerably below oscillation. The signal is then carefully tuned in, and  $R$  is advanced to the point where the selectivity is as great as desired. Then  $C$  is carefully adjusted to make the signal at the peak of the filter response. If the receiver or transmitter signal drifts slightly,  $C$  can be adjusted to compensate for it. In general, if  $C$  is adjusted very slightly,  $R$  will require readjustment. When set for maximum selectivity, there is a very distinct ringing on the output. However, cw can be copied quite easily at a rate of 10-15 wpm, which is about as fast as one should go under severe interference conditions anyway. The filter really has to be used to be appreciated. With it, it is possible to make clean copy from signals which appear to be hopelessly buried with the filter switched out. Slight adjustments of  $C$  keep the signal really naked and all by itself as the receiver drifts slightly. Another advantage of an audio filter that is not commonly realized is that it increases the sensitivity of a receiver greatly. The ultimate sensitivity of a receiver depends on its ability to separate a signal from a noise. At low frequencies most of the noise we are concerned with is atmospheric or man made in origin, but reducing the bandwidth still has the effect of increasing the sensitivity of the receiver. To cite an example: with a typical receiver bandwidth of 3 kc this filter will produce an improvement in sensitivity of 18 db. The same result that would be obtained by boosting transmitter power 60 times.

Construction of the unit is not at all critical. The choke and capacitor were mounted on a phenolic board, but any insulating material would be satisfactory. The rotor of  $C$  must be rotating, of course. Power supply requirements are 150-250 V. @ 2 ma. and 6.3 V. @ .3A and may be obtained from any convenient source. In my case, I borrowed the power from the transmitter screen supply.

I designed this unit originally because I had persuaded my wife to get her Novice ticket, and so I became curious as to what went on in the jam-packed Novice bands. A few sessions in the melee convinced me that I needed something better than I had to make sense out of the confusion. This little gadget is simple and non-critical enough for any Novice to build, and will add immensely to operating pleasure in a crowded cw band.

My thanks to my good friend Ed Carr for the fine photographic work. ■

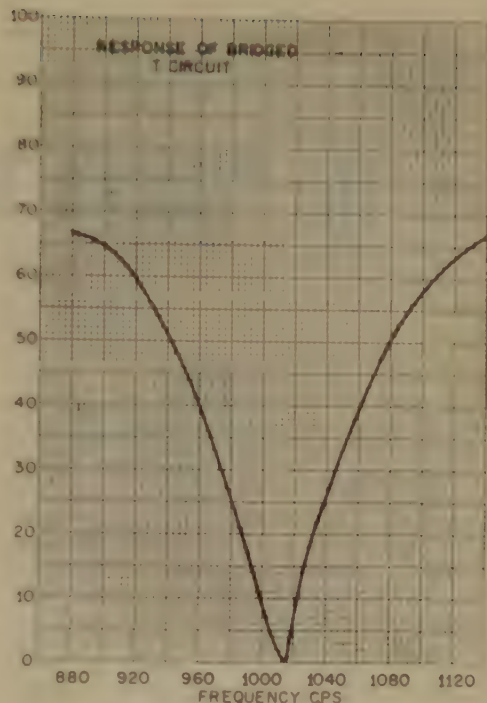


Fig. 1—The Bridged T network increases the receiver selectivity.

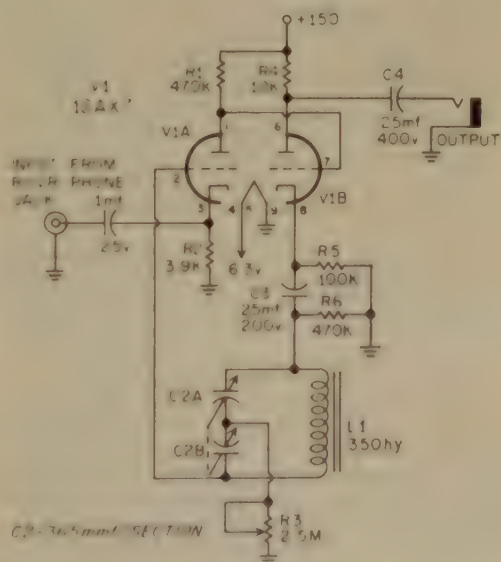


Fig. 2—The circuit diagram of the Tunable Audio Filter. An external power supply is required.

# The "Macy's Special" Patch

Will A. Connelly, W6QID

14529 Manecita Drive  
La Mirada, California

There is no question of the fact that 'phone-patch activity is on the upswing and that the services performed by hams with patches are gratefully accepted by their patch-less brethren. Some dandy 'phone patches have been described in the past, varying in complexity and cost but none do a more acceptable job than the "Macy's Special" . . . so named because of its low, low price of *only* \$2.98! Behold also, gentlemen, the ease of construction: mount a switch, a jack and do twenty minutes worth of wiring. What could possible be easier . . . save only filling out the subscription form on page XX?

The heart of the "Macy's Special" is an item only recently seen on the surplus market, the RM-52 Signal Corps Remote Control unit. This device consists of a case  $6\frac{1}{2}$ " x  $3\frac{1}{4}$ " x  $4\frac{1}{2}$ " overall which encloses a transformer, two condensers, a battery holder, a mike jack, a phone jack, two screw-type terminals and an SPDT switch. The whole unit is waterproof, an important consideration for those of you who run patches while skin-diving.\* The RM-52 is, in fact, a field telephone except that it lacks a handset, ringer and magneto. Although its original function is not known, it probably did a first-rate job of whatever it was supposed to do for the components are of the highest quality.

Lest some irate ham string up the author for incorrectly quoting costs, let it be said right now that \$2.98 covers the cost of a new RM-52\*\* only and that it is assumed that the average junk-box will yield a couple of garden-variety rf chokes, a couple of condensers, a standard phone plug, two resistors, and a PL-68 mike plug. If these items are not available, the total cost may run to as much as five or six dollars, depending upon how handily you dick with your local surplus emporium or fellow ham. Watch out for the latter! He may be building a "Macy's Special", too.

Perhaps a complete description of the patch is in order.

\*[here, here . . . ed]

\*\*RM-52's are probably available from:  
Fair Radio Sales  
132 S. Main Street  
Lima, Ohio

at \$2.98 each brand new or \$1.95 each used.

## The Line Section

Basically, a patch transfers audio *voltage* from the line to the transmitter when transmitting and audio *power* from the receiver output to the line while receiving. Telephone lines have a nominal impedance of 600 ohms so the 600 ohm transformer winding is used to make the connection to the line. While a patch *could* work with the transformer winding connected directly across the line, this must not be done for it presents a dc load to the line that looks exactly to the line like an off-the-hook telephone. Obviously, failing to disconnect the patch under these conditions would prevent dialing of your regular telephone (which depends upon intermittently opening and loading the line) and would create a busy signal for all incoming calls. If you're on a party line, you would also destroy your neighbor's telephone service. There is no surer way to get yourself in hot water with Ma Bell. To prevent this sort of horror, the two 4 mfd condensers found in the RM-52 are connected in series with the transformer 600 ohm primary winding.

Unless you are a pure genius and have a *perfectly* flat antenna line and *perfect* grounding and shielding for your rig, you are going to have *some* rf on the phone line when you are transmitting. Equally certain is the fact that somewhere in your transmitter audio you will rectify some of this rf and wind up with rf feedback. So it is also necessary to provide some filtering to keep the rf out of the transmitter audio. This chore is done by the rf choke and bypass in each leg of the transformer primary circuit.

## The Receiver Connections

Getting the audio from your receiver to the patch is simply a matter of running the audio from the 'phone jack or the speaker voice coil connections to the 150 ohm winding of the transformer. Don't worry about impedance mis-match; for all practical purposes, the only problem created by mis-matching is a loss of efficiency in power transfer. This is actually no problem at all, however, because you only need a small fraction of a watt of audio into the line and you won't have to be very efficient to handle *this* power! Your real concern should be directed toward holding the power *down* to a



el that won't cause cross-talk in the line. ore on this later.

No switching is needed in this circuit. It is necessary to break the speaker connection when the patch is in operation as long as you use some form of receiver muting in your station when you transmit. This is usually done by opening the receiver B plus, though any other arrangement which silences the receiver while you're on the air will do. The amount of phone line audio absorbed by the constant load of the 150 ohm secondary will not be serious if you have ample gain in your transmitter speech amplifier to compensate for this loss.

## The Transmitter Connections

In this circuit the transformer couples voltage from the phone line to your speech amplifier, utilizing the 4000 ohm winding. Again, a curious-looking mis-match occurs which is of no consequence. When connected to the phone line, with an average voice speaking at the other end, a half-volt or more of audio will be present across this winding. Your microphone only delivers a few millivolts when you talk at it, so instead of worrying about mis-match, we'll concern ourselves with getting this half-volt (or more) chopped down to a usable

level. This is done with the dividing network consisting of R1 and R2. In most cases, this network will bring the voltage which will appear at the speech grid down to a level that will necessitate little modification of your normal microphone gain control setting. If you find that you must drastically reset your gain control to prevent overmodulation or undermodulation, you may find it more convenient simply to wire in a 'patch gain' control instead of the network. We eventually did this so we could "ride gain" on the line without disturbing our normal mike settings. Incidentally, this network also "bridges out" the transformer to present a high impedance to the speech amplifier grid and, if the gain control is used, a capacitor should be provided as shown in fig. 1 to maintain a high impedance input at full patch gain. A switch pole is provided here to connect the transformer to your rig when the patch is in use and the microphone in normal station operation. The mike plugs into a standard phone jack on the front of the patch.

## Construction

Now, to the actual construction. Remove the unit from its case and discard the old batteries which may, or may not, have been left in the

1-MIC-PATCH SWITCH  
2-PATCH POSITION

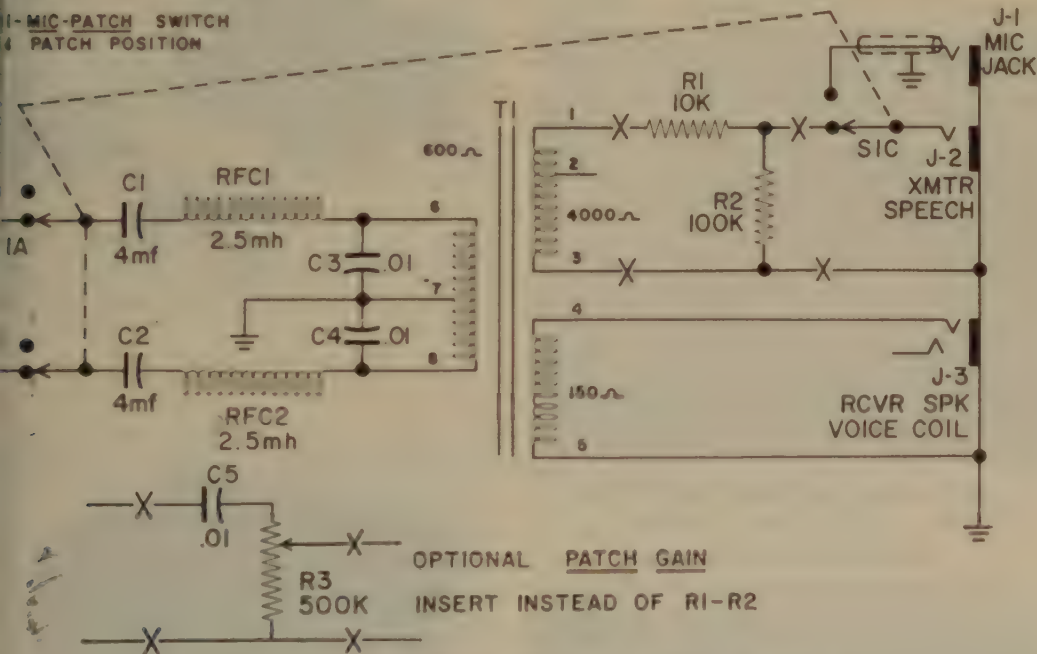


Fig. 1—Circuit diagram of the phone patch special. Network C5—R3 may be substituted for R1—R2 to permit the riding of gain.

## PARTS LIST

C2—4 mfd, 50V\*  
C3—100 mmfd to .01 mfd (Use identical parts)  
C4—.01 or larger

J1—Phone jack  
J2—Phone Jack\*  
J3—8 circuit jack\*  
R1—10,000 to 50,000 ohms, 1/2 W  
R2—10 times resistance R1

R3—Patch Gain Control (optional in lieu of R1-R2)—100K to 500K pot.  
RFC1, RFC2—RF chokes, 2.5 mh

S1—4PDT switch; Centralab 1458 or equal.  
T1—Transformer, 600 ohms to 250 or 4000 ohms and 150 ohms.\*



battery holder; RM-52's are somewhat corroded inside but none that we have seen, seriously so. At any rate, they're easy to clean up with a toothbrush and a solution of bicarbonate of soda. Clip the wires to the battery holder and remove it. This is worth saving, if it's clean enough, for a good many transistorized items require a 6 volt source. Now fire up your soldering iron and remove *all* the old circuit wiring; note that you must remove the two jacks to get to their terminals because of the rubber waterproofing seals. If you *don't* plan to run patches while operating underwater, just nip the seals away with a pair of dikes. Remove the SPDT switch. The part list calls for a Centralab 1458, 4 pole, 2 position switch which will cost about six-bits. If you have some other switch on hand (or switches, an SPDT and a DPST toggle, for example), there's no reason why you can't substitute if it will fit into the patch housing. If you do use the 1458, mount it  $\frac{3}{4}$ " in from one side of the patch; the screw mounting centers are  $1\frac{1}{2}$ " and the slot between the screw holes should be  $1-1/16$ " long by  $1/16$ " wide. Now drill a  $\frac{3}{8}$ " hole one inch from the opposite side of the patch and centered vertically on the panel. This is the mounting hole for the mike jack. If you substitute a volume control for the R1-R2 network, drill a  $\frac{3}{8}$ " mounting hole right smack in the center of the panel. The dirty work is done . . . you'll be testing in another 20 minutes. The remaining work consists of the simple wiring of the unit in accordance with the schematic. Note that electrical components which are not supplied in the patch are not critical and that the junk-box should be able to provide everything required within the barn-door tolerances allowable. Use shielded wire for the microphone and transmitter leads.

As soon as your Macy's Special is wired, visually check all the connections and then connect an ohmmeter to the two binding posts. Flip S1 to "PATCH" position and, after allowing a moment for C1 and C2 to charge, check the resistance: if it isn't infinite, *do not connect it to the telephone line* until you've found out what's awry and corrected the situation. The resistance must also be infinite with S1 in MICROPHONE position. You will only get into hot water unless you observe every precaution in keeping dc loads off the phone line.

### Installation and Operation

Now, before you fire up your Macy's Special, here's one point which you should inscribe indelibly on your mind (it may be burned in with a soldering iron if desired); *the audio power from your patch into the telephone line must never exceed 1 milliwatt*. This power will be present when an ac voltmeter connected across the line reads about 0.75 volts and is, in broadcast or telephone talk, zero level, zero VU or zero dbm—you pays yer money and takes yer chance but you *never* insert a higher

[Continued on page 112]

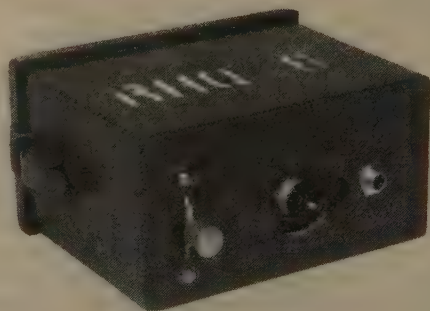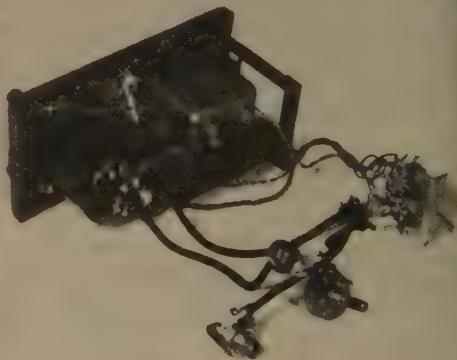

Three views of the completed patch. Note that the author used R3 for variable gain.



# All Band Mobile

## (Almost)

L. Chilton Jr., W5THI

22 Whittier St.  
Ft. Worth, Texas

About 5 years ago my wife presented me with twin girls (Two Happy Infants—W5THI) and I had to go out of the fixed station business. So I found a willing buyer for the Collins car and decided to go all out mobile. I have come up, after many modifications, solder ironing, etc., with an all band (almost) mobile. The rig starts out with a 1957 V8 air conditioned 4 door Plymouth. The receiving line to consist of a Gonset G66B receiver with an on-set 6 meter converter to give me coverage thru broadcast. In the trunk is a crystal controlled receiver on 29640 and on 2 meters, with squelch controls up front. The transmitter to consist of an AF67 covering 6 thru 30, plus a 2 meter crystal controlled unit in the trunk. I modified the AF67 to hit 6 meters. Other innovations include a Leece-Neville alternating system with ammeter and volt meter, panel mounted loop jack for transmitter hunts and conelrad control. The log book is carried in the glove box! The antennas consist of a 5BZO all band base loaded job, 10 meter whip on 29640, and 2 meter whip mounted center of top. I might say the fins on the 57 Plymouth make a FB place to mount antennas, if you can bear the stares from the curious public. ■



W5THI and his Plymouth. Note the 2 meter antenna on roof.



W5THI operating mobile standing still.

The 2 meter crystal controlled rig in trunk.



# Stop Those Harmonics

**E. H. Marriner, W6BLZ**

528 Colima Street  
La Jolla, California

**The Harmonicker** (GE Ham News Nov/Dec 1949, Vol 4-#6) circuit is becoming increasingly popular because more amateurs are using vertical and all band antenna systems. A dipole type antenna offers a great amount of attenuation to the second harmonic of the transmitted signal. The vertical and all-band type of antenna radiates all of the harmonics. The FCC has been issuing numerous citations because the harmonics of the lower amateur band 2nd harmonic signals are interfering with commercial stations.

Another good reason for using this harmonicker filter in place of the low pass type is for compatibility of urban living. There are 160,000 amateurs and many live within a few blocks of each other. It behooves us to help each other out by reducing interference as much as possible so both may enjoy his hobby. If one fellow is on 80, the other can work 40 if the other gents harmonics are down.

This type of filter will reduce the second harmonic 30 db. This attenuation to the second harmonic will help prevent overload in the double conversion receivers. The receiver generates spurious signals when overloaded and you will hear the other fellow all across the dial unless his signal is down. This simple filter will reduce other harmonics correspondingly each octave. It will give 48 db attenuation to the third harmonic, 59 db to the fourth, and 79 db attenuation to the eighth and down a long ways at the TV frequencies. This is theoretical, but in actual construction some rf may by-pass the filter if good construction is not followed.

There are several disadvantages to the harmonicker circuit. One unit is needed for each band. It is difficult to make any good rf switch which doesn't leak rf. Therefore separate boxes and connectors are needed for each band. Perhaps some ingenious manufacturer will put these filters on the market with a good switch.

The original harmonickers were designed

[Continued on page 96]


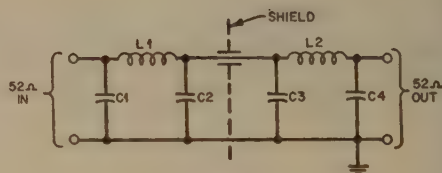


Fig. 1

## Parts List

Boxes	ICA Flexi-Mount cases Type 29439 2 1/4" x 2 1/4" x 5"
80 meters	C-1, C-2, C-3, C-4—800 mmfd each, Type DD Disc Ceramics 1000 v wkg. L-1, L-2—2.3 $\mu$ h each. 12 turns #808T Air Dux Miniductor coils. Illumitronic Co., Sunnyvale, Calif. (1" dia., 8 turns/inch)
40 meters	C-1, C-2, C-3, C-4—500 mmfd each, type CRL DD disk ceramic 1000 v wkg. L-1, L-2—1.0 $\mu$ hys each 11T of #508T Air Dux coils. (5/8" dia., 8 turns/inch)
20 meters	C-1, C-2, C-3, C-4—220 mmfd Type CRL DD disk ceramics 1000 v wkg. L-1, L-2—.55 $\mu$ hys each 10T of #408T Air Dux (1/2" dia., 8 turns/inch)
15 meters	C-1, C-2, C-3, C-4—150 mmfd disk ceramic CRL DD 1000 v wkg. L-1, L-2—.37 $\mu$ hys 7T of #504T Air Dux. (5/8" dia., 4 turns/inch)
10 meters	C-1, C-2, C-3, C-4—110 mmfd CRL DD disk ceramics 1000 v wkg. L-1, L-2—.28 $\mu$ hys Air Dux or 5 turns #504 (5/8" dia., 4 turns/inch)

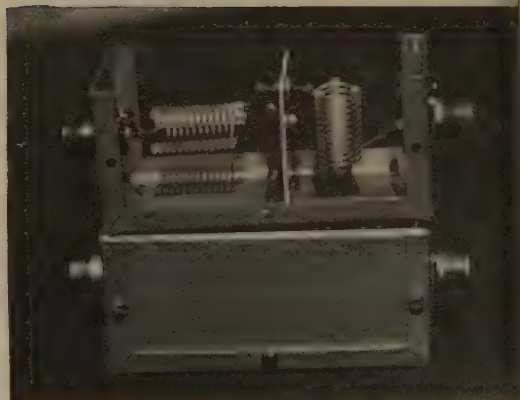

# The Vox-Break

President,  
R. F. Gilson Associates

President,  
R. F. Gilson Associates

**Modern methods of amateur communicating** streamlined "One-switch" stations are no longer in style. The time is now rapidly approaching when all stations, whether 'phone, A or both, will have to be equipped with a break-in system in order to achieve efficient station utilization.

The Aug. 26 issue of QST featured articles on both cw and phone break-in systems for amateur use. This article describes a Vox-dec adaptable to any type of amateur station. Referring to the circuit diagram of fig. 1, it is seen that the input to the (12AX7) two-stage speech amplifier has no grid input resistor. This feature was incorporated in order to cause no alteration of the transmitter speech amplifier input characteristics.

A (6A1.5) gating control tube is used in both modes of operation, one half for cw and the other for phone. Here the negative bias voltage as seen by the (12AU7) output tube grid through the phone—cw selector switch is sufficient to keep the output tube from drawing plate current in the absence of a phone or cw signal. In the 'phone case, one half of the output tube is wired as a diode which in the presence of speech voltage provides a ground return path for the phone portion of the gating tube. In the cw case, depressing the key provides the required grounding path. In both cases the negative bias on the output tube grid is reduced to the point where current flows actuating the plate circuit relay.

[Continued on page 106]

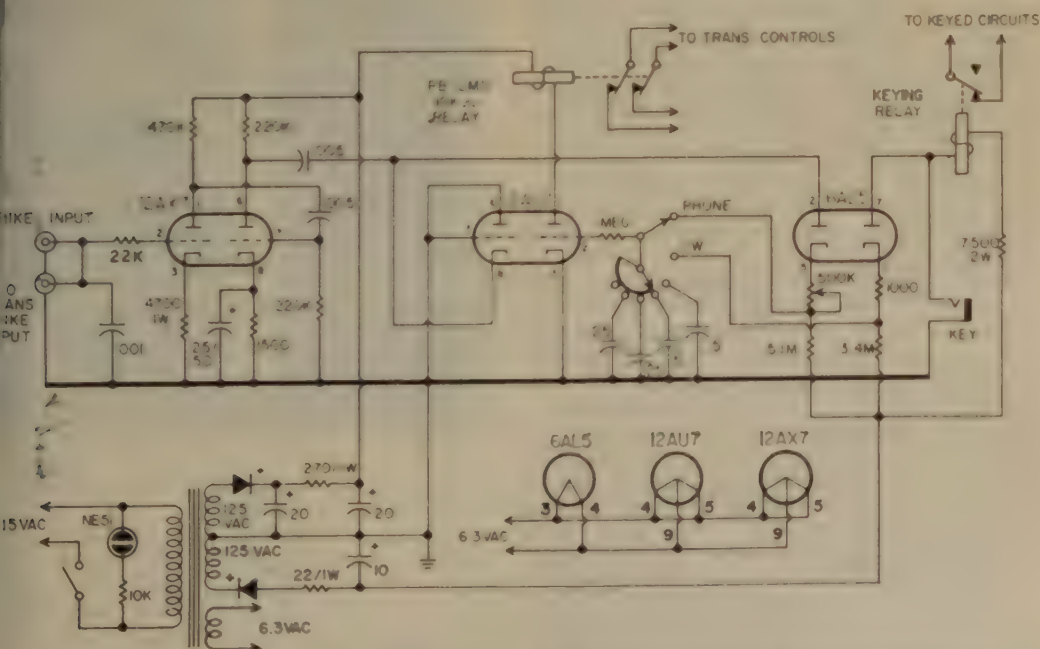


Fig. 1—Circuit of the Vox Break-in device. The pot in the 6AL5 cathode permits control over the audio gating level.

# THE MONOMATIC

A. L. Williamson, W8JVD

181 E. Wilson Bridge Rd.  
Worthington, Ohio

For many years I have experimented with various monitors for working cw but have never found any that would satisfy me. Therefore cw operation lately, on my rig, has been a rare event. Most monitors either have a short antenna, need to be tuned, or else must be coupled closely to a final amplifier. This of course is asking for trouble since any stray leads radiating harmonics would create a real TVI situation. A receiver could be used for monitoring but this becomes difficult if the other station operates about 10 kc away.

Being a firm believer in tuned "cloud warmers" with coax feed lines I have found that an swr bridge is a most useful piece of equipment. In addition this bridge, with the following inexpensive modifications, meets my requirements for a cw monitor.

The original bridge is of the type that can be left in the line for continuous observation of the swr. Physically the bridge is mounted behind the transmitter with shielded leads running to the meter located in front of the transmitter. With the cw key closed a signal is transmitted along the feed line and also through the bridge. Here a portion of the output is sampled providing a source of dc voltage that activates the meter for swr measurements. A check of the forward voltage at this particular meter (0-1 ma.) indicates there are 7 volts on 10 meters which drops to 1.5 volts on 40 meters. Between swr readings this voltage is available to power the monitor. This monitor consists of a simple transistor circuit using only a few common components which should cost no more than 3 dollars. The components may all be mounted on a 4 point terminal strip and installed inside the swr bridge meter case. A word of caution here: be sure to connect to the forward voltage point, observe proper polarity, and always turn off the monitor when taking swr readings since it does draw power and would cause an inaccurate reading. Notice that the monitor requires no tuning, no antenna, and no separate power supply. It will also operate on quite a range of voltages (1 to 22 v) using a CK-722 transistor. A clean signal of approximately 1000 cycles is generated without any noticeable change of amplitude on all bands from 10 to 40 meters.

Monitoring might be done in several ways on the "Monomatic." I use a single headphone and copy from my receiver speaker. A speaker and headphone set could be rigged with one phone for monitoring and the other (with separate cord to the receiver) for copying. Another method might be to eliminate the use of headphones entirely by designing a battery powered transistor amplifier/speaker system which could use the "Monomatic" as a driver.

Any way you might use the "Monomatic" I believe you'll find it has many advantages and a few, if any, of the disadvantages of other cw monitor systems.

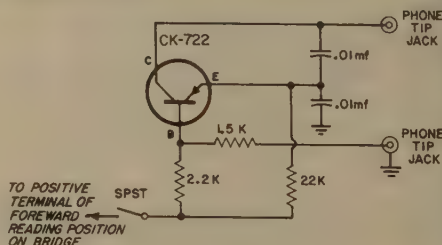


Fig. 1



# The 6AU8 Driver



Albert Newland, W2IHW

206 S. Highwood Ave.  
Glen Rock, New Jersey

Before building or modifying an existing 50 mc transmitter with the idea of using a 6U8 tube it might be worth while to study the following. A survey of some past articles shows the use of the 6U8 with voltages and currents similar to those of fig. 1. As may be seen, Resistor  $R_1$ , recommended by the International Crystal Co., when using the 6U8 as a 50 mc crystal is missing. This alone requires a voltage to be developed across the

crystal that is somewhat in excess of that recommended by the manufacturer. The high value of the pentode grid resistor and the high grid voltage is for the purpose of tripling and not straight through operation. This high value is to increase the harmonic content in the pentode section which is undesirable when operating straight through. The 6U8 is rated at 18 ma for the triode and 10 ma for the

[Continued on page 104]

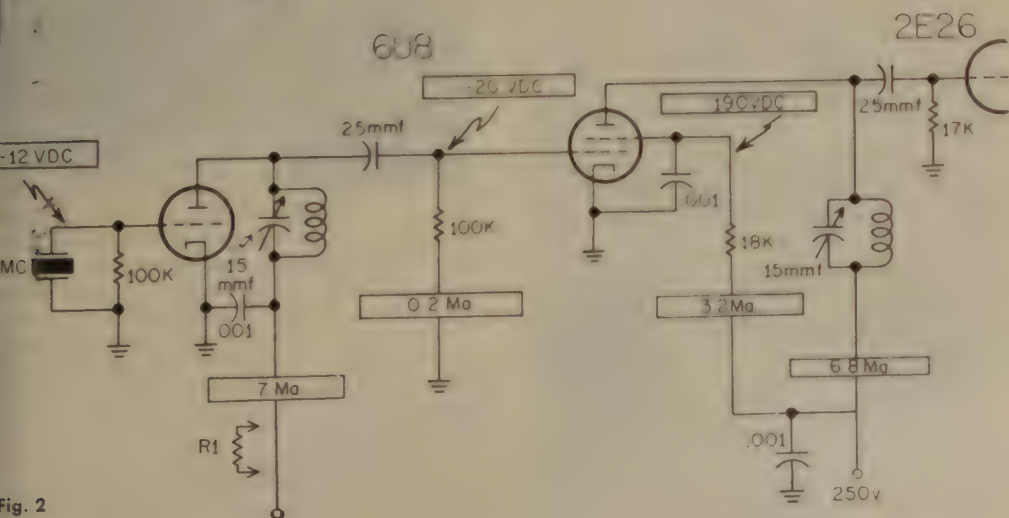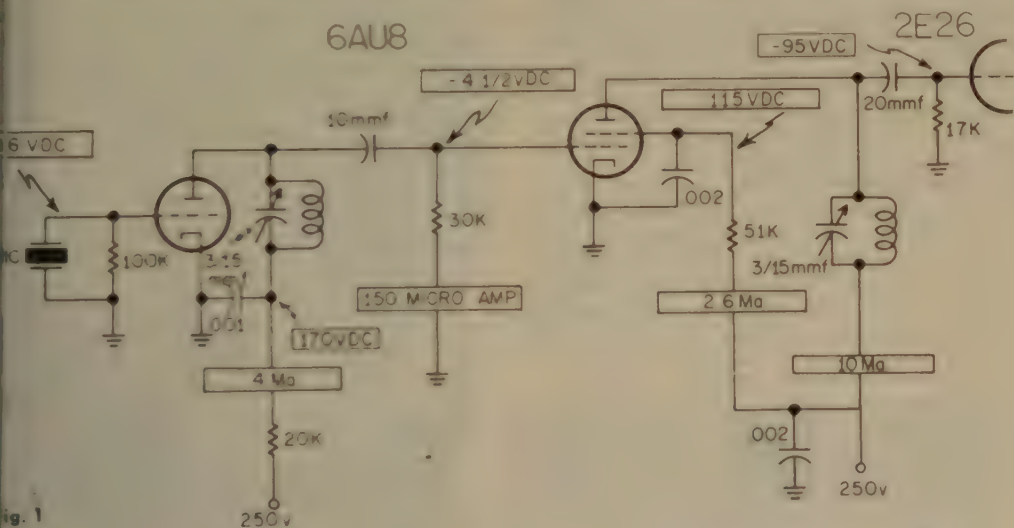

# WATER COOLED RIGS



**Paul M. Barton, W6JAT**


Jennings Radio  
P.O. Box 1278  
970 McLaughlin Ave.  
San Jose 8, Calif.

Some form of cooling the rig has been found necessary since the first spark rig zipped its tune.

Most of today's medium and high power rigs use air cooling from blowers. However, the noise from blowers is somewhat objectionable in a quiet (?) ham shack.

Water cooling has been common in commercial rigs for years. This overcomes the noise problem and substitutes a few other problems, such as leaks, etc. Fortunately, these new problems are not insurmountable. Like SSB, they just need getting used to. After becoming familiar with water cooling you may even find you prefer it to air cooling. It takes a lot of

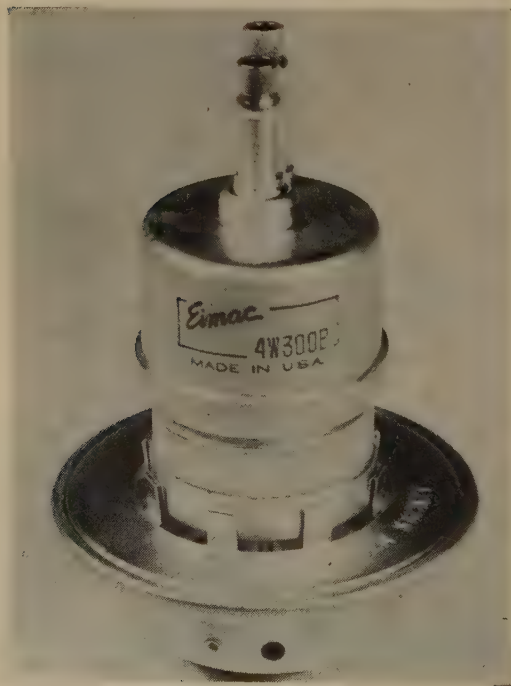air to do the cooling of a few quarts of water. About ten years ago, Jo Jennings, W6JAT and Lew Steward, W6JTQ discovered the beauty



ties of the 4X150A tube, and built up some of the smallest high power rigs in existence, using them. However, the blowers were large and noisy. So they removed the air radiator from a couple of 4X150A's and soldered on a copper water jacket. The results were so good that Eimac was encouraged to do the same thing. This eventually resulted in the Eimac 4W300B and 4CX300W. This may be the biggest little jug in the world.

It is thought that a pair of these little jugs installed in a Collins KWS-1 would be a vast improvement. The whole rig would run cool and the blower could be operated with a series



istor, cutting down the air noise.

Recently, Eimac has brought out the 4CX100A\* and its water cooled equivalent, still under an experimental number, the X703. These are possibly the most desirable tubes for high power ham rigs on the market today. Their size, stability, gain, efficiency, etc., are the greatest."

Why such a high power tube in a KW maximum rig? Why do they build a good "Hi fi" for home use with enough power capability for an auditorium? It's because good quality from a linear amplifier can only be had by



operating the amplifier well below its maximum capability.

If you are to operate *low level* AM under unmodulated conditions with 1KW input you will have about 333 watts output and 666 watts of plate dissipation, continuously. This is just about right for the 4CX1000 or X703.

For SSB operation, these tubes are just right for a legal gallon of high quality with low water co-efficient.

For water cooling, a gallon metal can, a small aquarium pump, or an electric fuel pump, and about eight feet of rubber hose make a complete system for a 4W300B. If you do lots of operating or run two 4W300B's with their water series, as in a KWS-1 modified, or if you use an X703, use a larger can. Be sure to ground the can to your rig.

Distilled water is not essential. The conductivity of tap water is usually low enough that the dc and rf leakage to ground through two four-foot lengths of hose in parallel is negligible. (2 megs for system shown with San Jose Water.) If your plate meter indicates over

See Jim Dandy amplifier using this tube in next month's Q.—Ed.



a few milliamperes of leakage, use longer lengths of rubber hose.

It is recommended that some water flow safety device be used to protect your tube. Commercial devices are expensive and sometimes not completely satisfactory for such a small volume system.

The can is aluminum, but a 5 gallon oil can or milk can would do very well. The size is not at all critical.

The pump is an immersion type aquarium pump. This particular one was made by Little Giant Vaporizer Company, Oklahoma City, Oklahoma. The one shown is Model 2, 110 vac, .75 amps and is sufficient for moderate operating or power. For more ambitious operation, use Model 3, 110 vac, 2.1 amps.

The water safety switch is more positive than most. The return water from the tube goes to a tubing in the water can lid. When the lid is in place, the water flows into the funnel attached to the arm of the micro switch. Micro switch #BZ2RW-A2, Minneapolis Honeywell Regulator Co. or local distribution. The micro switch contacts control the filaments of the tube. The funnel is formed of .010" copper and soft soldered. The hole in the bottom is about 1/4" and is not critical.

Your water system *must* be light tight. Light encourages the formation of "stuff." Let the experts name it. Your system should be maintained below 120°F as salts in the water will remain in solution and not coat the inside of your tube water jacket, like the inside of a tea kettle, below 120°F.



Even with water cooled anodes, it is recommended that some air be blown over the filament seal. Over-heating any part of the tube seriously shortens its life, and may cause it to gas up immediately. ■

# The Power Saving Voltage Dropper

Howard M. Felperin, K2KVG

202 No. High St.  
Mount Vernon, N. Y.

While browsing along New York's "Radio Row" one Saturday afternoon, I came upon a 6000 volt plate transformer with a somewhat unbelievable price tag of \$4.00. Why so cheap? Simple, no center tap. However, it was so appealing in its clean, gray, hermetically sealed case that I bought it anyway, all 40 pounds of it. Now the question was what to do with it. I reasoned that there must be a way to preserve its 500-1000 watt capabilities, while at the same time bypassing its two disadvantages, namely, the lack of a center tap, and the impractical voltage rating. The first problem could be solved by the use of a bridge rectifier, but the second was a bit more perplexing. How could I drop the secondary voltage into the practical region of 3000-4000 volts?

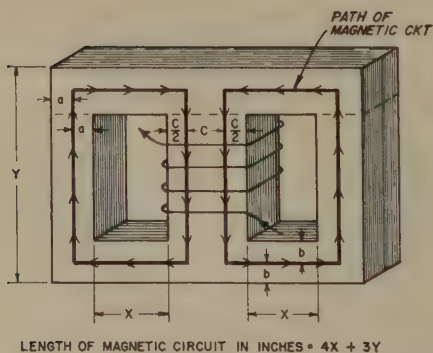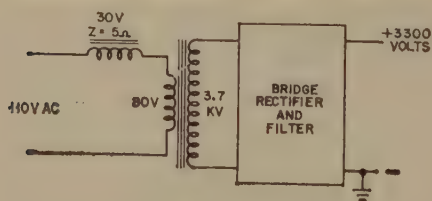

Immediately, I began scanning old copies of CQ and QST as well as the *Handbook*, but the only methods I was able to find were a resistor in series with the primary, or a filament toy train transformer connected so its secondary was in series with the primary of the power transformer and bucked the line voltage, hence dropping it by that amount. In order to draw 600 watts from the secondary, the primary current would have to be more than 6 amperes, and as much as 8 or 9 with the transformer operating at reduced voltage. The idea of a resistor in the primary was thus discarded, since to reduce the primary voltage by 30 volts would mean a resistor capable of dissipating a large quantity of useful power. While at the same time the toy transformer idea was impractical also, since its low voltage secondary must pass the same 8 or 9 amperes, and transformers like this are just not available. Of course, I could have rewound the whole secondary, but that seemed much too drastic a step. Now, what to do?

At this point I recalled that Ohm's Law applies equally well for impedance and reactance as for resistance. In accordance with this principle an inductor in series with the primary of the transformer could easily provide sufficient reactance to drop the voltage across the primary to approximately 80 volts. Also a well designed iron cored inductor would consume negligible power provided the dc resistance was low, as it would be when you consider that it need provide only 5 ohms impedance for a drop of about 30 volts. (See fig. 1).

Before proceeding to design a suitable inductor I purchased an old 6.3 volt, 5 ampere filament transformer for a dime (at the same place where I made the fateful purchase described earlier), removed all windings already on it, and exposed the steel core. Now to the design of the reactor. A digital computer would be desirable; a slide rule and full coffee pot could be tried as a substitute. First we must change 5 ohms impedance to an equivalent value of inductance. If #16 wire is used, then the r



inductance of the inductor will be negligible and we can consider the 5 ohms impedance as pure resistance. Hence in the formula  $X_L = 2\pi fL$  we can substitute  $X_L = 5$  ohms,  $2\pi = 6.28$ , 60 cycles. Thus  $5 = 6.28 \times 60 \times L$ , and after grinding the crank we come up with  $L = .013$  henries. To compute the inductance of an iron cored coil we find the formula (Radio Designer's Handbook, 4th Ed pp. 2-243).

where

N = number of turns

(a) a = effective cross sectional area of coil in square inches

(l) l = length of the magnetic circuit in inches (see Fig. 2)

$\mu$  = effective permeability

$$L = \frac{3.2 \times N^2 \times \mu a}{10^9 \times l}$$

Solving for N, we get

$$N = \sqrt{\frac{L \times l \times 10^9}{\mu a \times 3.2}}$$

The typical value of  $\mu$  in a core made of 4% silicon steel is about 400 (4% silicon steel is the standard core material at 60 cycles). (Reference Data For Radio Engineers 4th Ed. Page 285). In my particular core the length of the magnetic circuit was 11 inches, and the two window cutouts provided for a coil with cross sectional area of between 2.1 and 2.7 inches<sup>2</sup>. Taking the average, I used 2.4 for a. Now I could make substitutions, for L 0.013, a 2.4, l 11, 400. Plugging these values into the formula and solving for N, we get,

$$N = \sqrt{\frac{0.013 \times 11 \times 10^9}{400 \times 2.4 \times 3.2}}$$

Again we grind the crank and come up with  $N = \sqrt{4658}$  therefore  $N = 68$ .

Now we come to the actual winding of the inductor. I decided that #16 cotton covered wire represented the best compromise between current carrying capacity and ease of winding. I found that the easiest method of winding the reactor was as follows. I removed all of the laminations from the core and rearranged them so that all of the "E" units rested upon one another. Then I wound the coil on the cardboard tube from a wax paper roll, and pressed it snugly over the center section of the



"E" laminations, using only as many laminations as needed for the form to fit over tightly. I then replaced the "I" laminations by butting them against the "E" units and replacing the outer frame.

All that was left to do now was to test the little monster. With great apprehension I plugged in the line cord and carefully touched the test leads from the volt-meter to the transformer secondary terminals. Success! The reading was 3700 volts. There was only one flaw. The reactor emitted a loud hum which seemed to be caused by the vibration of the outer laminations against the frame. This was quickly remedied by placing a few layers of insulating tape between the two parts in order to absorb these vibrations. The inductor in actual operation only gradually warms up and then remains comparatively cool as it easily dissipates its small quantity of power.

The principle upon which this device operates lends itself to many applications. The reactor which I have described represents a problem within a problem, since it had to be designed to pass extremely high current. This factor made necessary the use of low gauge wire and hence a large core. In many applications the construction of a similar inductor is simplified, since the power involved is much less than 600 or 700 watts. To illustrate this,

[Continued on page 59]

# Mercury

## Rectifier

## Tests

**Paul M. Barton, W6JAT**

Jennings Radio  
P. O. Box 1278  
970 Mc Laughlin Ave.  
San Jose 8, Calif.

It has been found that mercury rectifiers, such as 857B, 872, 866, FG-105, etc., can be reliably tested by examining their firing voltage on an oscilloscope.

Light the filaments and allow to warm up *completely*—often many minutes more than is necessary for normal use.

Apply ac voltage across the tube through a suitable current limiting resistor. Increase the current to the rated maximum continuous duty

current for the rectifier. A 125 volt supply is quite satisfactory for this. Then put the oscilloscope directly from anode to cathode of the rectifier and observe the waveform.

The most meaningful pattern is seen when the scope is across the rectifier under test.

The sine wave starts to go positive and when it is far enough positive, the tube fires and the scope trace drops back to the DC tube drop. During the inverse half cycle, the negative

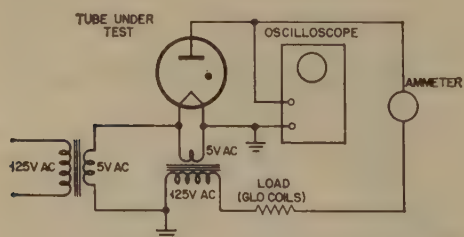


Fig. 1—Set up for observing waveform across the mercury vapor rectifier under test. Note the use of the filament transformer for plate voltage.


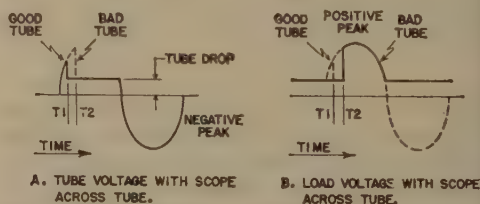


Fig. 2—Waveforms that should be developed across the load and tube. They may be compared with some actual scope waveforms shown on next page.

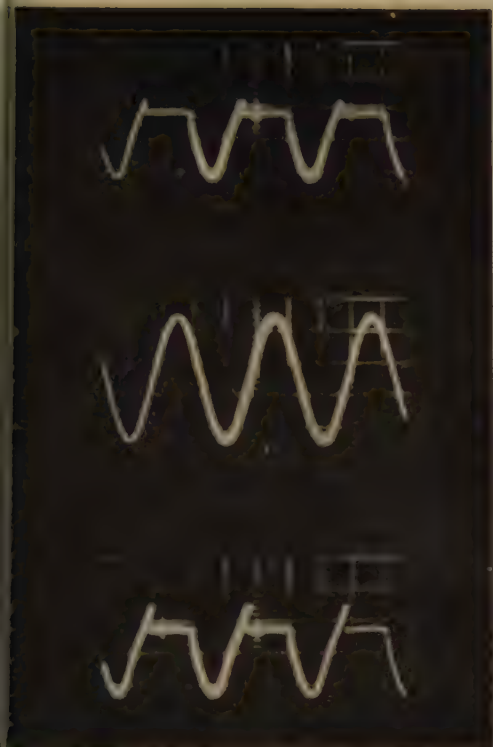



Read from top to bottom

Doubtful tube possibly good

Sine wave for comparison

Definitely bad tube



ac component in the dc output of a rectifier system and can be appreciable in some cases.

This test has been used very successfully to detect rectifiers that were likely to "invert" in service. The use of this test has materially reduced power supply breakdowns due to rectifier inversions.

It is important to test (& operate) these tubes at rated filament temperature. A low temperature increases the probability of inversion of the rectifier.

Mercury vapor rectifiers, particularly large ones like the 857 B, should, ideally, be brought up to filament temperature slowly. This reduces the likelihood of a drop of mercury getting under the oxide coating and raising the coating.


To prevent damage to the filaments from mercury, stored rectifiers should be brought up to heat for thirty minutes or more at least every 3 weeks.

Read from top to bottom

Good tube

Sine wave for comparison

Very bad tube (expanded scope trace)

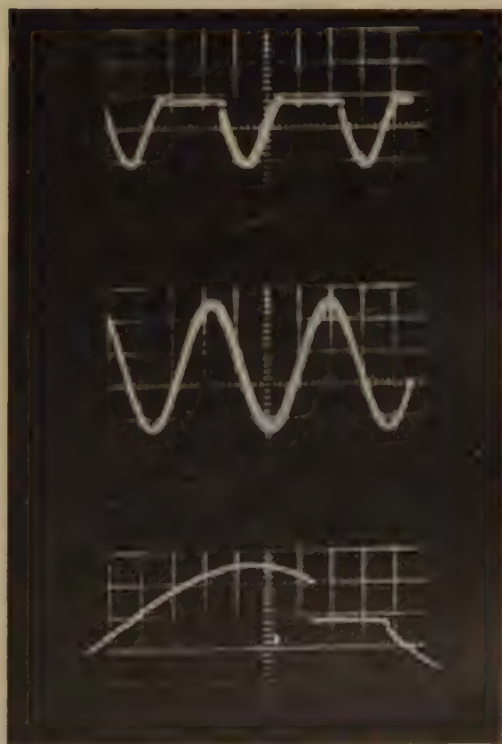

peak of the sine wave is seen on the trace.

The important point for this test is the height of this spike at the beginning of the positive peak. A "bad" tube will show a higher spike. A good tube will show a small spike.

For a given supply voltage and load resistor, a good tube will indicate a certain (pre-set) current. By comparison in the same setup, a marginal or bad tube will indicate a lower current. Normal variation between good tubes is about 5%. Bad tubes will be from 6% to 10% low with the same set-up.

For a new set-up to conduct this test, use known good and bad tubes for comparison, to become familiar with the size of the trace of the spike or overshoot voltage.

The firing voltage, as indicated by the height of the spike is related to the "hardness" of the tube, which is, in turn, related to its operating peak inverse voltage.

This spike, or overshoot, actually represents an

# Simple VOX for Sane Mobile Operation

Stan Bell, K6ESZ

5009 Grove Street  
Oakland, California

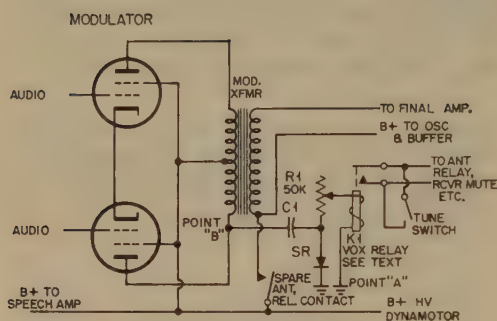


Figure 1 is a typical mobile transmitter employing push-pull modulators.

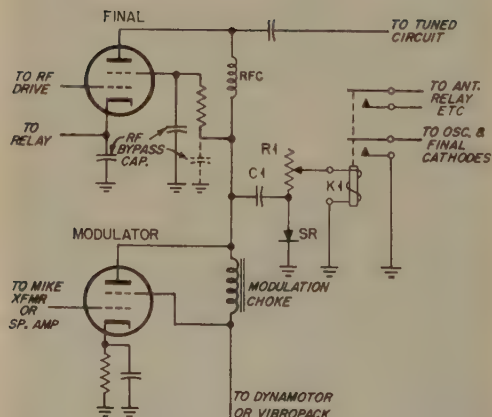


Figure 2 is a typical Heising modulated rig. Keying the rf section in the cathodes is convenient for VOX with single ended modulators.

This article could be titled, "Look Ma, No Hands" but I believe this would be carrying things too far. After all, I still need to turn my mobile rig on and off when I enter and leave the car.

In crowded traffic or on hairpin mountain turns I feel that a driver's hands should be on the wheel of the car and not gripping a microphone. To this end, I have put a very simple gadget on my rig which enables me to put my transmitter on the air without the use of my feet or hands—all I need do is to open my mouth and talk.

No complicated tube circuits are used in my voice-operated break-in scheme, nor is it necessary for me to continually worry about complicated adjustments.

Most mobile transmitters are put on the air with one or more relays which are actuated by pushing the button-switch on a hand-held microphone. Usually, one relay switches a common antenna between receiver and transmitter and at the same time starts the high-voltage dynamotor. Extra contacts on the relay may be used to mute the receiver.

In my system, the high-voltage dynamotor is turned on and left on; only supplying voltage for the modulator. Referring to the circuit diagram, it can be seen that when I speak into the microphone AF is generated which is the "motive power" to operate a relay which applies high voltage to the final, as well as operate the antenna relay and receiving mute contacts. It is as simple as that!

To use the rectified AF however, a small low current dry disk rectifier is needed. A 50,000 ohm potentiometer is used to set the "voice trip level" and works very effectively.

Proper adjustment of the potentiometer results when the receiver will not throw the transmitter on.

The relay used in the system is a surplus relay that will operate within a range of from twenty to sixty volts. Its coil will have a resistance running between 3000 and 12,000 ohms. Coils which do not draw more than 10 milliamperes will have little effect on the audio.

Although there may be concern over the amount of current drawn by the dynamotor while it feeds the modulator and is awaiting

[Continued on page 59]



# ALL IN A NAME

by Al Edwards, W2BOH

Bellerose, New York

VOJ is a Hollander, W1RL is a Dane and  
W7LEE is a Turk

Call ZS1PQ, if you want to work Dixie.

As item

Two Californians, K6LNM and W6LSL  
make New York!

Refreshments named after hams

Some of them are probably teetotalers)

ch W4IRH

arbon W5VYD

W1FAT

W6S1J

zer W9KHU

ers W9S1O

K6GSO

e W3YGW

mpagne K6DVI

W3HYU Sherry G6JK Martini W7IFW

Sweet K6MAA Dry W5TAA

Straight W5IOY

takes two hams to make a highball ...

h W9KCL

W7IKE

Two others will make applejack ...

le W9HQF

W6AHO

Shaker is W8Q1R

Flask is W3BNI

Glass is K2JNY

Bar is DL9EJ

erage and Cola are W1MGP and W2VZO

Note: K6GMG is not permitted to mix  
the drinks!

LOO may mix them but keep him away  
from the expensive stuff.

Shhhh ...

(W7MO is a Drinker)

Look up W3HRA if you want a Treat

ILQ and W5HVE will make Black Coffee  
together

very young hams:

W5AXB and W9IWF will make Lemon Ade

Motor Vehicles and Accessories named  
after hams

ee advertising for some cars and a truck)

ge W7BTV Lincoln W3SLU

d W5CHE Packard W6ISQ

h K4BAZ Studebaker W0GZR

tin W1AHX Hudson W9FFN

Buick	K21HR	DeSoto	K61MW
Chrysler	W1RHM	Jeep	W0EDT
Olds	W6JTM	Mack	K2ABS

Rolls-Royce K6BWC-W3SKF

Some of these may still be around ...

Moon	W2NVW	Maxwell	W3SZQ
Chandler	W4FLW	Durant	W2JCR
Hupp	K4GSP	Star	W3UWL
Chalmers	W3UMF	Pierce	W3LNZ
Mercer	K4EDW	Graham	W4FDA
Franklin	K4GSO	Paige	W3QMS

Start is W0WZJ ... Stall is W0JER

Speed is W4BIP ... Park is W0EAR

Driver is W9GDQ ... Passenger is W3LOD

... Parts and Accessories ...

Brake	W9VMS	Dimmer	G3ERJ
Piston	W3IEJ	Horn	K2BDP
Spring	W6IRD	Heater	W4WHI
Shackle	G2DVQ	Hub	DL9OG
Pump	W8IXK	Trim	W1ATC
Rocker	W2MNU	Carrier	K6CLY

Fender and Hood are W6NUK and W0QOY

... Dash is WN3DTP

Lock and Key are K6JGT and W7WUA ...

Jack is K1KXR

Van-W9IGK Hack-K2BP Buggy is W3KZ

Rumble and Knock are W9LHS and W3SDU

Rattles is W0ZW1

Bump and Dent are W7VOY and W4VJU

Wham and Smack are K4EJB - W3AYS

(For Service, call W4IE or W2MTY)

Tires and Tubes?

Fisk	K2CRK	Goodyear	K4IDQ
Lee	W4IK	Firesone	W2UYH
Dunlop	ZL4FY	Goodrich	W4SPV

We wonder if any of these hams  
are what their names indicate?

Alderman	W4BVK	Miller	K4ABO
Baker	W5YCC	Miner	W9DIDA
Banker	W3BHV	Monk	W0J1L
Barber	W8ALY	Nurse	W9YNK
Bishop	W2VUW	Painter	K61YC
Bookbinder	W6GSV	Parson	W9DEI
Boss	K2GHM	Pastor	W2KCN
Brewer	W0AG	Pilot	K2EDQ

Butcher	W81WJ	Porter	W0AGG
Butler	K5DHK	Postman	K2ALY
Carpenter	W8AA	Priest	W0DGR
Chancellor	W51M	Purser	W4TWP
Collier	W0EG	Rector	W0LKF
Constable	W7UYV	Sailor	K4HXP

Cook	W5DDU	Seaman	WØRDZ
Dancer	WN8BKT	Sergeant	WØWAJ
Deacon	K4BSZ	Sexton	W7VCR
Ensign	K2ABX	Shepherd	W7TXH
Farmer	WØYCT	Sheriff	W9FLI
Foreman	W8WZK	Shoemaker	W9WAR
Glazier	W2OXP	Showman	W3PVG
Guide	W1YVE	Singer	W2RQJ
Hunter	W2TH	Skipper	W6KF
Judge	W2GIC	Steward	W4AFI
Knitter	W9AGR	Stoker	W5AFS
Lawyer	WN3FTL	Usher	W4JMH
Major	W9NEO	Warden	WØYYF
Mason	K2AFO	Weaver	W1AKL
Mayor	K2DJD	Workman	W7MFD
Merchant	W2LGF	Writer	W6TRU
Messenger	W3AGF	Yeoman	WØQWY

KNØCEG is a Sportsman  
W1WUA is an Earl  
W7AAP is a Duke  
W9FGF is a Baron  
W3RT is a Knight  
K5DTV is a Prince  
VE3AWN is a Sovereign

#### Music and Dance terms named after hams:

Music	W7UUO
Band	W2PTJ
Melody	W9EXO
Medley	W9FYH
Tune	W4GUB
Horn	W2LLA
Pipes	K9ARB
Fife	WØOSD
Drum	W2AZB
Viola	K6DGO
Organ	W1JBP
Gong	W6TPW
Harp	W5ICC
Minor	W4HRB
Major	W9NEO
Scales	W1BOB
Treble	K2GSM
Sharp	K6CAE
Keys	W8MYL
Sing	W7OOA
Alto	VE8TS
Bass	K4EKU
Dance	W3YQU
Swing	W2OWM
Whirl	WN3FCE
Waltz	W6JIY
Peabody	W6JUW

Rock and Roll are DL4MX and W2DPZ

List of hams whose names are used in games.  
(Indoor type)

Chess:	
King	W2LTJ
Queen	W2OUX
Bishop	W89XM
Knight	W1VMG
Rook	W2JMQ
or	
Castle	WØGDA

No Pawn has a ticket.

The term 'Check' was donated by W3NBJ.  
Mr. Chess is W3WKX!

Cards:	
Hand	K6EH
Bridge	K2IQA
Deck	W1RAC
Deal	WØOZK
Trump	W3VLT
Spade	W9PIL
Diamond	W2BRY
Club	W6HGY
Meld	W2HHA
Pass	WØMSA
King	W2JW
Queen	K4BAF
Jack	W6AHO

Who is a Joker?

W1DRO is a Card!

There would be plenty of Hearts if certain hams  
would spell their names correctly!

Names of hams with ham terms for names:

Gear	KØBXM	Tester	W9BIE
Driver	K6GNK	Current	W4VNN
Slicer	W3UL	Ohms	W9DA
Trimmer	W1SCZ	Watts	W7AQ
Patch	W8BPD	Power	WØVFI
Crystal	W6KJY	Plate	W2RR
Key	W5CDO	Blower	W2AX
Signal	Z13HB	Clamp	W5NF
Carrier	K6BKQ	Dial	K5AD
Gain	W6KFN	Coil	K2QF
Peak	W1BWN	Link	W2VK
Null	W8VKP	Loop	WØZL
Hum	G5UM		
Ripple	W9SIZ		
Shields	KØCNH	Pole	W2ZQ
Tower	W2HJG	Guy	W3JO
Beam	K2BX	Cable	K4BK
Boom	W6BHS	Zepp	W4OO

Shock is WØJWF

Spark is W9UWK

Lines and Mains are W2EIQ and W6ARJ

Band Hopper — W2SMN & W2ZXZ

Call Book — WØMBW & WØSPP

High Pass — WØWWB & WØMSB

Hobby Shack — W9KCU & W9AVY

K2HMH is S9 plus

Hardware and Tools for hams:

Brace	WØFJY	Bolt	W1DGA
Drill	K9CLS	Rivet	VE2SN
File	W9PMN	Washer	VE2AS
Reamer	K2MOE	Staples	W4IDE
Wrench	WØMQB	Screws	W5UQ
Hammer	W9AUU	Pulley	W2TQC
Vice	W5VCE	Hook	W6DJC
Punch	G6UR	Rod	W2KVY
Solder	G5FA	Fitting	W1NJS

Putting hams' names together ...

... to make a common expression:

Candy and Cake	VE2QC	es	G3CNO
Ways and Means	W3ANL	es	K4ARC
Hope and Pray	WØPAA	es	K6GTJ
Hunt and Fish	W4ROA	es	K6EYS
Rod and Reel	W2KVY	es	KN4IAL
Hug and Kiss	W5CFQ	es	W2REZ
Kiss and Tell	W9JEI	es	W6IEC
Ham and Swiss	W1RRX	es	WTIUW
Wit and Wisdom	W3BTC	es	K6KDO
Lock and Key	W4YPX	es	WØSGJ



Look and Eye	W2NPF	es	W3PSX
Bank and File	W8VQG	es	W4KBJ
Adam and Eve	DJ2UF	es	VK2JC
One and Dandy	K2CWS	es	G3BJB
Lock and Roll	K2EKR	es	W5ULH
Alt and Pepper	Z1ICK	es	W7JDC
Look and See	W4PCZ	es	W5LTD
Gold and Silver	W2IHX	es	K2AXI
Locks and Bonds	K4HLO	es	WN7AJ
Idle and Handy	W5RDS	es	W5GPG
Tough and Ready	Z13DT	es	W7IES
Fun and Ache	G3ATH	es	W3NEC
Life and Drum	W7IDI	es	W2AZB

To express opposite conditions:

Rich or Poor	W4OSJ	es	W6JSO
Black or White	K4HHV	es	W5CCR
High or Low	W3FJI	es	K6GBI
Sharp or Dull	W6LNF	es	W2PHW
Tout or Slim	W5SFQ	es	DL2XY
Long or Short	W2JBY	es	W7BCU
Old or New	W8VDL	es	W4SRM
Broad or Narrow	W4KTN	es	K4AG
Senior or Junior	W2VUM	es	W2HPS
Straight or Bent	W5IOY	es	W7IES
Walk or Ride	W5SZB	es	VK3NH
Damp or Dry	W2VVK	es	W5TAA
Low or Stern	VE7KJ	es	K2LMA
Full or Dole	W2WW	es	W2JNC
Bright or Dull	W2QPI	es	W2PHW
Early or Tardy	W4YKR	es	W6JLA
Sweet or Tart	K6MAA	es	K2CFP
Lead or Foot	K4AOC	es	VK3ZAL
Young or Old	K6OAR	es	W5LAN
Real or Fake	W6PUY	es	W2EQP

What do you know, they are naming colors after radio amateurs.

	W2ABS
	W8LXJ
	W7AVB
n	W2NSD
vn	W7AMZ
age	W3DF
nder	W5WXA
nition	W7KBR
ie	W5CCR
Black	W1LQ
MPN is Blacker	

Note:

No Red is licensed, but some use this for a nickname like W6HJY.

Associated terms:

K6DTR
W2LCV
W4PNT
W2YGP

AMPLE VOX [from page 56]

For final current, there need be no alarm unless the dynamotor is one of those which would frighten off the largest battery. However, if you use a class B type modulator or one in class AB<sub>2</sub>, current demands are great.

For tuning up, a switch is merely paralleled across the switch contacts supplying the high-voltage for the final.

No sir! there is nothing like operating mo-

bile with both hands on the wheel; your eyes on the road and alert for any emergency. It only takes a regular operator's headset or a chest microphone easily made out of a pair of coat hangers and the few parts shown in the diagram.

## INSTALLATION NOTES

1. See that audio is available to throw the relay.

Plate voltage must be supplied to the modulator and speech amplifier stages, (if any), on standby as well as after the relay has thrown. If the speech amp will not stand full voltage install a dropping resistor and bypass.

2. Select C<sub>1</sub> large enough to cause the relay to stay closed between words after R<sub>1</sub> has been set.

For mobile operation it is safer if the relay drops out between sentences; emergency breaks then are possible. Your voice governs the value of C<sub>1</sub> but expect values of 8 to 20 mfd.

3. For high powered rigs it is convenient to connect point "A" of fig. 1 to the modulator supply line rather than ground. This makes it possible to use a condenser rated at 150 volts rather than one rated for the full supply voltage.

4. Smoother operation may result with point "B" connected to either modulator plate lead so try both.

Install this simple system of voice operated control and you'll be glad you did! ■

## POWER [from page 53]

assume that you need a 5 volt, 6 ampere filament transformer, and you have a 6.3 volt transformer which is capable of supplying the necessary current. You guessed it; just wind a coil and place it in the primary of the 6.3 volt transformer. And remember, there are only 30 watts involved, so the reactor need only be designed to pass about 300 mils. This inductor could be wound very conveniently on a ferrite core.

If, however, the reactor is to be wound on an iron core, there is one thing to look out for, saturation of the core material. All core materials have what is known as a BH characteristic or curve which plots the flux density against the magnetizing force within the core. If the core is being operated within the linear portion of the curve of the material of which it is made, everything will be fine, but if the core is being operated in the region where the BH curve flattens out, anything can happen. The way to avoid this is to use a core which comes from a transformer whose total ampere turns are more than the total ampere turns in your inductor. (See Reference Data for Radio Engineers, 4th Edition pp. 324-326). ■



## semiconductors

by DONALD L. STONER, W6TJ

P.O. Box 137, Ontario, C

Circuits for transistorized ham gear continue to arrive for this column, and several of the more interesting devices are reproduced this month. I should point out that these circuits have not been tested by the author and I cannot assume responsibility if you slash your wrists trying to get such a unit to work. Additional information can only be supplied by the contributor.

W6AHO, 653½ Sunset in Venice, California, leads the column with a clever device to generate harmonics of a 100 kc and a 1000 kc crystal for communications receiver calibration. A circuit for the calibrator is shown in fig. 1. It is particularly applicable if you hesitate to make power connections, to your receiver, for a conventional vacuum tube calibrator. A collector potential of six volts is supplied by four flashlight batteries which will last for essentially shelf life. A General Electric 2N170 NPN transistor is used as the crystal

oscillator. The resistors are not critical; 20% values should be satisfactory. Any of the following coils can be used for the 5-35 mc. inductor: Meissner rf chokes—19-6891, 19-6892, 19-6889, or any width coil with appropriate inductance range. The 100 kc markers are strong to 18 mc, and the 1000 markers can be heard to 30 mc.

Looking for "high power" transistor transmitters? The circuit shown in fig. 2 will run watts input on the 80 meter band, and was supplied by John W. Hopkin, W1SPU. John reports that he has worked several W6's and V's with this device. The transmitter uses two 2N269 PNP transistors in a novel push-pull circuit. The crystal is connected between bases of the output tank is fed by the collectors. Coil L1 is 30 turns, center-tapped, wound on a 1/2" diameter form. It should resonate at 3.5 mc with the 200 mmfd variable capacitor about half-meshed. The link winding is 4 turns tight

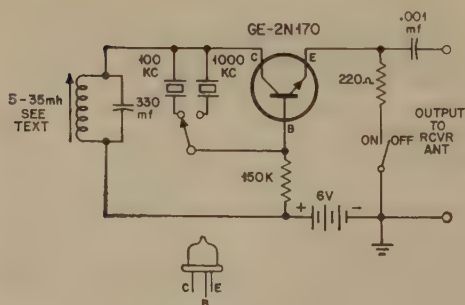


Fig. 1—Circuit for a simple calibrator. Markers up to 30 megacycles can be heard.

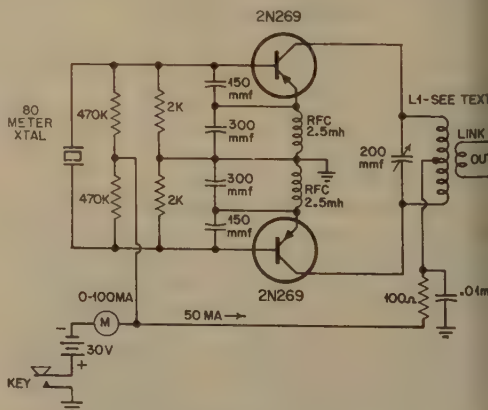


Fig. 2—"High Power" for 80.



ound and coupled at the center of the L1 winding. With a potential of minus 30 volts at the collectors, the transistors should be loaded to about 50 ma., in the bottom of the resonance dip.

From Microtran, 145 E. Mineola Avenue, Valley Stream, N. Y. comes another circuit for DC-DC power converter, and is designed to work with their new line of transformers. The transformer is actually "two-in-one." The winding that couples the collectors to the load is wound on a standard frame, while the feedback winding (between collectors and bases) is a toroid device. This feature is well worth considering when brewing your own DC power inverters. Since the toroid only handles the base current, it can be a very tiny unit, thus lowering the overall cost. So long as the feedback voltage is supplied by a square loop source (such as would occur with a toroid form) the voltage step up transformer can be almost any core unit. But, I digress—for more information on the Microtran DC-DC power converter transformer write to the above address.


### NEW LITERATURE

General Electric Company has prepared data sheets on their new computer line, types N524 through 2N527, and are available by requesting ECG-308 from the Semiconductor Products Department, General Electric Co., Syracuse, N. Y.

Data sheets ECG-309 and ECG-314 describe the new General Electric triode transistors, the 3N36 and 3N37 respectively.

That fascinating device, the unijunction transistor, is described in two new brochures published by GE. One of the brochures contains information on the six types currently available, while the other shows 12 basic circuits for using the unijunction. If interested, write for GP-176, the above address.

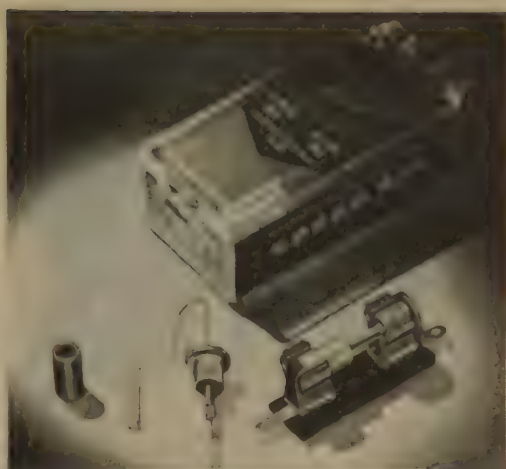Don't miss this one! Motorola, Inc. has published a practical application brochure for their low cost experimenters transistor, the 2N554. The booklet describes amplifiers, power supplies, battery chargers, control units, an



The International Rectifier Corporation SD-500 kit is a truly universal rectifier replacement. It may be wired in place of defective rectifiers, or clipped into holder with the accessory parts supplied.

electric organ, plus a completely transistorized geiger counter. This brochure is available from Motorola distributors only. Los Angeles area—Kierulff Electronics.

CBS-Hytron has announced a new line of PNP transistors in five packages with large signal current gains and high collector-base ratings. Complete data on over 100 EIA types in this broad new line is available by writing the Advertising Dept. Parker Street, Newburyport, Massachusetts, and ask for bulletin E-288.

Information has been released by General Electric on their new silicon controlled rectifiers. The development type ZJ39A is described in bulletin ECG-322 and a reprint on solid state thyatron switches is available in ECG-320.

### TRANSISTOR NEWS

General Electric Company is marketing a new germanium power rectifier, in the 4JA3011 [Continued on page 66]

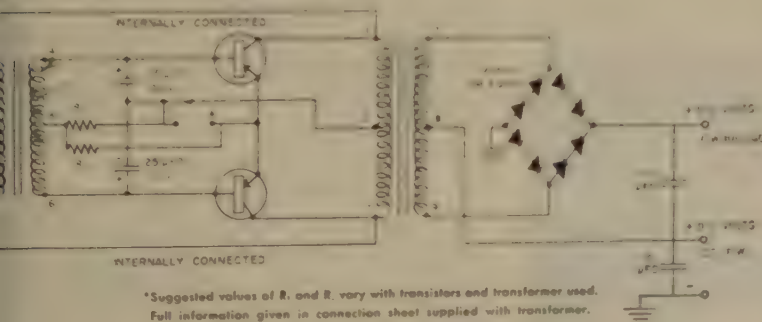


Fig. 3—A typical DC-DC converter using the new Microtran power supply transformer. Full load efficiency may run up to 90% using this transformer and circuit.





# RTTY

Byron H. Kretzman, W2JTP

16 Ridge Dr., High Hills,  
Huntington Station, N. Y.

## Amateur Radioteletype Channels

National, FSK 3620, 7140, 27,200, 29,160, 52,600 kc.  
National AFSK 27.2, 147.96, 144.138 mc.

### Area Nets:

California	147.85	Mc.	AFSK on AM
Chicago, Ill.	147.70	Mc.	AFSK on FM
Detroit, Mich.	147.30	Mc.	AFSK on FM
Washington, D.C.	147.96	Mc.	AFSK on AM
	147.495	Mc.	AFSK on AM
New York City	147.96	Mc.	AFSK on AM
Livingston, N.J.	146.30	Mc.	AFSK on AM
Buffalo/Niagara	147.50	Mc.	AFK on AM
Boston, Mass.	147.96	Mc.	AFSK on AM
Seattle, Wash.	147.00	Mc.	AFSK on AM
Spokane, Wash.	147.15	Mc.	AFSK on AM
Minneapolis, Minn.	144.90	Mc.	AFSK on AM

Clean keying with fsk is something to which most of us haven't paid much attention. As those of you who have worked W2JTP know, an i-f converter is used in conjunction with an SX-101. (CQ, May '58, pg. 61) An ordinary 'scope, connected to look at the 50-kc i.f. is used as a tuning indicator. Initially, the 'scope was adjusted to get a good look at the keying pulses of the fsk signal being received. It soon became obvious which stations were using direct keying (from the keyboard or TD) and which were using polar relays.

Now, the transients observed on those stations using direct keying do not mess up the copy—unless the signal is weak and fading down into the QRN. *That is* when clean keying really makes the difference between copy and no copy.

Sure, it's easier to key the fsk diode directly from the keyboard or TD. That's a good way to get started on RTTY, but as you operate you will soon see the advantages of using a local loop, and clean keying is one of the most important among them.

This month, the tidy tidbit of teleprinter technology is for TD's, especially; however, the basic principles can be applied equally well to a keyboard. It comes from Phil Catona, W2JAV, designer of the very good Terminal Unit that was described in the April '58 issue of CQ.

Fig. 1 is the schematic diagram of Phil's very simple but effective way of operating a polar relay, such as the WE 215A or 255A, from a TD. As you can see, connections are quite simple. Power is supplied from an "isolation" transformer *T* or from a small power transformer such as the Stancor PA8421. If you already have such a supply, just connect the 1500-ohm resistor to one side and ground the other.

Adjustment is extremely simple. At point *X*, in series with one of the relay coils, insert a zero-center milliammeter (50-0-50 ma or 100-0-100 ma) and adjust the 5k pot *R* for equal and opposite currents for mark and space. That's all there is to it. The "reversing switch" is not a necessity, but it is handy if you have two different kinds of diode keyers like the W6AEE and the W6NRM types.

At W2JAV, the polar relay base was removed and the relay was mounted in a plastic box with an octal socket. The whole works was then mounted inside the Model 14 TD; actually on the underside.

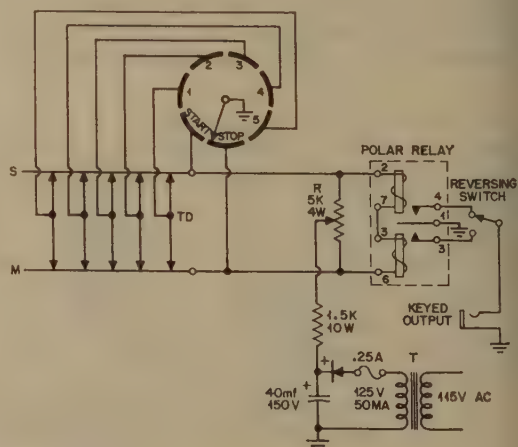


Fig. 1—Schematic Diagram, W2JAV's TD Keyer



## ACROSS THE NATION

Activity in the 1st Call Area is perking up with WINJF in Worcester, Mass., WILFI in West Boylston, Mass., and OBS W1OUG going strong. W1ZXA reports that he will soon be closing down his Rhode Island station for good. (Better get in that QSO for WAS-RTTY!)

W8GWZ in Ann Arbor, Michigan, has written a fine article on TU engineering. Watch for it. W8OKK is now slant-3 in Emporium, Pa., and has built the W2JAV TU from April '58.

K2GQ in East Orange, N. J. (ex-W4VP), has disposed of his Model 26 and now has a new Model 15. W2OKO in Summit, N. J., is setting on 2-meters with the W2JAV Tone Generator from Feb. '58 CQ. (See the Good Brief Dept. pg. 85, Aug. '58 CQ) K2HJC in Morrisville, N.Y., has acquired a Model 15, Kleinschmidt TT-4A, a CV-31C converter, and an 0-5 FR exciter.

W9YBG, Trustee for K9ATE, reports that the Wheaton Academy club is set up with a Model 19, a KWS-1, and a 75A-4. W9LXQ has moved to a new QTH in the Indianapolis area, but will soon have his 32V2, with a pair of 4-400's as a final amplifier, back on with his Model 26 and 75A-4. W9QUN in Milwaukee, Wisconsin, is getting ready for RTTY.

W3ZCS in Pittsburgh, Pa., has built the W2JAV TU, with band-pass filter, and is now building the W2JTP transistorized fork standard (pg. 56 RTTY Handbook) W3CRO is setting up a 60-foot well-guyed tower in spite of difficulty with the "town Fathers." W3PYW has worked VK3KF and W2ZXN/MM several times. Frank has been working hard planning the RTTY program for the ARRL Convention.

The July meeting of the RTTY Society of So. California, Inc., at W6AEE had 78 attending, including 18 XYL's. It started at 3 pm and had talks by W6CMQ on low-noise VHF receiving gear, W6TD on converters, and W6ORS on a miniature exciter.

## SOCIETIES

W9GRW reports the organization of the Chicago Area Teleprinter Society, Inc. (CATS). The first convention will be held in connection with the National Electronics Conference October 12th. Plenty of equipment prizes, including a Model 15 door prize! Contact Ray Morrison at 8029 Keeler Avenue, Skokie, Illinois (ORchard 3-0016) for the details.

## GOOD GRIEF DEPT.

Back in the July '58 RTTY Column, Fig. 1 and Fig. 2, the "Basic Circuits of Old and New Tuning Indicators" are reversed.

On page 84 of the August '58 issue, the caption that was supposed to go with the photograph got lost on the cutting room floor. What it should have said, was:

Left to right, Jack Pitta W6CQK and Byron Kretzman W2JTP visiting the Press Wireless, Inc. transmitting station at Belmont, California. Photo by F. A. Bartlett (Bart, W0OWP) of Prewi.

On page 86 of the same issue, in the diagram of the Zero Bias or Distortion Generator, there should be a jumper between the second and third contacts of the left hand wafer of the function switch in order to apply the 14-volt battery minus in the mark position.

## COMMENTS

A few years ago, your RTTY Editor asked the ARRL how come W1AW didn't put out ARRL Official Bulletins on RTTY as well as on CW. A very nice and detailed reply was received at that time from WIBDI who explained that facilities, manpower, and time just were not available to provide this additional service. A later visit to W1AW confirmed this: only a Model 12 (in the basement) was available, and the regular operators had their hands full preparing Kleinschmidt tapes for the bulletins and the code proficiency program.


Although years have passed and RTTY activity has steadily increased, the situation at W1AW is still pretty much the same. The breach was filled to a considerable extent, up to last year, by WIBDI personally, who painstakingly punched tapes from the Bulletins and transmitted them for the East Coast RT Net.

This year, as most of you know, Boyd (BeeP) Phelps, W0BP, began his famous "Forty RTTY Net" and has since done yeoman service to the RTTY fraternity by transmitting taped bulletins of all kinds. At his conveniently central U.S. location in Minneapolis, BeeP has added another high power transmitter for 15-meters. This fall a fourth transmitter will be added for 6-meters. Simultaneous transmission will be then made on 7140-kc, 21,090-kc, 52.6-Mc, and 144.9-Mc. Roll call starts at 2 pm CST Sundays, and stations not included in the regular roll call are invited to join by answering CQ calls directed to their district. The frequency of listening will also be indicated.

**P.S. Help stamp out Dual Identification!**

(See Comments, p. 86, August 58 CQ)

73, Byron, W2JTP

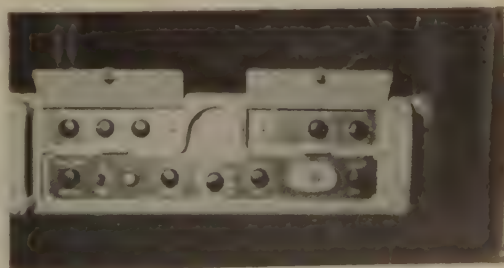

URA/8A Converter used at K2AAA in Bayside, New York. This is a discriminator-audio type of terminal unit.

sideband  
sideband  
sideband

## SIDEBAND

Six hundred enthusiastic operators attended the Single Side-Band Dinner on August 16th, held in Washington during the ARRL's tenth Convention. Side-banders from nearly every State in the Union, and from twenty foreign countries saw General "Butch" Griswold, KØDWC do a splendid job as master of ceremonies. Many door prizes were awarded during the convention to lucky winners. General Curt LeMay, K4RFA, Brig. General Earl Cook, W4FZ and Admiral Virden, on behalf of the Armed Services, praised the accomplishments of the amateur fraternity, and especially pointed out the superiority of SSB in military applications. Vice President Nixon during his speech, referred to the reliability of SSB from his plane while flying through the South American countries recently.

The technical sessions with Sam, W3HN as program chairman were very informative and very well attended. Papers were read by John Hunt of Collins, Stu Seeley, W2ZE of RCA, Wes Schum, W9DYV of Central Electronics, Walt Zarris of Johnson Company, Tom Stewart, WØREP of Hallicrafters, Hank Adams of Eldico, and Jim Noland, WØAWX of WRL Labs.

During the past month six additional "Worked 100 Countries SSB" were awarded to WØQXZ, WØFUH, W8PQQ, ZL3PJ, K2MGE, and W2OQO bringing the membership in this exclusive club to nineteen. Evidently the QSL problem is still very tough. We especially congratulate K2MGE who received number 18 and is the first of the opposite sex to qualify. Considering that she has a husband and four children to look after while chasing DX and QSL cards this is really a remarkable accomplishment.

We hope you were all lucky enough to work the latest DXpeditions including: VQ9GU, Saychelles; FO8AT, Clipperton; YXØAB, Aves Island; HB1TL/FL, Liechtenstein and VP2VB, British Virgin Islands. Your editor is happy to have worked them bringing the total count of countries worked since moving to Silver Spring to 124. Among the leaders in two way SSB DX are: W6UOU, 130, W2JXH, 130; W6ITH, 130, ZL3PJ, 130, VK3AEE, 134, F7AF, 130, TI2HP, 130; K6GMA, 130; W4IYC, 126; and VE3MR, 123. There are probably many others with as many or more worked but these are the only ones which have advised their totals.



John, GC3AAE

Harry, W2JXH gives us the following good news from Rundy, W3ZA/3W: On August 7th the FCC approved the portable operation of W3ZA/3W in the Republic of South Viet-Nam and communication between that station and other amateur stations licensed by the FCC is *not* prohibited. This does not change the status of Viet-Nam with regard to Article 42 Section 1 of the Atlantic City Conference and working stations in Viet-Nam other than W3ZA/3W is still prohibited. Rundy's QSL's are handled by W2JXH. Send a self addressed stamped envelope to Harry at 101 East 72nd Street, New York, N. Y.

Bob, K2ZSQ, is active on six meter SSB with 75 watts. K2IQR and K2ZOB are also on six with side-band. We expect to hear of some excellent results from side-band operation during the next openings.

Joe, 9G1BF whose picture appeared in our last column has returned to Guernsey, on the Channel Islands for a six months' holiday, and will operate as GC2MF.

John, GC3AAE whose photo appears this month reports a very successful DXpedition to the Channel Islands during June, last. Fifteen hundred SSB contacts were made with 112 countries, all on the twenty meter band. QSL's were sent out direct if IRC's were sent to John, otherwise the cards were sent via the bureau. John is looking the map over to select another new country to operate from soon.

W6WFR, Vic sends us the unusual photo of his Volkswagen with a large transformer in



rear. While this is just being transported to home, Vic intends to remove the case and the transformer itself in his new 1KW line for the car installation with his KWM-1 as a ver. Wonder where the passengers will sit? We welcome the following newcomers to B: ZP5KA, MP4BBW, PY4AEK, PY4OD, 7CP, UB5FJ, HI9KR, ZC4DA and 1MB.

Cliff, K9EAB of Peoria, Illinois was stricken with polio in 1949 and as a result is almost completely paralyzed. He must remain in an "iron lung" twenty-two hours each day. His right thumb is the only extremity with useful motion, and with it Cliff has learned to operate key at 25 W.P.M.; some days a little faster. He received his Conditional license in November, 1956, after becoming interested in amateur radio through his cousin, K9CDC, and helped Doc, W2KFR. After a short time on AM and CW, Cliff went on SSB and so far has worked seventy-five countries. His total DX worked on all modes of communication is 161 countries. The photo of Cliff operating from his iron lung shows some of the certificates he has been awarded including: WAC, DXCC, worked SSB, WAVE, WAS, WAA, BERTA, and he is close to WPX. Cliff handles many one patches, keeps regular schedules with many other amateurs including VK4AB. K9EAB and Ramsey of VK4AB have enjoyed 5 consecutive QSOs, and Cliff says Ramsey is his number one "old buddy." Cliff handles VK4AB's W/K QSLs.

Ahmed, HZ1A



A big thrill for Cliff was during a roundtable with OD5BZ, OH0NC, SM5KP, YV5FL and VK4AB and if an African station called in it would have made it WAC on 20 meters. Another highlight of his life was in having Mark of HZ1AB visit with him after Cliff had phoned-patched HZ1AB on several occasions.

Cliff's Dad while not a Ham officially, is the secretary, antenna erector, leg man, band changer, dial tuner and phone patcher. Our hats are off to you Mr. Corne for helping Cliff so thoroughly enjoy side-banding and in setting such a wonderful example to the rest of us. Listen for K9EAB with Cliff's cheerful voice on the mike, it will be a very nice QSO.

73, Bob, W3SW



Cliff, K9EAB

## SEMICONDUCTORS [from page 61]

series. The 3011 A, B, and C have peak inverse ratings of 100, 200 and 300 volts respectively. Full load current is 5 amperes for the A and B, and 2.5 amperes for the C rectifier. Bulletin ECG-321 describes these new units.

A new silicon rectifier all purpose adapter kit is available at International Rectifier Corp. distributors. The SD-500 silicon junction rectifier can operate at 100°C ambient with a resistive, inductive or capacitive load and will supply 130 volts per rectifier at ½ ampere.

An extension of the Pacific Semiconductors "Vericap" line, has been announced, along with price reductions up to 40%. The capacity

class B audio amplifiers. For more information write Lansdale Tube Company, Lansdale,

RCA is in pilot production of two new diode rectifiers and should be in full production the time you read this. The diodes, which will be available from RCA distributors, are rated at 400 and 500 volts, peak inverse, at 500 forward current. I understand the price of the diodes will be very competitive!

Data sheets are now available for the newly redesigned 2N301 and 2N301A. As reported last month, the rating has been stepped up to 5 watts, an increase of more than 85 per cent over the original design. The data sheets for these, and other RCA transistors may be obtained by writing RCA, Semiconductor Division, Somerville, N. J.

The 2N351 and 2N376 are 4 watt power transistors from RCA, and are intended for car radio audio output stages, or push-pull class B modulators or amplifiers. The package is the same as the new 2N301 (see photo).

An extension of the drift transistor family has been announced by RCA. The 2N372 is intended for 455 kc i-f amplifier applications while the 2N374 is designed to be employed in converter service in broadcast band radios. Application data sheets are available for both of the two types and they contain typical circuits.

Sylvania has brought out two new transistors for high speed data processing systems. The 2N576 and 576A are NPN devices with a feature 20 and 30 volt collector ratings, respectively.


Sylvania is also manufacturing drift transistors. In addition to the 2N247, 2N338, 2N371, and 2N372, they have just announced the 2N544. This unit is designed as an rf amplifier at frequencies up to 1.5 mc. It should be noted, however, that the gain is useful even up to 20 mc.

The Sylvania renewal line has been expanded to include 22 power transistors. These include the 2N155, 2N176, 2N234, 2N34B, 2N351, 2N250, 2N255, 2N256, 2N257, 2N283, 2N301, 2N301A, 2N307, 2N307A, 2N351, 2N351, 2N352, 2N353, 2N399, 2N419, and 2N420.


Tung-Sol Electric, Inc., Semiconductor Division, 95 Eighth Avenue, Newark 4, N. J. are introducing a new cold-weld seal process that produces a hermetic, copper-to-copper seal, which makes possible an all copper transistor. This course helps to dissipate the heat generated at the junction. This new process has been incorporated in the Tung-Sol 2N378, 2N378, 2N380, and 2N459. For more information write to Tung-Sol, 200 Bloomfield Avenue, Bloomfield, N. J., Attn.: technical publications dept.

That about saturates our collector for this month fellows, if there is any particular circuit you would like to see, drop a line.

73, Don, W6T

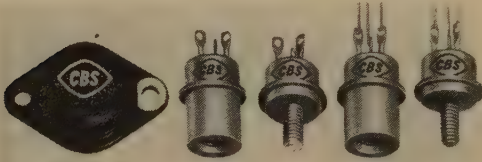

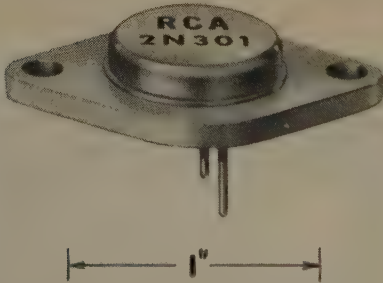CBS-Hytron is now supplying power transistors in these packages. The unit shown at the left is their famous \$1.35 experimenters transistor, the 2N255.



Introducing the new RCA 2N301 transistor. The rating of this device has been stepped up 85%, and it is now rated at 5 watts! Same low price.

ranges from 20 to 100 mmfd and the voltage controlled capacitors have high "Q" factor and are particularly useful in AFC and modulation applications. Curves, ratings, and detailed specifications and application notes are available from Pacific Semiconductors, Inc., Culver City, Calif.

Four new germanium PNP alloy junction transistors, 2N670 through 2N673 have been announced by Philco, and are designed for use in high voltage, high current pulse amplifiers and switching circuits. Typical uses are for magnetic core switching, magnetic drum or tape writing, relay actuating and large signal



by **GEORGE JACOBS, W3ASK**  
607 Beacon Road, Silver Spring, Md.

# PROPAGATION

## CQ DX CONTEST SPECIAL

Propagation conditions during the upcoming DX Contest are expected to be almost as good as last year's record breaking Contest.

Despite the fact that the peak of the present spot cycle has passed, solar activity during October and November, 1958, is expected to pass the level observed during any previous Contest period, except last year's. Because of the correlation that exists between solar and atmospheric behavior, propagation conditions during this year's Contest should be almost as good as last year's, and better than during the Contest previous to 1957. Exceptionally good DX conditions are forecast to all Zones of the world on the 10, 15, and 20-meter bands during the Contest, provided that no sudden radio storms develop.

## CONTEST DATA

The Phone Section of the CQ World wide

DX Contest will be held from 0200 GMT October 25 until 0200 GMT October 27. The CW Section from 0200 GMT November 29 until 0200 GMT December 1. See page 32 of August CQ for complete Contest details.

## FORECAST

For the past eight years CQ has provided a special Propagation analysis for the Contest periods. Previous forecasts have attained exceptionally high accuracy. This year's forecast contains an analysis of more than three hundred paths centered on eight major geographical areas of the United States. There's one almost custom made for your QTH. The analysis is based upon normal propagation conditions. In the event that a radio storm should develop during the Contest, paths passing through or near the auroral zones may become weak, fade considerably, or may blackout entirely. On the other hand, during such storms, conditions on north-south circuits often improve. If a radio

# LAST MINUTE FORECAST FOR OCTOBER

Normal propagation conditions are expected during the CQ World Wide DX Contest period October 25-26th. Radio storms are forecast for October 10-12 and 18-20.

MONTH: OCTOBER, 1958					OCTOBER, 1958				
ALL TIMES IN E. S. T.					ALL TIMES IN C. S. T.				
NORTHEAST USA TO:	10 Meters	15 Meters	20 Meters	40/80* Meters	CENTRAL USA TO:	10 Meters	15 Meters	20 Meters	40/80* Meters
NORTHERN EUROPE	5A-7A (3) 7A-1P (4) 1P-5P (2)	5A-8A (3) 8A-2P (4) 2P-6P (2) 6P-9P (2)	4A-7A (4) 7A-1P (3) 4P-9P (4) 9P-4A (3)	5P-7P (2) 7P-3A (4) 7P-2A (2) *	WESTERN & CENTRAL EUROPE	6A-10A (3) 10A-12N (4) 12N-2P (3) 2P-4P (2) 4P-9P (2)	5A-11A (2) 11A-2P (4) 2P-5P (4) 5P-2A (3) 2A-6A (2)	11A-3P (2) 3P-8P (4) 8P-2A (3) 2A-6A (2)	5P-12M (2) 6P-11P (1) *
CENTRAL & EASTERN EUROPE	6A-8A (2) 8A-1P (3) 1P-3P (2)	5A-8A (2) 8A-2P (4) 2P-5P (2)	3A-6A (3) 6A-12N (1) 12N-3P (2) 3P-7P (4) 7P-3A (2)	5P-8P (2) 8P-1A (3) 8P-12M (1) *	SOUTHERN EUROPE & NORTH AFRICA	6A-8A (3) 8A-1P (3) 1P-3P (2)	5A-8A (3) 8A-2P (4) 2P-5P (2)	12M-3A (2) 3A-6A (3) 6A-4P (1) 4P-8P (4) 8P-12M (3)	5P-2A (3) 6P-1A (2) *
SOUTHERN EUROPE & NORTH AFRICA	5A-7A (3) 7A-2P (4) 2P-5P (3)	5A-8A (3) 8A-1P (2) 1P-7P (4) 7P-10P (2)	8A-1P (1) 1P-10P (4) 10P-6A (2) 6A-8A (3)	5P-7P (2) 7P-3A (4) 7P-2A (2) *	CENTRAL & SOUTH AFRICA	5A-10A (1) 10A-12N (3) 12N-3P (4) 3P-7P (2)	5A-12N (1) 12N-2P (3) 2P-5P (4) 5P-10P (3)	1P-3P (2) 3P-6P (3) 6P-10P (4) 10P-4A (2) 7A-9A (1)	6P-1A (2) 7P-11P (1) *
EASTERN MEDITERRANEAN	5A-7A (2) 7A-10A (3) 10A-4P (2)	5A-7A (2) 7A-11A (1) 11A-7P (3) 7P-9P (2)	3P-5P (1) 5P-7P (4) 7P-11P (3) 11P-4A (2)	7P-1A (2) 8P-12M (1) *	GREENLAND	9A-12N (2) 12N-5P (3)	8A-2P (2) 2P-5P (3) 5P-8P (2)	6A-4P (2) 4P-8P (3) 8P-12M (2) 12M-6A (1)	6P-5A (2) 7P-4A (1) *
CENTRAL & SOUTH AFRICA	6A-11A (2) 11A-4P (4) 4P-7P (3) 7P-9P (1)	5A-8A (2) 8A-11A (1) 11A-1P (2) 1P-6P (3) 6P-9P (3)	1P-3P (2) 3P-10P (4) 10P-5A (3) 5A-8A (2) 8A-7A (3)	6P-12M (2) 8P-11P (1) *	ANTARCTICA	9A-2P (2) 2P-8P (3)	8A-11A (2) 11A-3P (1) 3P-7P (2) 7P-11P (3) 11P-3A (2)	3A-9A (2) 9A-2P (1) 2P-9P (2) 9P-3A (3)	12M-5A (1)
CENTRAL AMERICA	6A-8A (2) 8A-4P (4) 4P-7P (3) 7P-10P (2)	4A-8A (2) 8A-3P (4) 3P-6P (5) 6P-4A (3)	7A-9A (4) 9A-4P (2) 4P-11P (5) 11P-3A (4) 3A-7A (3)	5P-6A (4) 6A-8A (2) 8P-4A (3) *	CENTRAL AMERICA & NORTH AMERICA	6A-8A (3) 8A-4P (4) 4P-8P (3) 8P-10P (2)	5A-8A (3) 8A-5P (4) 5P-10P (3) 10P-5A (2)	1A-6A (3) 6A-9A (4) 9A-5P (3) 5P-10P (4) 10P-1A (4)	7P-5A (4) 5A-7A (2) 8P-4A (3) *
SOUTH AMERICA	5A-2P (3) 2P-5P (4) 5P-10P (2)	6A-10A (3) 10A-3P (2) 2P-7P (4) 7P-3A (2)	3P-6P (2) 6P-1A (5) 1A-3A (3) 3A-8A (2)	6P-5A (3) 8P-2A (2) *	SOUTH AMERICA	6A-8A (2) 8A-4P (4) 4P-8P (3) 8P-10P (2)	5A-9A (3) 9A-2P (2) 2P-6P (4) 6P-2A (3)	12M-5A (3) 5A-8A (4) 8A-5P (1) 5P-12M (4) 12P-2A (4)	8P-4A (3) 9P-3A (2) *
MALAYA & SOUTHEAST ASIA	7A-10A (1) 7A-3P (2)	7A-10A (2) 4P-9P (3)	6A-9A (2) 4P-9P (1) 9P-2A (3)	NIL	HAWAII	10A-12N (3) 12N-8P (4) 8P-10P (2)	9A-4P (2) 4P-8P (4) 8P-11P (3) 11P-2A (2)	2A-5A (3) 5A-8A (2) 8A-5P (1) 5P-7P (2) 7P-2A (4)	11P-7A (4) 12M-6A (3)
AUSTRALASIA	8A-12N (2) 12N-4P (1) 4P-7P (3) 7P-10P (2)	7A-9A (3) 9A-4P (2) 4P-11P (3) 11P-1A (2)	9P-12M (2) 12M-4A (3) 3A-7A (2) 7A-9A (4)	2A-8A (3) 4A-8A (2) *	AUSTRALASIA	8A-11A (2) 11A-3P (1) 3P-6P (2) 6P-10P (3)	7A-10A (3) 10A-4P (2) 4P-10P (3) 10P-2A (2)	4P-8P (1) 8P-11P (2) 11P-3A (4) 3A-9A (3)	2A-7A (3) 3A-6A (2) *
JAPAN AND FAR EAST	4P-8P (2)	3P-5P (2) 5P-9P (3) 9P-11P (2)	4P-9P (2) 9P-2A (3) 2A-8A (2)	12M-5A (1)	JAPAN & FAR EAST	2P-5P (2) 5P-7P (3) 7P-9P (2)	6A-9A (1) 9A-2P (3) 2P-5P (4) 5P-8P (4) 8P-11P (2)	2A-8A (2) 8A-2P (1) 2P-8P (2) 8P-2A (3)	12M-7A (1)
GUAM & PACIFIC	8A-11A (1) 2P-4P (2) 4P-6P (3) 6P-8P (2)	8A-11A (2) 3P-5P (2) 5P-11P (3)	7P-10P (2) 10P-3A (3) 3A-8A (2)	11P-3A (1)	MALAYA & SOUTH EAST ASIA	1P-3P (1) 3P-6P (2)	7A-11A (2) 2P-4P (2) 4P-10P (3)	6A-9A (2) 8P-11P (2) NIL	NIL
OCTOBER, 1958					OCTOBER, 1958				
ALL TIMES IN E. S. T.					ALL TIMES IN C. S. T.				
SOUTHEAST USA TO:	10 Meters	15 Meters	20 Meters	40/80* Meters	NORTH CENTRAL USA TO:	10 Meters	15 Meters	20 Meters	40/80* Meters
EUROPE & NORTH AFRICA	6A-8A (3) 8A-1P (4) 1P-5P (2)	6A-8A (3) 8A-12N (2) 12N-4P (4) 4P-9P (2)	1A-7A (3) 12N-3P (3) 3P-10P (4) 10P-1A (2)	5P-7P (3) 7P-10P (4) 10P-12M (3) 7P-11P (3) *	EUROPE & NORTH AFRICA	7A-10A (2) 10A-12N (3) 12N-2P (2) 2P-4P (1)	7A-11A (1) 11A-1P (2) 1P-4P (2) 4P-8P (1)	1P-3P (1) 3P-6P (3) 6P-11P (1) 11P-3A (2)	5P-11P (1) 6P-11P (1) *
CENTRAL & SOUTH AFRICA	7A-12N (1) 12N-2P (2) 2P-5P (4) 5P-9P (2)	12N-3P (2) 3P-6P (4) 6P-8P (3) 8P-11P (2)	1P-5P (2) 5P-10P (3) 10P-2A (2) 7A-9A (2)	5P-7P (1) 7P-12M (2) 8P-11P (1) *	CENTRAL & SOUTH AFRICA	7A-9A (1) 9A-1P (3) 1P-5P (4) 5P-7P (2)	10A-12N (1) 12N-4P (2) 4P-6P (4) 6P-10P (3)	2P-4P (1) 4P-6P (2) 6P-10P (4) 10P-4A (2)	7P-12M (2) 8P-11P (1) *
AUSTRALASIA	7A-12N (2) 12N-3P (1) 3P-5P (2) 5P-7P (3) 7P-10P (2)	7A-10A (3) 4P-7P (2) 7P-9P (3) 9P-2A (2)	7P-11P (3) 11P-3A (4) 3A-7A (3) 7A-9A (4)	2A-7A (3) 3A-7A (2) *	AUSTRALASIA	7A-9A (1) 1P-3P (1) 3P-7P (3) 7P-10P (2)	7A-9A (2) 9A-2P (1) 2P-6P (2) 6P-9P (3) 9P-2A (2)	6A-6A (3) 6A-6P (1) 6P-11P (2) 11P-3A (4) 3A-7A (2)	12M-7A (3) 1A-6A (2) *
MALAYA & SOUTH EAST ASIA	7A-11A (2) 11A-2P (3) 2P-8P (3)	6A-9A (1) 2P-6P (1) 6P-11P (2)	5P-8P (1) 6A-8A (1)	NIL	MALAYA & SOUTH-EAST ASIA	9A-11A (1) 1P-3P (1) 4P-8P (2)	9A-12N (1) 12N-2P (2) 2P-5P (3) 5P-10P (3)	6A-9A (2) 2P-6P (1) 6P-10P (2)	NIL
FAR EAST	4P-6P (3) 6P-9P (2)	3P-6P (2) 6P-9P (3) 9P-2A (2) 6A-9A (2)	9P-6A (2) 6A-8A (3)	NIL	FAR EAST	2P-4P (2) 4P-8P (3) 6P-8P (2)	2P-6P (2) 6P-9P (3) 8P-11P (2)	1A-6A (1) 6A-9A (2) 2P-7P (1) 7P-10P (2) 10P-1A (3)	2A-7A (2) 4A-6A (1) *
SOUTH AMERICA	7A-3P (3) 3P-6P (4) 6P-10P (3)	6A-9A (3) 9A-3P (2) 3P-9P (4) 9P-3A (3)	6A-8A (3) 8A-3P (2) 3P-5P (3) 5P-4A (4) 4A-6A (2)	6P-5A (4) 5A-8A (2) 7P-4A (3) *	SOUTH AMERICA	7A-9A (2) 9A-2P (3) 2P-6P (4) 6P-10P (2)	7A-9A (3) 9A-1P (2) 1P-5P (4) 5P-9P (4) 9P-2A (2)	2P-4P (2) 4P-6P (3) 6P-9A (2) 2A-8A (3) 8A-2P (1)	6P-4A (3) 8P-2A (2) *
ANTARCTICA	2P-4P (2) 4P-6P (3) 6P-9P (2)	5P-7P (2) 7P-12M (3) 12M-3A (2)	7P-10P (2) 10P-6A (3) 6A-8A (2)	2A-6A (2)					



OCTOBER 1958  
 ALL TIMES IN P.S.T.

	10 Meters	15 Meters	20 Meters	40/80 Meters
<b>EUROPE &amp; NORTH AFRICA</b>	6A-6A (2) 6A-1A (2) 12N-2P (2) 2P-6P (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *
<b>CENTRAL &amp; SOUTH AFRICA</b>	7A-12M (2) 12M-1P (2) 2P-5P (2) 5P-7P (2)	12N-3P (2) 3P-5P (2) 5P-7P (2) 7P-6P (2)	2P-5P (2) 5P-7P (2) 7P-6P (2) 1A-6A (2)	7P-12M (2) 12M-1P (2) 1P-6P (2) 6P-12M (2) *
<b>ASIA &amp; PACIFIC ISLANDS</b>	7A-6A (2) 6A-1A (2) 12N-2P (2) 2P-6P (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *
<b>SOUTH AMERICA</b>	6A-12N (2) 12N-4P (2) 4P-6P (2) 6P-12M (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *

OCTOBER 1958  
 ALL TIMES IN P.S.T.

	10 Meters	15 Meters	20 Meters	40/80 Meters
<b>EUROPE &amp; NORTH AFRICA</b>	6A-6A (2) 6A-1A (2) 12N-2P (2) 2P-6P (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *
<b>CENTRAL &amp; SOUTH AFRICA</b>	7A-12M (2) 12M-1P (2) 2P-5P (2) 5P-7P (2)	12N-3P (2) 3P-5P (2) 5P-7P (2) 7P-6P (2)	2P-5P (2) 5P-7P (2) 7P-6P (2) 1A-6A (2)	7P-12M (2) 12M-1P (2) 1P-6P (2) 6P-12M (2) *
<b>ASIA &amp; PACIFIC ISLANDS</b>	7A-6A (2) 6A-1A (2) 12N-2P (2) 2P-6P (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *
<b>SOUTH AMERICA</b>	6A-12N (2) 12N-4P (2) 4P-6P (2) 6P-12M (2)	6A-10A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7A-1A (2) 1A-2P (2) 2P-1P (2) 4P-6P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2) 1A-6A (2) *

OCTOBER 1958  
 ALL TIMES IN P.S.T.

	10 Meters	15 Meters	20 Meters	40/80 Meters
<b>EUROPE &amp; NORTH AFRICA</b>	7A-9A (2) 9A-12N (2) 12N-2P (2)	9A-10A (2) 10A-2P (2) 2P-4P (2)	7A-11A (2) 11A-2P (2) 2P-8P (2)	7P-11P (2) 11P-12M (2) 12M-1A (2)
<b>CENTRAL &amp; SOUTH AFRICA</b>	8A-6A (1) 6A-12N (2) 12N-3P (2) 3P-10P (2)	6A-11A (1) 11A-2P (2) 2P-6P (2) 6P-11P (2)	12N-4P (2) 4P-8P (2) 8P-12M (2) 12M-1A (2)	6P-10P (2) 10P-12M (2) 12M-1A (2) 1A-6A (2) *
<b>SOUTH AMERICA</b>	8A-12N (2) 12N-4P (2) 4P-6P (2) 6P-12M (2)	8A-10A (2) 10A-2P (2) 2P-6P (2) 6P-12M (2)	9A-1A (2) 1A-2P (2) 2P-8P (2) 8P-12M (2)	9P-3A (2) 3A-1P (2) 1P-6A (2) 6A-12M (2)
<b>GUAM &amp; PACIFIC ISLANDS</b>	11A-1P (2) 1P-7P (2)	10P-7A (2) 7A-9A (2)	4A-7A (2) 7A-9A (2)	11P-7A (2) 7A-12M (2) *

OCTOBER 1958  
 ALL TIMES IN P.S.T.

	10 Meters	15 Meters	20 Meters	40/80 Meters
<b>AMSTERDAM</b>	7A-10A (1) 10A-12A (2) 12A-2P (2) 2P-6P (4) 6P-12M (2)	7A-1P (3) 1P-3P (1) 3P-7P (2) 7P-11P (4) 11P-3A (2)	4A-7A (1) 7A-6A (1) 6A-11A (1) 11P-1P (2) 1P-6A (4)	12M-7A (2) 7A-6A (2) 6A-1A (2) 1A-6A (2) *
<b>JAPAN, OKINAWA &amp; FAR EAST</b>	12N-2P (3) 2P-7P (4) 7P-9P (2)	12M-8A (2) 8A-11P (1) 11A-1P (2)	6A-11A (2) 11A-1P (1) 1P-10P (2)	10P-8A (2) 8A-1A (2) 1A-6A (2) *
<b>PHILIPPINE IS. &amp; EAST INDIES</b>	8A-11A (2) 11A-2P (2) 2P-10P (1)	8A-10A (4) 10A-2P (2) 2P-4P (1) 4P-10P (2) 10P-4A (2)	8A-6A (2) 6A-6A (2) 6A-11A (1) 11A-10A (2) 10P-4A (2)	2A-6A (2)
<b>MALAYA &amp; SOUTH EAST ASIA</b>	8A-11A (2) 11A-2P (2)	8A-12N (2) 12P-10P (2)	1A-7A (2) 7A-12N (2)	4A-6A (1)
<b>HONG KONG, MACAO &amp; FORMOSA</b>	1P-3P (3) 3P-7P (4) 7P-9P (2)	7A-10A (1) 10P-6P (2) 6P-12M (3) 12M-2A (2)	4A-7A (2) 7A-11A (2) 11P-10P (2) 10P-4A (2)	1A-4A (2) 4A-1A (2) *
<b>ALFUTIAN IS.</b>	10A-12M (2) 12N-6P (4) 6P-8P (3)	8A-11A (2) 11A-7P (4) 7P-8P (2) 8P-12M (2)	11A-6P (2) 6P-10P (4) 10P-4A (1) 4A-11A (1)	8P-6A (3) 6P-5A (2) *
<b>GUINIA</b>	1P-3P (3) 3P-6P (4) 6P-8P (2)	8A-6P (2) 6P-10P (4) 10P-12M (2)	6P-9P (2) 9P-12M (4) 12M-4A (2)	10P-6A (3) 11P-5A (2) *

OCTOBER 1958  
 ALL TIMES IN P.S.T.

	10 Meters	15 Meters	20 Meters	40/80 Meters
<b>NORTHWEST USA TO:</b>				
<b>EUROPE &amp; NORTH AFRICA</b>	8A-11A (2) 11A-1P (1)	6A-10A (1) 10A-2P (2) 2P-5P (1)	10A-2P (2) 2P-10P (4) 10P-12M (1)	6P-8P (1) 8P-5A (2)
<b>CENTRAL &amp; SOUTH AFRICA</b>	8A-11A (1) 11A-1P (2) 1P-6P (2)	1P-3P (1) 3P-9P (2) 9P-12M (1)	1P-4P (1) 4P-8P (1) 8P-12M (1)	5P-9P (1)
<b>AMSTERDAM</b>	11A-2P (3) 2P-5P (2) 5P-7P (4) 7P-10P (2)	6A-9A (3) 9A-2P (2) 2P-7P (1) 7P-10P (2)	8A-12N (2) 12P-8P (2) 8P-10P (4) 10P-6A (2)	8P-7A (3) 7A-6A (2) 6A-6A (2) *
<b>MALAYA &amp; SOUTH EAST ASIA</b>	8A-4P (2) 4P-6P (2) 6P-8P (2)	7A-9A (2) 9A-3P (2) 3P-8P (2)	7A-8A (2) 8A-5P (1) 5P-11P (2)	2A-6A (2) 4A-6A (1) *
<b>FAR EAST</b>	12N-2P (2) 2P-5P (4) 5P-8P (3)	6A-9A (1) 12N-4P (3) 4P-7P (4) 7P-12M (2)	6A-8A (3) 8A-1P (2) 1P-5P (1) 5P-10P (3) 10P-6A (2)	11P-6A (4) 6A-1P (2) 12M-6A (2) *
<b>SOUTH AMERICA</b>	8A-7A (2) 7A-1P (3) 1P-6P (4) 6P-12M (2)	6A-8A (3) 8A-11A (2) 11A-4P (3) 4P-8P (4)	12M-7A (2) 7A-3P (2) 3P-6P (3) 6P-12M (4)	6P-3A (3) 7P-2A (2) *

SYMBOLS INDICATING NUMBER OF DAYS CIRCUIT IS FORECAST TO OPEN  
 PERIOD MONTH

- (1) 1-4 days (2) 5-11 days (3) 12-18 days (4) 19-26 days (5) over 26 days
- \* Indication time of possible eighty-meter openings.
- The 80-meter band is likely to open approximately 10% of the nights on those circuits for which 80-meter openings are shown with a symbol of (3) or better.
- 80-meter openings are likely to occur on approximately 10% of the days on those circuits for which 10-meter openings are shown with a symbol of (4) or better.
- The CQ DX Contest Special Propagation Charts are based upon a double-sided A.M. radiated power of 500 watts at radiation angles less than 15 degrees. For each 6 DB difference in radiated power, adjust the symbol shown by 1. These forecasts are calculated from basic radio propagation data published by the Central Radio Propagation Laboratory of the National Bureau of Standards, and are valid through November 15, 1958.

storm should develop during the Contest period concentrate on working east-west paths during the daylight hours, and north-south paths during the morning and evening hours. The east-west paths appearing in the Propagation Charts with a rating of (3) or higher are expected to hold up during all but the most severe type radio storm. A "last minute forecast" for the Phone Section, made at press time, appears elsewhere in this column. Up to the minute propagation forecasts during the Contest period can be obtained from WWV on 2.5, 5, 10, 15, 20 and 25 mcs, at 19½ and 49½ minutes past each hour. WWV forecasts are intended primarily for north-Atlantic circuits, with a similar forecast for north-Pacific circuits broadcast from WWVH, Hawaii, on 5, 10 and 15 mcs at 9 and 39 minutes past each hour. These forecasts consist of a letter-number combination transmitted in slow Morse Code. The letter "N" indicates conditions at the time of broadcast are normal; the letter "U" that conditions are presently unsettled or erratic, and the letter "W" that conditions are disturbed and a radio storm is in progress. The number indicates the average quality of propagation conditions forecast for the next few hours as follows:

- |                |                |
|----------------|----------------|
| 1—useless      | 6—fair to good |
| 2—very poor    | 7—good         |
| 3—poor         | 8—very good    |
| 4—poor to fair | 9—excellent    |
| 5—fair         |                |

This year CQ begins a *new* Contest propagation service for its readers. Five days before each Contest period (Phone and CW) CQ will prepare a special forecast, based upon all the latest ionospheric data, for each six hour period of the Contest. Copies of these forecasts will be available from the Propagation Editor, 607 Beacon Road, Silver Spring, Md. for a self-addressed stamped envelope.

## SIX METERS

Although the six-meter band is not included in the Contest, a few DX openings are likely to occur during October, becoming more numerous later during the winter months. In conditions to South America, Europe and Africa should peak around noontime, with a band opening towards the west later during the afternoon.

## SUNSPOT CYCLE

The monthly sunspot number reported for July, 1958 was 198. This results in a smoothed sunspot number of 198 centered on January, 1958. The smoothed sunspot number forecast for October, 1958 is 155.

## SOLAR ECLIPSE

On October 12, 1958 a total eclipse of the sun is expected to occur. The eclipse will be visible along a path extending from the South Pacific islands off the east coast of Australia eastward across the Pacific to Chile and Argentina. It will not be visible in the northern hemisphere. A total eclipse is of great importance to radio propagation research since during such an event the sun's radiations are cut off from reaching the earth, and theoretically the ionosphere should become very weak. Measurements made during previous total eclipses have substantiated this fadeout in the ionosphere. Shortwave radio signals being reflected from the ionosphere along the path of the eclipse on October 12, can be expected to be subject to weak signal strength and rapid fading.

Next month's column will contain an analysis for the CW Period of the CQ World-Wide DX Contest. Good Luck.

73, George, W3A

Hmmm—I thought so . . . . .





by **DON CHESSER, W4KVX**  
R.F.D. 1, Burlington, Ky.

# DX DX DX DX DX DX DX DX

## WAZ

744	G110R	Patrick J. A. Gowan	(19th GB)	762	W9KXX	Paul Niles	(40th W9)
745	G1AJP	John D. Baker	(41st GB)	763	KGAYA	Ronald B. Patterson	(100th K6)
746	W1BRV	Frank J. Albert Jr.	(40th W1)	764	W0AJU	M. G. Bulluck	(28th W0)
747	W1BJ	Raymond Farwell	(24th W1)	765	JA4BP	Seimi Hamada	(1st JA3)
748	O1IRE	Ort Emmersbach Rath	(10th O1)	766	HBNET	Kurt Ruesch	(16th HB)
749	W0BWS	Donna W. Egan	(33rd W0)	767	DL7CS	Bruno Stangnowski	(5th DL7)
750	J4W4D	Wimco Tawazeti	(2nd J4)	768	W9HCR	Elmer C. Zindars	(41st W9)
751	W4AAU	M. Chason Spang	(25th W4)	769	DL3BJ	Josef Kruse	(8th DL3)
752	W1NCF	M. S. Hunter	(37th W1)	770	G3GFG	D. R. Payne	(15th G3)
753	ZN0U	Jane P. Bowman	(2nd ZN)	771	SP7HX	Roman Izykowski	(1st SP)
754	G4XU	P. B. Briscoombe	(8th G4)	772	W3JZY	Andrew H. Abraham	(38th W3)
755	W1BTL	Eugene B. Pettit	(1st W1)	773	W9YOR	Donald Novak	(42nd W9)
756	W4NPD	Ernest L. Stevens Jr.	(10th W4)	774	PA0FX	H. VanBreen	(3rd PA0)
757	UB1KAB	Les P. Yarnes	(1st UB)	775	ZL1AH	J. D. Wightman	(9th ZL)
758	VE1KE	Victor Williams	(15th VE)	776	ZL2HP	T. J. Kendrick	(5th ZL2)
759	W4NUJ	Ear Stiffell	(168th W4)	777	ZL4BO	V. R. Jackson	(1st ZL4)
760	W1ZW	P. K. Baldwin	(20th W1)	778	W2BYP	George A. Mack	(50th W2)
761	W2QJM	Frank N. Kryos	(49th W2)	779	W3AYS	C. Gayard Smack Jr.	(39th W3)
				780	VK3CX	Alan G. Brown	(7th VK3)

Congratulations are due the above successful winners of CW/Phone WAZ awards. The shorter list than usual represents stabilization of WAZ processing, which is now current. All applications are now being processed immediately on receipt.

But this editor is now being bombarded with cries of "Where's my WAZ certificate?" Investigation by Wayne uncovered a huge stack of them under a mailing table in CQ's New York office. A new mail clerk promises faster service, but even so the two-weeks' interim for reparing the certificates has proved unrealistically optimistic. Please amend that to a month, and please be patient!

The following leather-lunged DXers have made WAZ the hard way—All Phone! Only two made it with JT1AA phone QSL's. The others have had zone #23 confirmed for years, but have hung up on the Russian zones, especially #19, which have proved nearly as difficult to confirm as #23. Congratulations, fellows!

### All Phone WAZ

13	OK1MB	Beda K. Micka	1st OK
14	CX2C0	Richard Sierra	1st C0
15	W6GVM	Emil F. Malek	3rd W6
16	W9NDA	Paul L. Edwards	1st W9
17	F8DC	Tony Pettitjean	1st F

718	9K1AZ	Wm. N. Burgess	1st 9K2
719	W0KBU	Buster Parker	1st W5

## WPX

At long last we're happy to start the WPX rat race, to publish the first box scores, and to announce we're also current with WPX processing. A list of all WPX certificates issued to date follows:

### CW WPX

1	W6KG	Lloyd Colvin	1st CW
2	W2HMI	Aug. Nickol (350)	1st W2
3	W1BFT	Carl B. Evans	1st W1
4	W3KX	Vincent L. Russo	1st W3
5	W3AFK	A. R. L. Marsh	2nd W5
6	SM5AHK	Curt R. E. Israelsson	1st SM
7	W9IU	Leslie D. Gregg	1st W9
8	W0KPL	W. W. Simpson	1st W0
9	LUSAQ	Antonio Navatta	1st LU
10	W4BPW	C. W. Timley	2nd W4
11	W2DGW	John Lubinski	2nd W2
12	OK1MB	Beda K. Micka	1st OK

### Phone WPX

1	W8WT	Lester A. Jeffery	1st Ph
2	G3D0	D. A. G. Edwards	2nd Ph

### SSB WPX

1	T12HP	Humberto Perez	1st SB
---	-------	----------------	--------

### 14 MC CW Sticker

W9IU	Leslie D. Gregg	811
------	-----------------	-----

Congratulations!  
The difficultness and scope of the WPX

award, incidentally, became apparent while checking the cards for these first awards. Every application above included complete sets of confirmations for dozens of other awards throughout the world, such as WAC, DXCC, WAA, WASM, even WAZ, and all since January 1, 1957! It would appear, at this first review, that WPX will prove all-encompassing. If you can qualify for WPX your ability to qualify for many other awards will be a foregone conclusion.

You are reminded that WPX is now being handled entirely by the DX department of CQ, and all inquiries, applications, and cards should be addressed to the DX Editor, address at the head of this column. Cards may be submitted in any quantities, and will be checked, accredited, and returned immediately. Please enclose sufficient postage for their return. A charge of \$1 in currency or IRC's is made for the WPX certificate, which will be issued and mailed from CQ's New York office, as with WAZ.

Following are a few notations made during processing of the first WPX cards: Only legitimate prefixes, as authorized by the governments concerned, may be counted. HB1TL/AR or HB1TL/FL count only as HB1, even though the latter is Liechtenstein. Those suffixes are used to indicate geographical locations, such as Swiss cantons. HE is the official Liechtenstein prefix. Likewise, VK2AYY/LH counts as VK2. The suffix /P indicates portable operation in many countries, but cannot be considered different from the prefix appearing at the beginning of the call unless another prefix is included, such as SM8AQT/LA/P, in which case it would be counted as LA8. In cases where no numeral occurs in the suf-


fix, the numeral appearing in the call's prefix will be used. Thus DL4GH/TA would count as TA4, and VE3BQR/SU as SU3. If no numeral appears in the prefix, use Ø. Thus RAEM counts as RAØ, and WAR counts as WAØ. To avoid confusion and unnecessary correspondence, no exceptions will be made in the few instances where the same prefix assigned two or more countries, such as KC4/Navassa and KC4/Antarctic. It is believed these instances are too few to make a difference in the over-all picture. Finally, the QSL cards must exclusively tell the story. No certified logs or affidavits, please. We have only a tiny staff to administer both WAZ and WPX, and we must keep correspondence over incorrect cards at a minimum. Thanks very much for your co-operation.

## DX NEWS

(All times noted are GMT)

Zone #2 leads off our DX roundup this month. If you need it for WAZ, a good bet is VE8PB, located on Ellef Ringnes Island (78°N, 103°W). He's quite active, and he QSL's via his Call Book QTH. The annual rash of vacationing DXers to FP8, zone #4, seems to have reached a climax, with Guy Roblot, FP8AP, doing a stunning job as St. Pierre's one-man chamber of commerce and welcoming committee. He has done a magnificent job of making the W's visits pleasant and enjoyable, and cutting red tape in local officialdom. Some W's have reported having their FP8 calls within two hours of landing on the island. These include FP8AB (QSL K2JGG), FP8AR (QSL to W2HTI), FP8A (W2EQS), FP8AT and FP8AU (K2GMV).

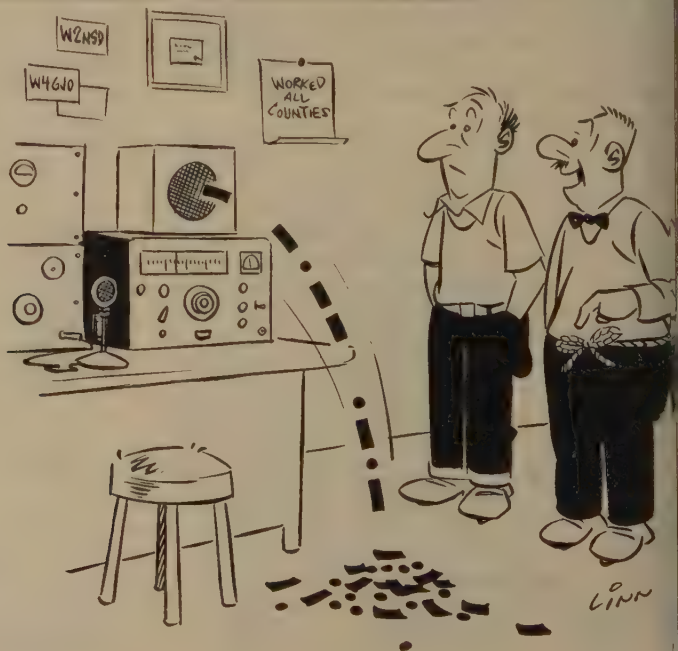"Sure puts out a solid signal, doesn't it?"





8AV (W3MYL), FP8AO (W2ORA),  
8AX (VO1BF), FP8AY (VO1BD), FP8AZ  
21AD), and FP8BA (K2YLD).

But the big DXpedition of the month was that of FO8AT, Clipperton Island, zone 27, sponsored by the San Diego DX Club, this expedition was another of those last minute shuffling affairs, with the official permission and license arriving from Tahiti only hours from ship sailing time. The usual frantic rush and confusion ensued, complicated by the inability of Bob, W6ZVQ, scheduled to make the trip, to get away from his work. Doug, K6RNM, was thrown into the breach at the last minute. Further complications arose in the failure of a new KWM-1, loaned by Collins for the purpose, to arrive in time for the sailing. A substitute KWM-1 was flown down by Jerry Tasto, a bank representative of Collins, which arrived in the nick of time. Other equipment included a Viking II, a 2-element tri-bander beam and a vertical antenna by Hy-Gain, and a 750 watt gasoline generator.

Previous arrangements had been made with Scripps Institution of Oceanography, whose sponsorship, the "Spencer F. Baird," makes regular trips to Clipperton waters for IGY studies, to include one radio amateur and his equipment on this trip. With the help of the San Diego DXers, Doug and his gear were tossed aboard in time for the ship sailing, August 1. They arrived Clipperton six days later and a successful and easy landing was made in the lee of the abandoned LST by Doug plus eleven men and one woman, put ashore to perform IGY studies. Soon after reaching shore, rains and extremely high winds arose, making immediate operation impossible. He finally got on the air the evening of August 8, resulting in one of the most massive pile-ups ever heard on 14 mc CW, later duplicated on 14305 kc SSB, and continuing at this writing. For some unexplained reason, the Clipperton party and itself with a shortage of gasoline for the AC generators, limiting FO8AT activities to about 5 hours a day, thus creating the continuous pile-ups. This, plus the unfortunate lack of a DX adaptor for his KWM-1, making it necessary for Doug to reset his VFO each transmission, have resulted in some criticism from DXers, most of whom have no inkling of the pressures and difficulties under which most DXpeditions are made. We can be sure Doug is doing his best under the circumstances.

FO8AT is scheduled to QRT August 24th and return to San Diego by air from Panama. Costs of this DXpedition are being underwritten by the San Diego DX Club, which hopes to recover some of the expenses by small donations from appreciative DXers. This is no "ollar a QSL" operation, and all cards will be answered, regardless. Send your QSL's and monetary thanks to George Keeler, W6KSM, 38 Rolando Knolls Drive, La Mesa, Calif.,

the FO8AT QSL manager. Cards are promised to be prompt and 100%.

If this DXpedition proves successful, financially, the San Diego DX Club hopes to come up with another, possibly to Socorro, XE4, and possibly in time for the CQ World-Wide DX Contest, CW weekend. We hope to have more about this next month. Other zone 27 doings: YS1MS, 14309 kc SSB, 1400GMT; YS1TT, 21410 kc SBB, 1900; YN1AA, 14009 kc CW, 0300; YS1IM, 14036 kc CW, 0530.

Another attempt at Navassa Island, KC4, zone 28, is planned this fall by HI7LS, presently on temporary assignment on Eleuthera, Bahama Islands, reports Andy, W4IYT. Using Coast Guard transportation (which will limit operation to one day), HI7LS, in company possibly with VP7BH and a third operator from Grand Turk, hopes to climb the cliff with DX-100, Viking II, a SSB rig, SX-100, HRO-7, and 2 kw power plant! John Beck, ex-W6MHB, TI9MHB, etc., operating as VP7BT, Eleuthera, has racked up 90 countries in the first 5 weeks of operation. Reg, W6ITH, now back at FS7RT, has cancelled or indefinitely postponed his Anguilla, VP0RT, trip, and so has Danny, VP2VB. The entire island of Anguilla is under smallpox quarantine, reports Larry, W5HJA, and no one is permitted in or out for the next month or two. Danny plans to continue his VP2 sweep with St. Kitts, starting about August 15th. Look for him on his usual freqs of 14075 kc CW, 14195 kc AM, and 14310 kc SSB. Some unhappy joker has been creating false pile-ups by signing VP0AA, first telling his QSO's to QSL via VP0AB (there's no such QTH), later telling them to QSL via W4KVVX. Sorry, fellows—you worked another weirdy! Fred, ex-VP2LU, is now on Grand Turk, awaiting a VP5 call, reports John, W2DGW. His VP2 call expired last January and the authorities would not renew it. If no VP5 call is forthcoming, he will operate VP5FH, and promises to cover all bands this fall and winter, including 160 meters (W1BB, perk up!). Other zone 28 activities: VP21B, 21248 kc AM, 1900; VP2GV, 21200 kc AM, 2300; VP2LO, 14057 kc CW, 0300; PJ2ME, 14058 kc CW, 0000; FG7XF, 14043 kc CW, 0000; VP2DA, 21200 kc AM, 0030; HI8GA, 21243 kc AM, 2000.

Belated word has reached us of an impending DXpedition to Galapagos, HC8, zone 10, by Ron, W0AGO as HC8AGO; Paul, W0LUX, as HC8LUX; and Vic, W0WGF, as HC8WGF, starting about September 19th and continuing for two to four weeks. Arranged in co-operation with the Quito Radio Club of Ecuador, of which two to four Quito members may also accompany the DXpedition as operators and interpreters, the foray promises to be big-time, with around-the-clock operation on SSB, AM, and CW, the emphasis being on SSB. Equipment includes HT-32, SX-

101, KWM-1, tri-band beam, trap vertical, two generators, and assorted movie and still cameras. Operations will probably be confined to the 10, 15, and 20 meter bands, with daily skeds with Quito on 40. Cards should go to the home calls of the individual operators, complete with stamped and addressed return envelopes. Small donations to help with expenses would be most welcome. The operators point out that they are not speed artists, and will avoid pile-ups as much as possible (!). If things get too rough they might shut down, for they have 62 islands they want to visit and photograph. They ask help by not interfering with their skeds with home, for they'll be away two months, and they want to keep in touch with their families.

Trinidad Island, PYØ, zone #11, attains new country status December first, writes W1WPO in a letter to PY1CK, with credits OK back to 1945. Jami, PY2CK, says he, PY1CK, PY1HQ, and PY7AN, are still planning a Trinidad operation, as PYØNA and PYØNB, on CW, AM, and SSB, using Apache and DX-100, for a week or ten days, during late October or early November, depending on when the Brazilian Navy has a ship going there. Other zone #11 activities this past month: ZP5LS, 14033 kc CW, 2230; ZP5MQ, 21240 kc AM, 0045.

G3ZY just completed a successful DXpedition holiday to Monaco, zone #14, operating as 3A2CF on 7, 14, and 21 mc from August 4th to 17th. QSL's should go to his home QTH. He reports that QSO's with a 3A2CF prior to those dates are worthless. It is possible that ARRL may soon recognize the United Nations extraterritorial ground at Geneva, Switzerland, prefix 4UZ, with DXCC separate country status, similar to Jerusalem, ZC6UNJ, writes Jean, HB9J. He, as Swiss delegate, and HB9SI, chief communications operator of the United Nations Radio, Geneva, discussed the matter with Budlong, W1BUD, at the IARU Region I convention in Godesberg, Germany. Bud seemed agreeable to the idea, Jean reports. HB9SI is now in operation from this possible new country, only 2 miles long, with 500 watts and excellent equipment, using the call 4UZA. Don't pass him up! OY7ML is on 14020 kc CW each Saturday and Sunday at 2300 looking for DX who still need that rare country. He is also active most days from 0730 to 0830, same frequency. Also, from zone #14: PI1BV, 14062 kc CW, 0400 (FB WPX!); SM1BVQ, 14040 kc CW, 0200; HB1TL/FL, 14310 kc SSB, 0400.

Still another DXpedition, this one promising to be the biggest and most awesome of them all, covering several continents and 5 years of travel, starting from Czechoslovakia, zone #15, this November and returning to the starting post in 1963, is described by Beda, OK1MB. OK2HZ and OK2ZH, well-known explorers and expeditionists, who made tours of Africa

and South America shortly after World War II will follow approximately this itinerary: Czechoslovakia, Roumania, Bulgaria, Greece, Turkey, Lebanon, Jordan, Egypt, Saudi Arabia, Yemen, back to Saudi Arabia, Kuwait, Iran, Persia, Afghanistan, Pakistan, India, Sikkim, Nepal, Ceylon, back to India, Burma, Thailand, Malaya, Java, Sumatra, Borneo, Celebes, Australia, Tasmania, New Zealand, New Guinea, many different islands in Polynesia, Philippines, China, Tibet, Mongolia, back to China, Korea, Japan, and back to Poland at home.

Equipment for the expedition will be two 8-cylinder trucks, equipped with photolathes, an inter-truck 30-watt radio crystal control in the 25-26 mc region, and two KWM-1 transceivers, purchased by OK1MB from TI Henry, W6UOU, for the purpose of keeping in touch with home, and for amateur radio. The KWM-1 units will be set-up at OK1MB and OK2HZ, in Gottwaldov/Zlin, for several weeks prior to departure of the expedition, resulting in the first SSB operation from the country.

OK1MB will act as QSL manager for the tour. Calls anticipated will be OK7HZ plus the /suffix (prefix) of the country visited, such as OK7ZH/AC4 and OK7ZH/JT1. Further details will be presented. Other zone #11 notables this month: UP2KBC, 14040 kc CW, 0200; UP2NM, 14065 kc CW, 0300; UR2KAE, 14074 kc CW, 0345; UQ2A, 14011 kc CW, 0300; HV1CN, 14105 kc AM, 2300.

The Maldive Islands, zone #22, operation continue with VS9MA as mainstay, shortly to be joined by VS9FUB (G3FUB) and VS9M. AP2U reports via the WGDXC Bulletin that amateur radio in Pakistan is now forbidden. There is no reason given; duration indefinite. 4S7PJ says the same goes for Ceylon. A state of emergency has been declared, and all 4S7's have been ordered to turn in their transmitters to the nearest police station. Other zone #22 activities: VU2SS, 21118 kc AM, 1730; VU2RM, 14322 kc SSB, 1130; VU2RA, 14011 kc CW, 0400; VU2AJ, 14020 kc CW, 1000.

Through a remarkable interpretation of the rules, the FCC has given Rudy, now signing W3ZA/3W, zone #26 the green light to legal work W's, so long as his call is thus sanctioned by Viet Nam authorities. Presumably, however, it is still illegal for us to work Viet Nam using such calls as 3W8AA or XV5A. Presuming even further, this may pave the way to the legal operation of Americans in other banned countries, such as 4W, EP/EQ, and PI if those prefixes are attached as suffixes to a call, and, of course, if such operation is permitted by the subject countries. It's a very interesting development! At this writing VS1B and party are still awaiting permission from the Indian government for their Nicobar and Andaman Island trek. Also from zone #26: XZ2TI



14014 kc CW, 1600; XW8AI, 14022 kc CW, 030; HS1C, 14023 kc CW, 1130.

VK9LE, Cocos-Keeling, zone #29, is now working 21220 kc AM most days around 1500, reports G3AAM. Other zone #29: ZC3AC, 14024 kc CW, 1300.

Alan, VK2AIR, recently returned from his K2AYY/LH, Lord Howe, zone #30, DXpedition, reports his exciting two-weeks trip a success after working 1911 contacts, 1428 of them W's. He worked 43 countries, made WAC in 10 minutes, and at his best pace knocked off 70 per hour (wowee!). Jack, W6NTR, heard in work W1ELR, Vermont, to complete his AS.

Conditions were poor during much of his session, Alan reports, and it's his opinion Lord Howe isn't a hot radio spot. He was caught in a radio black-out the day he arrived, and it took days to recover. Fifteen meters was practically useless, and he heard only one signal in 28 mc. Although the island is only 400 miles from Sydney the islanders cannot hear the medium and short-wave BC stations much of the time. About 80 calls found their way to Alan's black-list for violations of his "ten commandments." He spent several nights visiting VK2FR with the intention of showing him how to contend with the pile-ups, but they spent most of the time overhauling VK2FR's station, VK2QL reports. They got it fired up and worked about 200 phone contacts. VK2FR is now continuing Lord Howe activities. W2CTN is doing a magnificent job of handling the North American distribution of VK2AYY/LH cards, and will do the same for VK2FR in the future. For your Lord Howe QSL, simply send W2CTN your card and include a stamped and addressed return envelope. Duplicate cards may be obtained under the same system. Other zone #30 doings: VK0TC, 14008 kc CW, 0500; VK0KT, 14040 kc CW, 0500.

The Chatham Islands, zone #32, near New Zealand, will be counted as a new DXcc country after October 1, with credits for QSO's back to November 15, 1945. John, W6BYB, cut short his tour of the South Pacific islands because of cancellation of airline flights. He managed a few hours visit to ZM6AS on his return, and a longer stay in Fiji. The VR5 expedition plans had to be abandoned. While in the Cook Islands John Met ZK1AK, who turned out to be none other than ex-ZL1FT, a well-known DXer of years ago. VR2DA, Vataoula, Fiji Islands, quite active with 5 watts on a 6AQ5 doubler (!), with understandably weak but consistent signals, promises a fast QSL. VK9AD finally got on SSB with low power and a temporary dipole, but he's installing a Valiant and re-erecting his quad beam. Further from zone #32: VR2DG, 14050 kc CW, 1200; KS6AG, 14082 kc CW, 1000; W1IDL, 14037 kc CW, 1245; VR2DA, 14018 kc CW, 1000; FK8AS, 14175 kc AM, 0730; OS8AK, 21090 kc AM, 0400; ZK1BS, 14080

kc CW, 0900.

VQ9GU's remarkable four weeks' operation from the Seychelles, zone #39, ended with Jim's even more remarkable comment that he was amazed at the interest shown in VQ9 by DXers! He'll be back, he says, the next time with his own AC generator. If you missed him (and the chances are you did!) QRX for next year's Seychelles trip by VQ4ERR, who will also bring his own power plant. Heard Island has been abandoned and all installations removed. Further Heard Island operations are not likely. Other zone #39 interests: FB8XX, 14060 kc CW, 0910; FB8ZZ, 14049 kc CW, 1100; VQ8AL, 14040 kc CW, 0500; VQ8AJ/C 14098 kc CW, 1430.

LA4DD reports the regular Jan Mayen personnel, zone #40, will arrive about September 15th and will be on the air about the 20th, after their license arrives. The call letters are as yet unknown. Meanwhile, LH1B/P, Arne, reported to be on Bear Island (counts as Svalbard), has been active on 14070 kc CW at 0000. Others in zone #40: KG1DL, 14061 kc CW, 0900; KG1EE, 14050 kc CW, 1400; and TF2WCY, 21250 kc AM, 1900.

## QSL NOTES

Over 1200 cards, about 300 of which are for W's, arrived in OK1JX's mail box this month from Mila, JT1YL, her first shipment for world-wide distribution. These long awaited cards from a zone #23 YL will soon be in the mail to their addresses, direct mail if an IRC was sent OK1JX, via the bureaus if not. Only a very few—W6YK, W6YY, W1FH, W8BKP, W9RBI, W3JNN, and W2HTI—will receive phone confirmations; the rest are CW.

Also, over 800 cards from ZD7SA, via CN8GU, hit the mails this month, about 500 of them via the bureaus, the remaining directly (to those who sent stamped and addressed envelopes). CN8GU is returning to the States September first, but he will continue the ZD7SA QSL chores from this address: RFD #2, Mascoutah, Ill.

Gene, W2FXA, advises he is handling QSL's for Gaby, FY7YF, for the W2/K2 gang, but it is also possible for him to obtain QSL's for other than W2's if all other methods fail. For direct service a stamped and addressed envelope to W2FXA will be required. Otherwise, cards will be distributed via the bureaus. Foreign stations should include sufficient IRC's to cover postage.

Mac, K2QXG, who is currently handling the QSL project of VK9VM, discloses his system of handling the cards, which he says works like a charm. VK9VM tells all his QSO's to QSL via K2QXG. Mac has a stock of his cards, of course. Once a week VK9VM sends Mac an air-letter sheet (cost 10 cents to anywhere in the world) listing log data on all the W's worked during the week. When Mac receives the W's card and return envelope he makes out

the VK9VM card, slips it in the provided envelope, and mails it. It's as simple as that. The local WXers have their QSL's in a week, and the cost to the rare DX station is virtually nil.

"VK9VM tells me many W's send their cards direct air mail, and expect him to QSL the same way," continues Mac. "The cost? Oh, brother! If some of the W's would take on the job for just one rare DX station QSLs would be accurate, fast, and 100%.

"I don't send the DX Card until I get the W's first," he adds. "I've had several notes expressing appreciation for the fine service, which costs me about one hour of my time per week."

WPX			
CW		Phone	
W2HMJ	444	W8WT	337
W6KG	353	G3DO	315
W5KC	351	CO8JK	300
OK1MB	338		
SM5AHK	311		
W9BPW	310		
W9IU	346		
W5AFX	308	SSB	155
W1BFT	304		
LU5AQ	301		
W2DGW	301		
W8KPL	300		
SM5CCE	299		
DL7CS	299		
W1NLM	285		
W4KVX	172		
K6SXA	150		

## ADDRESSES

**BV1US**—(For QSO's from March 9, 1956 to Dec. 3, 1957) SFC Leo W. Fitzpatrick, K2MZM, HQ Det, QTC, APG, Aberdeen, Md.

**CE0AC**—c/o RCC, P O Box 761, Santiago, Chile

**CN9 QSL Bureau**—Amateur Radio Club Zona Norte, P O Box 124, Tetuan, QSL's may be sent via CN9BK, AAEM, or URE

**CN9BI**—Manuel Lobato Ricos, C. Mohamed V 13, Tetuan

**CN9BK**—Fernando Diaz Gomez, Pl. Ben Azuzz 3, Tetuan

**CN9BL**—Augusto Gruls Tintorel, Eletras Marroquies Presa del Lau, Beni Hassan

**CN9CA**—Luis Llodra Isaco, Cine Avenida, Larache

**CN9CB**—Pedro Rizo Buades, Avenida Navarra 8, Tetuan

**CN9CC**—Juan Astorga Quires, Avenida Navarra 1, Tetuan

**CN9CD**—Antonio Gonzales Ocana, Ada. Hospital Militar 8, Tetuan

**CN9CE**—Andres Trinidad Saiz, Cuartel Mejasnia Pabellones, Suboficiales, Tetuan

**CN9CF**—Carlos Irisarri Calwey, Pabellones Prensa, Tetuan

**CN9CG**—Francisco Gonzales Ocana, Pasa Buruaga 12, Tetuan

**CN9CH**—Rosa Fuentes Cascajares, Pl. Ben Azuzz 3, Tetuan

**CN9CI**—Enrique Perez Flores, C. General Aliau 2, Tetuan

**CN9CJ**—Juan Lopez Rodrigo, Avenida Hospital Militar C. Rabida 19

**CN9CK**—Francisco Torres Burgueno, C. Miramar 53, Rio Martin

**CN9CL**—Alfredo Feliz Gracia, Pl. Ben Azuzz 3, Tetuan

**CN9CM**—Juan Lozano Cabanas, C. Correo 1, Rio Martin (Tetuan)

**CN9CN**—Jose Miguel Sanches Ortega, C. Mohamed Ben Hossains 7, Tetuan

**CN9CO**—Antonio Martinez Moreno, C. Falange Marruecos 10, Tetuan

**CN9CP**—Hermelinda Cabanas Sesena, C. Mohamed V 13, Tetuan

**CN9CQ**—Carmentsoler Flores de Astorga, C. Antonio Navarra 1, Tetuan

**CN9CR**—Jose Fernandez Miranda, Iglesia San Antonio (Porteria), Tetuan

(Note: Include "Spanish Morocco, North Africa" with all the CN9's)

**CR6AI**—Joao Chaves, P O Box 64, Caala Angola

**ET2TO**—QSL to W0WET, Howard T. Olson Jr., 821 26th Ave. N E, Minneapolis 14, Minn.

**FP8AT**—QSL to K2GMV, 119 East 38th St, New York 16, N. Y.

**FP8AU**—QSL to K2GMV, 119 East 38th St, New York 16, N. Y.

**FP8AZ**—QSL via Richard A. Daynard, K2IAD, 55 Central W., New York, N. Y.

**FP8BA**—QSL via Jonathan M. Marks, K2YLD, 117-16 Park Lane S, Kew Gardens 18, N. Y.

**FU9AY**—QSL to Jacques Legoff, Base Chaleix Noumea, New Caledonia

**HB1UE/FL**—QSL via HB9UE

**HC4IM**—Box 4881, Manta, Ecuador

**HI8GA**—44, Dr. Delgado Street, Ciudad Trujillo, Dominican Republic

**I1DCO/M1**—Luigi Venuti, 13/3 Paolo Street, Ferrara, Italy

**KA5MK**—Marcel Kurbin, 610 AC&W Sq, Det 7, APO 929, San Francisco, California

**KB6BK**—Bill Mace, Canton Island, Phoenix Group, South Pacific

**KC6ZD**—J A Rudick, Kusaie, via Task Unit 7.1.3., Task Group 7.1., APO 436, c/o PM, San Francisco, California

**KH6AZM/KW6**—QSL to KH6AZM, Robert B. Figueroa, 1351 Palolo Ave, Honolulu, Hawaii

**KJ6BU**—Ray, 2011 Mormon Rd, Roanoke, Va

**KM6BL**—Navy 3080, FPO, San Francisco, California

**KM6EVK**—Navy 3080, Box 99 FPO, San Francisco, California



- 4AMX—c/o U S Weather Bureau, San Juan, Puerto Rico
- 6HP—QSL via Okinawa Amateur Radio Club, Box 739, APO 331, San Francisco, California
- 6AX—Midway Amateur Radio Club, Navy 3080, Box 19, FPO, San Francisco California
- 6BX—Bikini Amateur Radio Club, APO 436, San Francisco, Calif
- 6CD—QSL to Leonard G. Parsons, W5LGG, 246 Southill Rd, San Antonio, Texas
- 6CE—NAN Radio Club, Task Unit 5, APO 437, Box 5, c/o PM, San Francisco, California
- 6CF—Alfred L. Rich, FPO 824, Box 6, San Francisco, Calif.
- 6CI—Sandia Radio Club, c/o JTF-7, APO 436, c/o PM, San Francisco, California
- 6CJ—P. R. Cleary, FPO 824, Box 11, San Francisco, California
- 6CK—L. H. Bauer, Task Unit 7.1.3., Task Unit 7.1., APO 436, c/o PM, San Francisco, California
- 6CL—R. A. Irvine, Task Unit 7.1.3., Task Group 7.1., APO 436, c/o PM, San Francisco, California
- 6CM—Margaret K. Ryburn, 1960th AACs Sqdn, FPO 824, Box 811, San Francisco, California
- 6CW—William N. Ryburn, 1960th AACs Sqdn, FPO 824, Box 11, San Francisco, California
- 6BB—George H. Hamilton, P O Box 407, Balboa, Canal Zone
- 6RC—P O Box 634, Elisabethville, Belgian Congo
- 4ZI—"Ibsen," P O Box 3, Itauma, Brazil
- 2AR—Box 253, Khartoum, Sudan
- 0WT—(Crete) Frank Trull, Box 458, APO 291, New York, N. Y.
- 2AYY:LH—QSL via John M. Cummings, W2CTN, 159 Ketcham Ave., Amityville, N. Y.
- 9BS—c/o A.P.C., Port Moresby, Papua Territory, Australia
- 9CP—Rev. Fr. C. J. Patrick, QSL via VK9YT or VK9MK
- 9DT—Doug Taylor, Dept. Posts & Tel., Port Moresby, P. T., Australia
- 9GY—G. V. Campbell, c/o Post Office, Lae, T.N.G., Australia
- 9MA—Don Tranmer, RAF Gan Island, BFPO 180, Maldives Islands
- 9ML—M. S. Lang, O.T.C. Station, Rabaul, T.N.G., Australia
- 9NT—Norm Casey, Dept. Posts & Tel., Rabaul, T.N.G., Australia
- 9RD—Ruth Donovan, Dept. Posts & Tel., Port Moresby, P.T., Australia
- 9SB—D. S. Brown, Dept. Posts & Tel., Port Moresby, P.T., Australia
- 9VG—Howard Vinning, Dept. Posts & Tel., Lae, T.N.G., Australia
- 2DA—QSL via W8VDJ, Robert E. Lora, Shady Acre Golf Course, McComb, Ohio (Include stamped and addressed return envelope)
- VB7BH—Wm. E. L. Morris, NAA c/o PAA, Eleuthera AAFB, Patrick AFB, Florida
- VP8BJ—G. N. Biggs, 5 Dean St., Port Stanley, Falkland Islands
- VP8BN—Joe Booth, c/o Supt. Posts & Tels., GPO, Port Stanley, Falkland Islands
- VP7BT—J. R. Beck, c/o VP7NM, Box 48, Nassau, Bahamas
- VP8CC—C. Johnson, c/o Mr. L. Hill, 12 Greencourt Rd., Petts Wood, Kent, England
- ex-VP8CZ—QSL to G3LWS (via RSGB)
- VP8DE—P O Box 195, Port Stanley, Falkland Islands
- VP9EB—QSL via VP9CY
- VQ4FK—Post Office, Manyani, Kenya
- VQ4HA—J. Biron, Cable & Wireless Ltd., P O Box 777, Nairobi, Kenya
- VQ9GU—QSL to Jim Chapman, VQ4GU, East Africa Film Services, P O Box 2818, Nairobi, Kenya
- VR1C—Daniel J. Allen, c/o Wireless Dept., Betio, Tarawa
- VR2DG—QSL via VR2AS
- VR4CI—QSL via ZL1ADU
- VS1FW—B. J. Poole, G3MRV, R. N. Wireless Strn., Kranji, Singapore 23, Malaya
- VS1GC—Nev, Bedok Village, Singapore 16, Malaya
- VS1JF—QSL via F. Johnstone, VS1FJ, 52/6 Upavon Rd., RAF, Changi Singapore 17, Malaya
- VS2DQ—J. C. Pershouse, Sungei Raya Estate, Langkawi Island, Kedah, Malaya or P O Box 600, Penang, Malaya
- VS5AA—QSL via Malayan Radio Society, Box 777, Kuala Lumpur, Malaya
- VS6DX—Sid, RAF, Little Sai Wan, Hong Kong
- VS90—G3IRQ QSL via RSGB only
- W0BKL/KG6—P O Box 1363, Agana, Guam
- XW8AL—Phanh, P O Box 115, Vientiane, Laos
- YS1MS—W/K stations QSL to W3EQK, Arthur W. Plummer, 3804 Rexmere Rd., Baltimore 18, Md.; VE/VO stations QSL to VE3AML, Rowland C. E. Beardow, R R #3, Sarnia, Ont. (enclose stamped and addressed envelope for cards return)
- YS1TT—QSL via W3NHB, Robert Richardson, W3NHB, P O Box 154, La Plata, Md. (enclose stamped and addressed return envelope)
- YV0AB—QSL via KV4AA
- ZB1VJ—V. J. Debono, 25 St. Margaret St., Sliema, Malta
- ex ZC4FB—QSL to G3LWS (via RSGB)
- ZD6NJ—P O Box 88, Zomba, Nyasaland
- ZD7SC—A. J. Davis, c/o Cable & Wireless Ltd., "The Briers," St. Helena
- ZE6JX—Vic Holliday, P O Box 703, Bulawayo, Southern Rhodesia

**ZK2AB**—C. P. Slaven, Niue Island, via New Zealand  
**ZM6AS** — Via F. Hip Fenton, Civil Air, Faleoko, Western Samoa  
**ZP5LS**—P O Box 512, Asuncion, Paraguay  
**ZS8R**—(Outgoing cards) V. V. Parkhouse, c/o Audit Dept., Imperial Reserve, Mateking B. P., South America (incoming cards) Philippe A. Bates, W3SOH, 4223 Frost St., Philadelphia 36, Pa.  
**5A1TX** — Box 666, Tripoli, Libya, North Africa

### The Ohio Valley DX Bulletins

If you would like much faster and more comprehensive DX news coverage and articles than space in this column can permit, we suggest you try the weekly Ohio Valley DX Bulletins, edited and published by W4KVV. Annual rates, for a minimum of 40 issues, are \$5 second class mail, \$6 first class, \$7.50 air mail, to the U.S., Canada, and Mexico, and \$4 a year plus postage to other countries. Write W4KVV (address at the head of the DX column) for further details. Sample copies are available upon request.

### de DL4LR/W2LR

"I recently returned from a four-year tour in Munich Germany where I operated DL4LR. If such a request is in order, I would appreciate a note in your DX section to the effect that I am back home to stay and will gladly send QSL's to any U.S.A. ham whom I have missed. I have my logs and plenty of QSLs on hand." G. L. Graveson, W2LR, 74 Washington Avenue, Amityville, New York.

### ADDRESS INDEX

Do you need an address that's been published in CQ this year? You can find it in the DX Department of the issue listed below. This list will be accumulative until December, when we'll drop the whole thing and start anew.

CE0AG	May	FP8AY	Feb
CN8GU (ZD7SA)	Aug	FY7YE	Mar
CN8IF	Feb	G3LWS/VP8	Sep
CN8JX	Feb	G5RV	Jul
CO2YZ	May	GC3MFS	Sep
CR4AH	Aug	HA8WS	Feb
CR8AC	Feb	HB1PL/AR	May
CT2BO	Sep	HB1RS/FL	Feb
CX3CS	Sep	HC1BP	Sep
DL4 QSL Bureau	Jul	HC8GI	Feb
DL4BL (K4ADU)	Feb	HE9LAC	Mar
DL4DH	Aug	HI8RM	Mar
DL4TW	Aug	HK7AB	May
ET2TO	Jul	HL2AM	Feb
EL3B	Aug	HL9KS	Mar
ET3PRS	Aug	HL0KT	Sep
FA3DU	May	HND9A	Aug
FB8XX	Feb	ex-HR2WC	Jul
FE8AK	Feb	HS1A	Mar
FF8AC	Feb	HS1C (ex-K2VOV)	Mar
FK8AS	Sep	I1AFS	Sep
FL8AC	May	JT1AA	Feb
FP8AB	Sep	JZ0HA	May
FP8AR	Feb	JZ0PB	Aug
FP8AS	Feb	K2IVJ/VE8	Sep
FP8AX	Feb	K6ICS	Feb

K8JTI/VE8	Sep	VP2AZ	
KA2MP	Mar	VP2KM	
KA2NY	Sep	VP2LB	
KA2QT	Sep	VP2LO	
KA6ZS	Feb	VP4TF	
KA8KW	Mar	VP4WI	
KA2IJ	Sep	VP5BE	
KA2SC	Feb	VP5FH	
KC4US	Feb	VP5RD	
KB6BH	Aug	VP5TS	
KB6BJ	Sep	VP8CI	
KB6BL	Sep	VP8CR	
KG1BB	Feb	VP8CW	
KG4AQ	Mar	VP8CY	
KG6FAE	Mar	VQ2FC	
KL7CEW	Feb	VQ3DQ	
KP4ANU	Jul	VQ4AQ	
KR6JR	Jul	VQ8AJ	
KR6QM (K9CZX)	Jul	VQ8AS	
KS6AD	Feb	VR1A	
KS6AG	Sep	VR3A	
KW6CA	Mar	VR3O	
KW6CE	Feb	VR4CW	
KX6CH	Jul	VR6TC	
LA2JE/P	Sep	VS1HJ	
LB9OE	Sep	VS1HS	
LJ3D	Sep	VS1HU	
LU1ZS	Mar	VS1HZ	
LZ1WD	Sep	VS6DS	
MP4BCG	Mar	VS9AG	
MP4BCK	Sep	VS9AG/ZD3	
OA4AP	Feb	VS9AJ	
OA4IGY	May	VU2 Bureau	
OD5CB	Sep	VU2GE	
OK1LM	Sep	VU2RC	
OO5IE	Sep	W4FCB/KS4	
OR4VN	Sep	W4QCW	
OY7ML	Sep	W4WHP/KG6	
PI1LS	Jul	W7CKY/KL7	
PJ2SA	Feb	WV4BW	
PJ3AB	Jul	XE0DOT	
PJ5AA/PJ5CA	Feb	XE0UN	
PJ5CB	Aug	XE0UUE	
PY3ANS	Sep	XV5A	
PY4AO	Sep	XW8AE	
SM8AQT/LA/P	Sep	ex-XW8AG	
SM8BYG/MM	Sep	XW8AI	
SP5KAB	Sep	XZ2OM	
SV1AB	Mar	XZ2SY	
SV1SP	Feb	XZ2TH	
SV0 Stations	Feb	YJ1DL	
SV0WB (Rhodes)	Aug	YU1UB	
SV0WE (Rhodes)	Aug	ZB1DS	
SV0WK (Crete)	Aug	ZB1DZ	
SV0WN (Crete)	Aug	ZB2R	
SV0WP	Mar	ZC4FL	
SV0WQ (Crete)	Feb	ZC4FM	
SV0WZ (Crete)	Aug	ZC4IP	
TF2WCO	Sep	ZD1EO	
UA1KAE (All)	Aug	ZD1FG	
UA9DK	Feb	ZD3F	
UA9DN	Mar	ZD3G	
UA0LA	May	ZD7SA	
UB5DW	Mar	ZD7SB	
UB5KAB	Mar	ZETJF	
UO5AA	Mar	ZK1BS	
UO5PK	Sep	ZS6AQA	
UQ2AN	Sep	ZS9G	
USFA	Sep	3A2 Bureau	
VE3AHU/SU	Feb	3V8CY	
VK2FR	Jul	4W2RP	
VK4AL	Aug	4X4DK	
VK9AD	Feb	5A5TK	
ex-VK9JF	Sep	9G1BL	
VK9RR	Aug	9G1BQ	
VK9VM	Sep	9G1CH	
VK0AS	Feb	9G1CM	
VK0TC	May	9K2AN	
VP1DL	Sep	9K2AP	
VP1WN	Sep	9K2AQ	
VP2AB	Sep	9K2AZ	



by THOMAS K. AALUND, K2VBI

Box 11, Roslyn, L. I., New York

## overseas echoes

Word comes from Telefunken that one of the pioneers of electronic tube development in Europe has passed away. Professor Hans Tukop, who died recently at the age of 75, was connected with tube development at Telefunken since 1914. He was on their board of directors until 1950 and later acted as a technical consultant for Telefunken. Time passes almost unnoticed and we hardly realize that our 'young electronic industry' is slowly reaching a rather mature age and has come a long way since its infancy.

But problems are part of development and our frequencies are getting more and more crowded. We all have noticed that commercial stations appear from time to time on frequencies allocated exclusively for the use of amateurs. Some of these stations appear to be operating on definite schedules, others only occasionally. A noteworthy step has been undertaken by Swiss amateurs, according to *Old* *an*, July 1958, HB. The USKA is sending at to all their members, report cards to be filled out and to be returned to USKA. These report cards contain space for time, date, frequency, as well as type of emission. A space is also provided for remarks. Who knows—maybe some day these cards will accumulate sufficient quantities and they may have enough weight to influence the powers that be. How about some other clubs considering something along similar lines?

The Boletín Informativo CRAG, April 1958, TG9, carried a reprint of W2NSD's editorial in the January 1957 issue of our CQ and also excerpts of his editorial of the January 1958 CQ. They urge all amateurs to take note of these editorials, particularly in view of the forthcoming conference on frequency allocations. We are pleased to note that they concur with the opinion of W2NSD and agree fully with their recommendation. The CRAG, incidentally, is looking back on a ten-year history as a very active club in Guatemala and its tenth anniversary was even given considerable space in one of the local newspapers here.

Amateur callbooks of the ARRL as well as other countries are a nice thing to have, but even with the most diligent efforts it is not

possible for all calls to be listed correctly, as there are new calls being issued daily, QTH changes, etc. Various foreign club magazines list up to date call sign directories from time to time, and this writer will make an effort to keep these listings on hand. A self-addressed envelope will bring a prompt reply giving the latest QTH if available. At present the following ones are on hand: TG9 as of April 1, 1958; OE, as of July 2, 1958. The *Short Wave Magazine*, July 1958, G, also starts with this issue a complete listing of all British mobile stations (separate license required for mobile operation in G), including call, bands worked, type of car and even license plate number. These are not changed there annually as they are here, so that they are a handy means of identification. The listing is not complete, but subsequent listings will be published. There are about 550 hams in G licensed for mobile operation. As a point of interest it might also be mentioned that they have 65 amateurs licensed for amateur television transmission.

Das Elektron, June 1958, OE, covers several applications for transistors and this writer took interest in two of the circuits offered: One is a two-transistor flasher unit for signaling devices using a six volt input and having a frequency of 1.5 cycles; the other is an AC power supply of approximately 50 watts output and having very good frequency accuracy, making it suitable for running such items as tape recorders from a low voltage DC power source.

With all the foreign publications that go through the hands of this department the question came to our mind if it is not a bit confusing to the average amateur to figure out just what type of tube might be referred to when you see, to take an example, ECC91 referred to in a European magazine. How many people know that this is a 6J6 or how many people have the means of finding such information? This writer is at present compiling a listing of American-European equivalents and it will be published in the pages of CQ as soon as it is complete. Any additional information will be published later as it becomes available.

73, Tom, K2VBI

# VHF

**50mc. 144mc. 220mc. 420mc. and above**

by **SAM HARRIS, W1FZ**

P.O. Box 2502, Medfield, Mass.




**Len Berg (SM6BTT) at six meter operating position.**

Two meters makes the headlines this month with the passing of the annual Perseids Meteor Shower. It is hard to evaluate the potentialities of a Shower using only the number of contacts completed as a measure. Many of the reports indicate fewer long bursts and fewer contacts than had been expected.

It has been three years since I have had any meteor skeds during the Perseids. This year I spent eight hours a night listening to schedules in all directions. The frequency of pings, bursts, etc., were certainly on a par with those of three years ago. For instance W5JWL

managed to put in 8 overdense bursts of 20 second duration one half hour period. (Later reports indicate that he heard nothing from me.) WØIFS in Minnesota was heard from Maine to Florida. All reports indicate numerous 30 second overdense bursts. W4EQM was heard (and worked) by many stations in the New England area and as far west as Illinois. All in all, I heard workable signals from Minnesota, Arkansas, South Carolina, Alabama and Mississippi. At last report W9WOK needed only Georgia for all states east of the Mississippi and a grand total of 40 states.

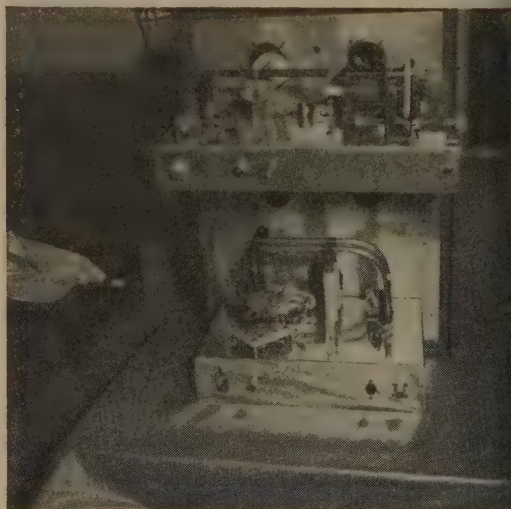

**144 mc rig (Swedish style) as of a year ago.**



was quite apparent however, that many acts were flubbed due to inexperience with high overdense occurrence found during Perseids. This shower practically guarantees one or four 15 to 20 second overdense bursts per hour. Twenty seconds is long enough to exchange calls, reports and SK's. If, however, schedule calls for 30 second transmissions from one guy followed by 30 seconds from the other guy, ad infinitum, it is obvious that optimum utilization of overdense bursts is not being obtained. For instance, while listening to the W0IFS-W1AZK schedule, I heard two successive 30 second, 5-9-9 transmissions from W0IFS followed two minutes later by another second 5-9-9 burst. As of last reports however, no contact was established. A simple one minute and a break takes about 7 seconds. If another operator happens to be awake he can waste another second getting back, and about 9 more seconds giving your call, his report and BK. You have used up 30 seconds of this burst and it behooves you to get on the ball. Proper procedure is R, 5-3, BK. Do not sign your call on this break. If you just don't have seven seconds to waste and you have already identified yourself and acknowledged his call on the previous break. Now comes the biggest hassle of all. If your overdense burst has petered out, you don't know if you heard your report and roger. He may feel you have made a complete contact and you feel without his final roger you haven't. If you are lucky and the burst holds out for another 5 seconds you will hear his SK, your call, his report. Now he is worried about whether you got SK or not. If your burst will last for another 5 seconds he is all set except you are not sure that he got your final OK etc.

The point is: During this entire burst you are exchanging information. No one has properly defined just what constitutes an exchange of information. Obviously if I hear you give my call de your call and break and I give you back and you hear me give your call de my call, we have exchanged information. Reports, R's and SK are more information. Where do you draw the line? For example, in the last 30 seconds of one of the half minute transmissions from W4EQM, I heard him S9 sending FZJ de W4EQM. Fortunately this was the ending of my 30 seconds and I sent EQM de W1FZJ, R, S2, BK. Whereupon I sent W1FZJ de W4EQM, R, S2, S2 and out I went. Now any fool can see that we exchanged information. But did we have a contact?

### Convention

The national convention at Washington done and gone. Things to remember: W1HOY, W1RUD, W1PYM and W1FZJ walking up to Washington Monument (889 steps) to save elevator fee (10 cents per.) Elevator ride was free.

VHF sessions included the "Antique Wireless Association's" latest slide show entitled "The World Above 50 Mc." Hank (W2UTH) presented the show and I can assure you it shouldn't be missed. Walt Bain (W4LTU), Ross Bateman (W4AO) and Steve Martin presented some good information on a parametric amplifier using PSI's vari-cap as the active element. Some excellent noise figures were obtained at H. F. and good results are predicted at VHF. CW assignments on the VHF bands was the prime topic of conversation. E. P. Tilton gave the best advice of all. "Don't waste your time arguing. Write the F.C.C." (Too late now.)

### CW Versus Phone

My Position on the cw versus phone has certainly been expressed in the past few years. No one has pushed harder for a voluntary cw band on two meters. I have an aversion to increasing the legislation within our band limits. I don't like a few "do gooders" telling the world how nice it would be if everybody thought like them. I think that it is the duty of our league to make a survey of the likes and desires of the members involved before making any recommendations to anybody about anything. I question the qualifications of anyone on our board of directors or on our payroll at Headquarters (EPT excepted) to make any decision or recommendation concerning amateur radio in the VHF region. Maybe you like a dictatorship but I am an American and I have come to like the democratic way of doing things.

### VHF Convention

The "Syracuse VHF Round-Up" is due again. The date—**October 11, 1958**. Advance registration must be obtained from W2EMW, 18 Homeland, North Syracuse, New York. Write now! Do not delay! Old Meteor Scatter himself, Walt Bain, will be the principal speaker. Large VHF forum with all the experts on the panel will follow. Special entertainment for the ladies. Good food, plenty of room, dancing to follow. Don't miss this one. Bring your C.C.C. cards and get your certificate on the spot.

### 1215 MC Record

Those intrepid W6ers have gone and done it again. W6QDJ/6 and W6MMU/6 operating portable from Mt. Pines (el. 8830 ft.) and Mt. Hamilton (el. 4420 ft.) respectively, made contact using the 1296 mc band. The 225 mile path is far from line of sight being mostly over a mountain chain with 5000 foot peaks. Equipment used included crystal controlled transmitters with 2C39 triplers in the output and crystal controlled converters (Microwave Associates 1N21 E's in the front end of course). CW was employed at both ends of the contact.

Mid-path assistance was provided by W6BUT at Taft, California, located approximately 195 miles along the path to the south of Mt. Hamilton. The two meter liaison equipment failed to make the grade over this difficult path and W6BUT provided the only pre-contact liaison. Credit for assistance should go to W6FZA, W6ABN, K6TAM and anybody else who helped. Those W6ers sure are triers. Guess us East coasters will have to import some west coast talent if we want to keep up. . . .

### Bag Bottoms and Coffee Pots

I don't know how they manage to do it but it seems that if the boys in the "Queen City Emergency Net" get ahold of 1000 bag-bottoms from Kroger Spotlite or French brand coffee bags they can get a forty-eight cup coffee urn. All good coffee drinkers and Hams are urged to send their bag-bottoms to W8MXR, 3862 Malaer Drive, RFD #2, Sharonville, Ohio. Bag-bottom donors from out of state are entitled to one free cup of good coffee upon application in person.

### Moon Bounce

Just as you have got used to not hearing about it, I feel that it is time to mention it again. No news from anywhere else at this time but W1FZJ is back on it again. Antenna is working and transmissions are being made each night during the period starting eight hours after moonrise and ending nine hours after moonrise, GMT. Transmissions are limited to the nighttime hours or between 2300 hrs. GMT and 1200 hrs GMT. (Still have to work for a living.) Transmissions are on the odd five minutes, frequencies ten kc above and below the transmitter are monitored on the even five minutes. Antenna at present is 128 elements on an el az mount. Schedules are solicited from interested parties. Transmitter frequency is 144.250.

### Goteborg S, Sweden — From Len (SM6BTT) via Leroy (W5AJG) we receive the following:

"I had schedules with OE6AP May 3, 4. His rig is 80 watts, 14 elements and E88CC xtal converter. E88CC is a European twin-triode with a transconductance of 12000 ohms, noise figures of 3-4 db is obtainable in Wallman cascade circuit. OE6AP didn't hear me and I didn't hear him either, but SM4BIU with 24 foot long Yagi heard some S6 bursts. However, the problem is that the distances are too short, about 650 miles. It's difficult to get schedule partners at the easy 0900-1300 mile range here in Europe."

"Tests with HB9RG during June 8th gave us two S7 bursts at his end. At 0911 local time he got me for 30 seconds but only at strength S3. I am sorry to say that I heard only a few weak pings from him, the Perseids will give us QSO's though."

"The NBS prediction cards for MUF gives us 50 mc hopes too. The MUF is rising during August and September and reaches 28 mc during September. As I have only the 1958 prediction cards I can't make any comparisons with 1957. Suggest that we had the peak last year, and then the band must be opened this fall and winter too. (This after studying 50 mc for years of 1946, '47 and '48)" Thanks for the interesting information Len (and Leroy). Hope we all see you on six again this fall and winter.

### Anchorage, Alaska—From the cold front at Jack Reich (KL7AUV), we hear that:

"Jim Tyrdy, KL7CDG, is being transferred to States at the end of August, but the rest of us locs are getting in shape for a good season, we hope. I expect to have my RTTY gear operating on six at will, believe CW will be my main mode. Built a new converter which isn't completely wiped out by Channel 2 five bands away, and hope to be able to operate West and Southwest afternoons and evenings while Channel Two is on. That RTTY sounds good to us Jack, maybe we'll see you there."

### Sudbury, Ontario—A bit of news from Don Mac Lean, (VE3CKA):

"There are five active stations on six meters here VE3BEK, VE3CJM, VE3CJI, VE3CJN and VE3CJ. Three of us are using Gonsets, thanks to the local C.D. had a fair opening on July 6th with some very strong steady signals, lasting about six hours. There was another on the 31st but not like the first."

"The band is monitored by VE3BEK fifteen hours a day, so how about you southern boys keeping the band up north?" Sounds like a good idea Don, we'll surely be a-lookin'.

### Cold Spring, Minnesota — Gerald Th (KØGLV) sends a bit of information from location:

"I have been on six about four weeks. Have no local activity within about seventy miles, so—so far no luck. The rig is a homebrew running about 20 watts and 4 element beam and a converted AR 2 feeding into a old S.R. 19. Would very much like to hear from anyone close to central Minnesota and try this rig out." With it you Minnesota gang, make Gerald's receiver sound like an opening.

### South Lancaster, Massachusetts—Some news from an expedition (all over now) and Maurer (W1QMS).

"Monitored six meters from Prince Edward Island from July 6th-14th. Used Gonset III with R9'r antenna. The 5 element Hi-Par beam was erected on the highest spot on the island and pointed at Massachusetts. Didn't even hear Helen!"

"Although plagued by two full days of radio blackouts and no openings I have some good news. I succeeded in getting Smitty, VE1ZM, on six and worked him mobile and fixed. He is now running 50 watts, has a hot converter, and a five element beam. I believe this is a first and he wants to work out. Look for him on 50.5."

"Needless to say my Saturn 6 Halo 'took' the island and the VE1's marveled at the Gonset III packaging. F. B. Mac, glad to know the VE1's are interested, will surely be looking for them."

### Forest City, North Carolina—Wayne McLeod (K4RSP), a newcomer to VHF sez:

"Would surely appreciate any information on converters, rigs, antennas etc., from anyone who would care to write. Have just been bitten by the VHF bug and need information on everything." Happy to welcome you to the ranks of VHF men, Wayne, and know boys will come through for you.

### Rahway, New Jersey—Bob Brown (K2ZS) sends us a little information about a lot of people.

"I just got up a 5 element beam, what a difference. Also got my dad on six meters, K2ZSP. He is on evenings usually after 1830."

"Several new stations on six locally K2MMM, W2A and K2ZDI, all of Rahway."

"My 35watt homebrew transmitter was built by Mike K2DZM, who is active on 6, 220 and 420. He has worked 11 states on 220. Runs 100 watts on all VHF bands. Uses an HQ129X for a receiver. Mike has a two meter ground plane, a 4 element 6 meter beam and two very long beams for 220 and 420."

[Continued on page 98]



# CONTEST CALENDAR

September	27-28	MARC VE W
October	4- 5	YK ZI Phone
October	11-12	YK ZI CW
October	11-12	Peruano Phone
October	18-19	Peruano CW
October	25-26	CQ WW DX Phone
November	8- 9	ARRI SS
November	15-16	ARRI SS
November	22-23	RSGB 21 28 Phone
November	29-30	CQ WW DX CW

## /ZI

This popular contest with the boys "down under" starts at 1000 GMT Saturday and runs a 24 hour period. We told you all about it back in July. This year you send your logs to the N.Z.A.R.T. Contest Committee, Box 489, Wellington, New Zealand.

## PERUANO

This one is a Pan American affair and offers good opportunity to get some of those missing countries for your WAA certificate. You have 36 hours starting at Noon EST Saturday to compete for a certificate. July Calendar has the details. Your log should be mailed within 20 days to: Radio Club Peruano, Attn. C. Omission Concursos, Casella 538, Lima, Peru.

## Air Force Mars Eastern Technical Net

Sundays 2-4 PM EDT 3295 KC, 7540 KC, 15,715 KC

- Oct. 5-12—Transistor Fundamentals—Panel of engineers from Philco Corp. Transistor Laboratory.
- Oct. 19—Information Theory—Mr. John Pierce of the Bell Telephone Laboratories.
- Oct. 26—Satellite Tracking at the Yale Observatory—Mr. James Douglas of Yale University.
- Nov. 2—Radio Traffic Control—Commissioner T. T. Wiley and panel, N.Y.C. Dept. of Traffic.
- Nov. 9—Sourcing and Curing Radio Interference—Mr. Harry Wallace, Consulting Engineer.

## WORLD WIDE DX CONTEST SCHEDULE

		Phone	
Time Zone	Starting Time	Ending Time	
GMT	Sat. Oct. 25th 0200	Mon. Oct. 27th 0200	
EST	Fri. Oct. 24th 9:00PM	Sun. Oct. 26th 9:00PM	
PST	Fri. Oct. 24th 6:00PM	Sun. Oct. 26th 6:00PM	
CW			
GMT	Sat. Nov. 29th 0200	Mon. Dec. 1st 0200	
EST	Fri. Nov. 28th 9:00PM	Sun. Nov. 30th 9:00PM	
PST	Fri. Nov. 28th 6:00PM	Sun. Nov. 30th 6:00PM	

## MARC VE/W

The annual Canadian/U.S. party is held the last week end in September. Work any 20 hours out of a 30 hour period beginning at 6 P.M. EST Saturday. Use any band, phone and CW, everything counts. See last month's calendar for details. Send your logs to Contest Chairman, Gordon H. Webster, VE2BB, 69 Pine Beach Blvd., Dorval, Quebec, Canada.

## CQ WW DX

You can't blame us if you don't know about this one. Rules in detail were published in the August issue. Copies were mailed to all foreign amateur journals as well as leading U.S. clubs. And each winner in last year's contest also received a copy. There is still time for you to send for a supply of log sheets and report forms. Send us a large self-addressed

*[Continued on page 100]*

## ARMY MARS

Wednesday Evenings 9 PM (New York Time whether EDT or EST) 4030 kc upper sideband.

- Oct. 1—"Engineering the White Alice Network" by Robert B. Stecker, Supt. Systems Engineering, Defense Projects Division, Western Electric Company.
- Oct. 8—"Characteristics of SSB Power Amplifier Circuits" by Warren B. Bruene, Technical Consultant, Collins Radio Company.
- Oct. 15—"Technical Facilities of Radio Free Europe" by Claude M. Harris, Director of Engineering, Radio Free Europe.
- Oct. 22—"Application of Transistors to Power Supply Equipment" by Sidney Moskowitz, Vice Pres. Electronic Research Associates, Inc.
- Oct. 29—"Maser Amplifiers and Oscillators" by Dr. Gerhard Weibel, Section Head, Submillimeter Research Section, Sylvania Electric Products Co., Inc.



The 8th Midwest YL Convention held at Toledo, Ohio on May 22, 1958, brought together these 27 Yls. L to r., front: W9SJR, W8's HWX, VWL, HRS, OTK. Second row: W8ATB, W4BLR, W8's RZN, HUX, MBI, VJO, W3UUG, W9's MLE, YWH. Third row: W9AYX, K9EMS, W9LRT, W8's IDV, VRH, RIR, M4E. Fourth row: K8's EJX, HWC, W8KLZ, W9RUJ, KN8JWQ, K8BPQ.



The 19th YLRL Anniversary Party will be held Nov. 12-13, 1958 (phone) and Nov. 19-20, 1958 (cw). Rules will be given in November CQ.

by **LOUISA B. SANDO, W5RZJ**  
212 Sombrio Drive, Santa Fe, N. M.

#### AWTAR

The 4th of July started off with a "roar" instead of a "bang" in San Diego—the roar of 61 planes taking off for the 12th Annual All Woman Transcontinental Air Race, with destination of Charleston, S.C. For the 6th year a network of amateur stations was in operation to relay information to race officials and to handle messages for participants in the race.

Radio chairman at San Diego was Pat, W6GGX. Other members of the San Diego YLRC operating W6GGX/6 (on 7210) at the Ninety-Nines Hq. in the Lafayette Hotel and W6MWU/6 relaying on 2 meters from the air-



W5TXK, Margaret, operating at the Jackson, M airport during the Powder Puff Derby. She was assisted by members of the Jackson Amateur Radio Club.



were K6QKE, Mavis; K6UHI, Betty; K6VRH, Ellie; W6VSL, Barbara; W6WDL, Babs; W6MWU, Mary; K6MGL, Becky, and hence Irwin assisted in logging plane information. Nightly skeds were kept between GTC, Carolyn, amateur net chairman, who is in Charleston, and Pat, W6GGX, on 20 meters via the SSB stations of W6JUT and 1TWW.

Other YLs who assisted were W7DRU, Fran, Tucson; K5MIN, Vera, at Abilene, Tex.; 1TMD, Betty, chairman at Tyler, Tex., assisted by Dextra Rogers, W5TYK, Margaret, chairman at Jackson, Miss.; K4AIQ, Carolyn, chairman at Macon, Ga. W4VCB:3, Ev, spent many long hours at Charleston assisting GTC.

On July 9 when the winners were announced in Charleston, W6QPI, Betty Gillies, AWTAR chairman, gave the information to Carolyn who relayed it to race officials in San Diego via BPL.

The YLs participating wish to thank each of the Hams who assisted in relaying traffic and helping to keep the net frequencies clear. They also appreciated the loan of Halliater's equipment at several of the stop-over cities.

### WITH THE CLUBS

The 4th Anniversary Party of the Texas YL Round-up Net will be held Nov. 8 at Tyler, Tex.,—"Rose Capitol of the World." Hostesses for the get-together will be W5's YAJ, LGY and K5's IHF and IMD. Reservations for the luncheon and party should be made with 1TMD, Betty, by Oct. 30. The TYLRUN at its writing numbers 106 members from Texas, La., La., N.M., Ark., Colo., Mo. and Kans. The LARKs held their annual family picnic in June and at that time elected these officers for the coming year: President, K9IVG, Roberta; VP, W9TMS, Blanche; sec'y, K9BWJ, Mary Alice; treas., K9EMS, Eve; Novice rep., 9IWR, Lynn. The LARK's cw net now meets Mondays at 1 p.m. CST on 3750 but NCS 9MYC will tune down the band for Novices. Members of WHOOT initiated their club call, K5QHI, and their transmitter and receiver modified by W5MTQ, for Field Day. WHOOT now offers a club certificate: Work even of their members, July 1, 1958, or after, and send log information (no QSLs) to Ruth Jones, K5GMI, 1908 Argentinia, Dallas, Tex. ZS6GH, Diana, 1958 secretary of the SAWRC, advises that the WAYL certificate costs 2/6d (7 IRC) and the KKK certificate is — (double the price of the WAYL certificate). SAWRC has quite a few W girls as members, and welcomes any others who are interested. Dues are \$1 a year.

The HAWKS of Indiana had a fine feature write-up in the Sunday Magazine section of the Indianapolis Star for July 27. It included a number of photos and details about many of the members, including 76-years young Lulu



## AMATEUR RADIO EQUIPMENT

*Courtesy of*

## WESTERN RADIO & TV SUPPLY

1331 INDIA ST. SAN DIEGO

Some of the San Diego YLs who assisted with the AWTAR radio net. L to r., W6GGX, Pat, S.D. chairman; W6VSL, Barbara; K6VRH, Ellie, and W6WDL, Babs.

Perrine, K9BZU, and Priscilla Rae Organ, Kn9MPN, who has become a Ham despite handicaps of spinal arthritis and impaired vision of 26 years duration.

### HERE AND THERE

W4UF/W4ZKD, Dot, was invited to present a paper on her research work on blood parasites at the 6th International Congress of Tropical Medicine and Malaria at Lisbon, Portugal Sept. 5-13. Dot planned to leave Florida in mid-Aug. to fly to England for a three-week visit there and in Scotland before flying to Portugal. . . . W4BWR, Ruth, is happy over her OM winning a '58 Mercury. Didn't take her long to get an Elmac installed in it.

How is this for coincidence—Jane Purcell of Hollywood holds the call Kn6RGM; her OM has the call Wn6RGM! No doubt by this time they both have Generals.

Bina, PY4APA (featured in this column in March CQ), has been released from the hospital and has an apartment in Tulsa with her sisters Eunice, PY4AUT, and Ziza, PY4AUL.


When Colfax, Wis. was struck by a tornado in June, W9RUJ, Mary, spent the night handling traffic. . . . KØATT, Freda, has been more than busy in the midst of the Kansas floods.

*[Continued on page 114]*

# SURPLUS

by **KENNETH B. GRAYSON, W2HDM**

110-20 71st Ave., Forest Hills 75, N. Y.

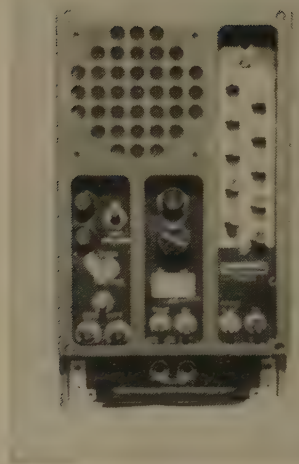

**Just about everyone** who dabbles in surplus converting has been interested in doing a job of the BC-603. And well they might, for this unit is available for under fifteen dollars just about everywhere, and is usually in pretty good shape.

If you are interested in a wide band FM receiver then you are all set to go by just powering the thing. But chances are that you will be wanting to change the original tuning range of 20-28 mc to the 50 mc band and modify it for AM reception. Last month we went into the six meter conversion and ac power supply for it. This month we cover the de-FMing of it, a much more formidable task. You see, once you start looking closely into the bowels of the 603 you find, much to your dismay, that all of the wiring has been made into a harness and is stuck together permanently with goo. This means that you have to perform major surgery for even minor conversion attacks.

Because FM is wide in bandwidth due to the sideband distribution, the FM receiver must be equally as wide in order to pass the necessary intelligence. It is common to "load" circuits in order to increase the bandwidth by adding resistors across the tuned circuits to decrease the Q of the circuit. This is what was done in the BC-603. Therefore the first part of the conversion is to remove the loading resistors and sharpen the receiver selectively.

The actual process of removing the components used to broaden the receiver is accomplished by removing one i-f transformer at a time by unsoldering the leads going to its terminals and removing the shield and transformer mounting hardware. When the shield is removed, the components will be visible. Un-

solder all resistors and those capacitors used for by-passing and save them for future use. The by-pass capacitors are square postage stamp type mica capacitors and usually have one lead connected to the screw stud used for mounting. The four rods (one in each corner) are all of the connections we will make use of. All other connections at the base are not used and may serve as tie-points later on. Note that the ends of each coil are terminated at these four rods, and that the resonating condenser is mounted between two of these rods. Each resonating condenser is about 50 mmfd. in value. With all unused components removed we will have a conventional i-f transformer with a resonant frequency of 2.65 mc or a little higher. Check the resonant frequency of each coil with a grid dip oscillator. Don't forget that there is an additional capacity due to wiring and tube capacity yet to be put across each coil, therefore the coils will probably resonate a little higher in frequency . . . say 2.8 mc. Reconnect the transformer after remounting it, using only the plate and grid connections. The AVC and B-plus connections will be added later.

The only i-f transformer that may give you trouble is the final one, FL-4, originally used as a discriminator transformer. On this one again remove all components including the resonating capacitors, but leave the coils alone for the time being. Clean up all excess solder and then carefully remove the bottom section of the output coil, leaving two identical coils one on each ceramic form. The leads of these coils should be connected to the corner rods as in the original transformers. A 56 mmfd is all that we should have to use in order to resonate each coil, but use a grid dip oscillator to check this to be on the safe side



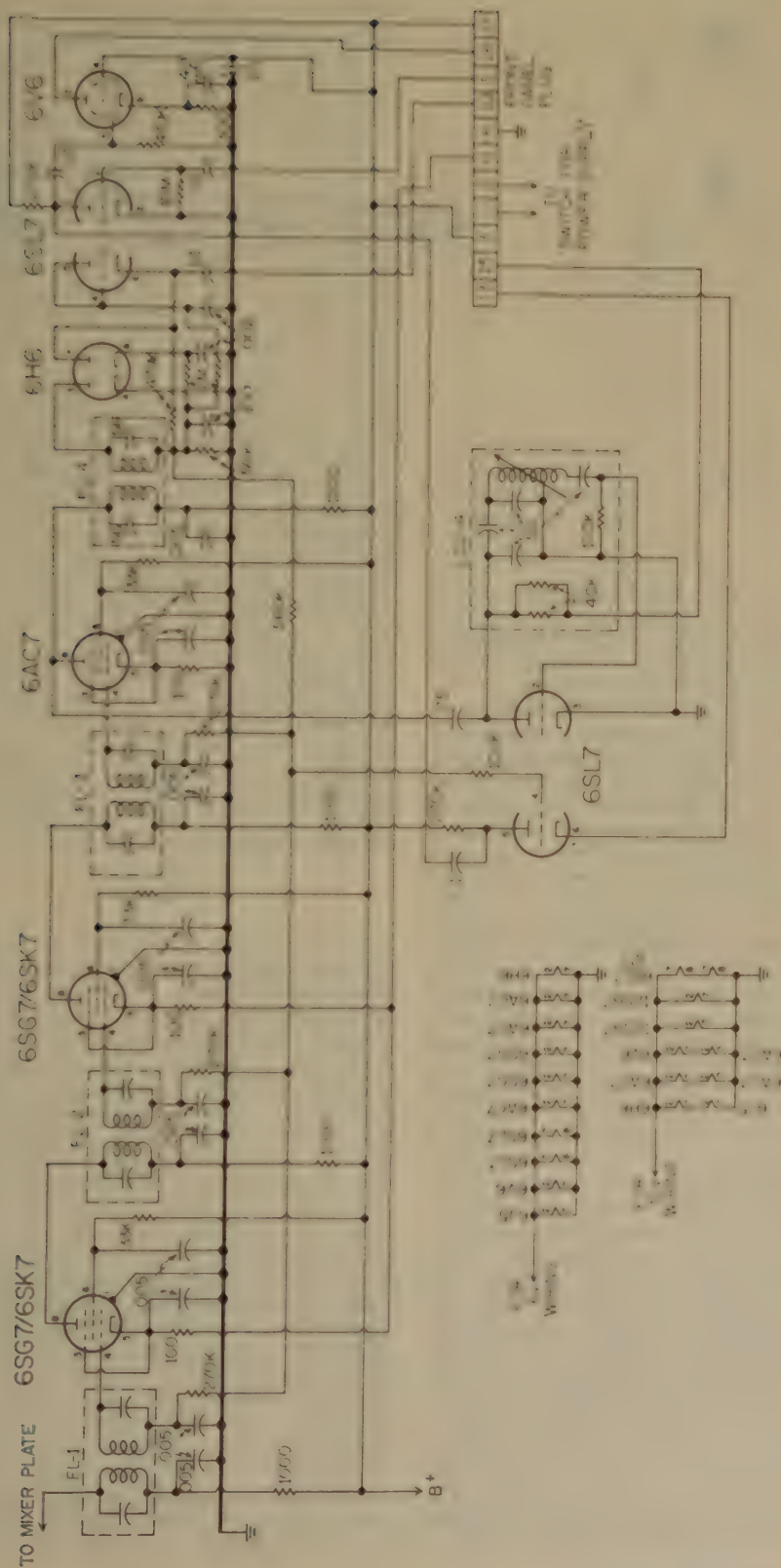


Fig. 1—Circuit of the modified i-f, detector, noise limiter, and audio of the BC 603.

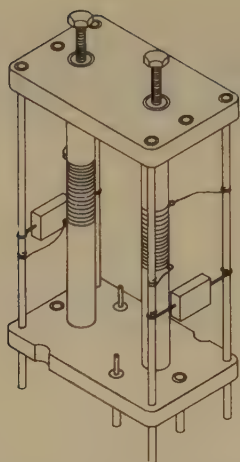


Fig. 2—BC 603 i-f construction.

once you install the condensers. It may be necessary on all of the transformers to adjust the slug screws in order to get to the exact frequency we want, and we will definitely have to do this later when we align the set.

The next step is the hardest (the hardest to get yourself to do). Completely remove all terminal boards, the main harness, and clean up all the terminals going to the front panel plug and all of the unused (so far) terminals on the tube sockets. That should sound like a big job—well it is. First a word of reason is in order. We found that a very complicated delayed avc circuit, a squelch circuit, a sensitivity control and an operator's alarm circuit were giving us a real headache. As a matter of fact this one part held us up for a full month. Next, the conversion can be speeded up by not relying upon the tracing of leads covered with that moisture and fungus paint that always gets in your way, and third why leave a lot of useless components hanging around especially since they aren't being used. Once you reconcile yourself to the facts it isn't too bad at all.

Rewire the filaments. It is up to you to decide what voltage you are going to use here. For mobile use six or twelve. For ac operation use 6 volts. When this is completed, wire in the plate and screen supply voltages, and then the avc voltages also known as the grid return. The detector and the noise limiter, audio and audio output stages and the bfo if you have removed anything from it are all that has to be done to complete the receiver. That is a big job, though and the circuit is shown in figure 1. Remember that the bypass capacitors should be wired with leads as short as possible. It may take a bit of hunting for it, so we'll give you the clue that the 6V6 cathode bias resistor is located near the two bath-tub

condensers on top of the wiring side of the tuning condenser. Remember that the values shown on the diagram, with the exception of the i-f tuning capacitors are relatively not critical. Any value within 20% of the value shown should work with little change in performance.

Naturally a noise limiter is needed and we added one of a very simple nature (sourced Radiotron Designers Handbook), together with a diode detector to provide avc. We left the bfo alone and it is still operated by the TUNE switch on the front panel. No modifications were made on the front panel wiring, and all connections to the front panel were made using the panel plug. Note that the volume control is on the front panel, so make sure that the leads going to the volume control are short and away from the leads going to the output transformer which is also located on the front panel. Getting back to the noise limiter, we found that two diodes were needed. Having only one left over from the other half of the 6H6 detector, we made use of the other half of the 6SL7 used for the audio amplifier by making the triode into a diode merely by connecting the plate to the grid. The other 6SL7 is used for the bfo and the squelch. The original squelch circuit of the BC-603 used a very complicated network and was fairly effective. We can't say the same for the one we used, except that it is simple and fairly effective. One more thing to remove is the inductor in the cathode of the limiter. This was used in the process of limiting and will find no use in an AM set, therefore take it out and add it to your junk box.

## Alignment

The alignment of the set is probably going to be the most tedious part of the conversion. The i-f transformers should all be about the same frequency without any further adjustments, so apply power and first check to see if the bfo is working. This can be done by using a grid dip oscillator as an absorption wave meter, or by actually measuring the grid bias of the oscillator tube. It will be on 2.65 mc providing nothing was touched inside the can. Using the bfo you can beat the signal provided by the grid dip oscillator to get an audio tone to tune in on. Of course a signal generator should be used if one is available. Start by connecting the signal generator (set 2.65 mc and modulated) at the grid of the last i-f amplifier and adjust the slugs of the output transformer. When they have been peaked, go to the grid of the previous tube and peak this. Keep this procedure up until you get to the grid of the mixer. Here you should pull the oscillator tube (6J5) out and peak all of the i-f transformers for a clean tone. Any sudden change in tone should be checked and if in doubt, turn the signal generator off for a

[Continued on page 102]





by DONALD L. STONER, W6TNS

P.O. Box 137, Ontario, Calif.

# Novice

The intense activity of the summer is letting up somewhat. Now that school has started the Novice bands are a little less crowded. On 15 meters, Novices were heard from dawn to dusk and a contact could always be had on 40 meters. Summer static was pretty bad on 80 meters but that will let up for the winter and Q5 contacts will be the rule rather than the exception. But enough of these reflections, let's get down to the business at hand.

I ran across a good deal on a book, that some of the readers may be interested in. The title is "Troubleshooting and Repair of Radio Equipment" and is available from the Government Printing Office, Washington 25, D.C. under the number D 101.11:11-4000. The cost is \$2.00 check or cash. The manual contains a wealth of information on the techniques of troubleshooting receivers and transmitters. It would be a valuable addition to your hamshack.

## THEORY

Last month we discussed oscillations and their connection with mechanical devices. It would be nice if we could connect an antenna to that steel rule (that was used to demonstrate oscillations) but unfortunately, that won't work. Why not, the man asks? Well, here's why not. The rapid motion of the rule created changes in air pressure that we call sound. Changes in air pressure don't travel very far before they are dissipated or confused with other pressures. How far can you yell? A mile? Possibly, but you surely couldn't make WAS that way! Rather than try to move the air, how about moving the tiny molecules that exist all around us? To do this, we must use electromagnetic energy, or radio signals as some people call them. Another thing wrong with propagating sound is that it is low frequency, usually in the hundreds or low thousands of cycles. To transmit electromagnetic energy to distant places usually requires frequencies that are millions of cycles per second.

As you may have guessed, the electromagnetic energy is in the form of an oscillation, but it is a variation (above and below an aver-

age point) of electrical potential (voltage). The transmitter supplies the electrical potential (in the form of oscillations) to the antenna, and the antenna radiates the oscillations in the form of electromagnetic energy. You might think of the molecules that exist between your transmitter, and the other fellow's receiver, as a long line of ping-pong balls. Your antenna energy "bumps" the first ball, which in turn bumps the second one, which in turn bumps the third one, and so on. Thus, at the receiving station the motion of the molecules duplicates the energy that was radiated by the antenna. In essence that is how you communicate with other stations. But, remember, it takes high frequency electrical oscillations (that are converted to electromagnetic radiation by the antenna) to accomplish this wonder. Also keep in mind that the antenna is like an electromagnet (which radiates magnetic force) and the transmitter is like a battery used to power the electromagnet.

Let's see how oscillations are created in the transmitter. The oscillator section is the heart of the transmitter, and the heart of the oscillator (in a Novice transmitter) is the quartz crystal. As you may know, the crystal determines the frequency of the oscillations, but you may not understand why. Last month we spoke of mechanical resonance. The piece of quartz that is placed in the holder is etched or ground so that it is mechanically resonant at the frequency marked on the case. When the crystal is "twanged," it will oscillate just like the steel rule. However, the oscillations will not be so extreme and they are very fast (you cannot see them). To start the crystal oscillating, we do not "twang" it with a finger, as we did the rule, rather we apply a pulse of voltage to it. Upon receiving the pulse, the quartz will start to oscillate at its natural resonant frequency, but the oscillations will die out very rapidly unless they are sustained. This is where the oscillator tube enters the picture. When the crystal oscillates, it generates a tiny voltage. This voltage is applied to the input of the oscillator tube. The tiny oscillations from the crystal are amplified in this tube (in other words the power or voltage is increased). This amplified oscillation

is applied (or fed back) to the crystal to sustain the oscillation. If this feedback voltage was not present, or was not strong enough, the stage would not continue to oscillate.

Fig. 1 shows a very simple oscillator circuit. The input to the tube is the grid and the output is the plate. The cathode is common to both input and output. The signal appearing in the output circuit is fed back to the crystal and also used to drive a power amplifier stage. The other end of the crystal is connected to the grid circuit (input) and the voltage "goes around in circles" from output to input. This is known as *feedback*. A similarity can be found in the public address system in your school. A person talks into the microphone (input) and the amplifier increases the level of his voice until it is strong enough to operate the speakers (output). But what happens if the microphone picks up the sound of the speakers? Feedback occurs between the input and output and you hear a very loud piercing squeal. This squeal is an oscillation! The acoustics of the room (and other factors) determine the frequency of the squeal. Thus, the room is "equivalent" to the crystal and the amplifier is "equivalent" to the oscillator tube. Next month we shall see how the oscillation and the oscillator stage fits in with the rest of the Novice transmitter.

### NET NEWS

Fred Leggs, KN9MXK, Indianapolis 2, Indiana, would like to start a Novice net and would appreciate tips and suggestions from anyone.

"The Palmetto Novice Net of South Carolina has not been in operation during the summer but will resume operation on Sept. 8, on 3745 kc at 2000 EST." All Novices are invited to check in, for more info write John W. Fuller, K4HQK, P. O. Box 407, Barnwell, South Carolina.

K1CVH, 194 Maxfield St., New Bedford, Mass. writes to inform us of a teen-age phone net on 40 meters. Teen-agers and/or ex-Novices are invited to check in. For more information write Bill, K1DDR, 210 Oberlin Rd., Hamden, Conn.

### WHO'S DX?

Staff Sgt. Bud Lafferty, KG1CK, has had considerable trouble with the QSL situation. I am having cards printed for Bud, and if those of you that have worked KG1CK will drop me a self addressed stamped envelope, I will check the contact against Bud's log and QSL for him. Sorry for the delay fellows, but these things happen.

Don Grantley, WIA-C2022, Mount Raven, Holbrook NWS, Australia, is a new DX reporter. Don's list of Novice stations heard in Australia is included in the column this month.

Another short wave listener, Jack Rouse, 96 Ward Street, Wallingford, Conn., advises us

that UA3KWA is always on the lookout for Novices on 15 meters, and has in-fact worked quite a few.

Hugh R. Paul, Jr. W8LMK, Paw Paw Michigan, sent along a photo of his friend Ken Haswell, G2CWL, and wishes to advise the readers that Ken works Novices on 15 meters. Look for these fellows.

### HELP WANTED

The Pomona Valley finally has a radio club and they are starting Novice code and theory classes. Club meetings the 2nd Wednesday of every month. For more information on the Novice classes, contact Hillis Hauck, KN6DQA, 794 Gleneagles Avenue, Pomona, Calif., or phone National 28993.

Paul Nugent, W1JNX, 149 Millet St., Boston 24, Mass., will be very glad to assist anyone in his area get a ham license. His phone is Columbia 5-4196.

Bob Brown, K2ZSQ, 67 Russell Avenue, Rahway, New Jersey, can be counted on for a helping hand to anyone that wants to obtain a ham ticket.

The following persons have written requesting help with the examinations. Can you help them?

W1—Ronald Wilbur, 199 County Street, Taunton, Mass. Telephone Vandyke 2-6928



Lon Woodbury, KN7BOM, Box 63, Kingston, Idaho has QSL wallpaper. Lon has a WAS of 45 and needs Vt., Nev., and Colo. to complete the list. Listen for him on 40, running the S-20R and Adventurer.



W7—Ronald White, 540 NE 44th, Apt. 7, Portland 13, Oregon  
 W9—Curtis Ewing, 528 North Earl Avenue, Lafayette, Indiana. Phone 29-8516  
 W0—Tom Vars, 1804 Stanford, St. Paul, Minn. Telephone MI-95343  
 Thomas L. Lloyd, Green City, Mo.  
 Douglas L. Millburn, Toddville, Iowa  
 Elsewhere—A/2c Fred Strickler, AF-2737, Box 475, 6930th RGM, APO 291 N. Y., N. Y.  
 Billy Mason, 3070 N. W. 186th, Miami, Florida. Phone NA-12754.

## LETTERS

Irving Livant, KN2JUG, RD #1, Ludlowville, N. Y., wonders about using a switch to change impedances on the Heath AM-2. I don't think it would be a good idea to switch the tiny rf voltage, Irv, but you might try it.

Herb Howe, KN7CWO, 527 S. Vancouver St. Kennewich, Washington, wrote a nice long letter describing his home brew transmitter and NC-173 receiver. He runs 8 watts on the 40 meter band and has accumulated 7 states so far.

John Pitman, WV6BGD, 610 Vesta St., Ontario, California, is knocking them dead with a Command Transmitter (per The Novice and Technical Handbook) running 20 watts input. John QSL's 100%, likes to gab, and would like pen pals.

Another friend, Steve Nix, WV6BMI, 334 Beverly Court, Ontario, California, doesn't even know he has a ticket yet. The little white envelope arrived the afternoon of the day that he left on vacation . . . hi

Carl Wells, KN6GUI, 2916 Heather Avenue, Redding, California, has collected 30 states and 3 countries with a DX-20 and an S-40A. He would like to sked Mont., Wyo., and Arizona on either 15 or 40 meters. All letters answered.

Al Marcus, KN6TQB, 574 Ninth Avenue, San Francisco 18, Calif. had a strange case of

BCI. Seems a little ole lady complained because Al "was playing his radio (ham rig) so loud." It turned out to be a defective air raid siren two miles away and was heard all over San Fran. Waaah, we get some pretty bad heterodynes out this-a-way.

Art Cheshire, 426 Elm St., Jonesboro, La. stomps 'em with a DX-40 and HQ-110 and has worked 29 states and 3 countries on 15. Art would appreciate some help with a new 15 meter beam.

Charles Carter Woodman, KN0KXR, 630 S. Patrick St., Rapid City, S. Dakota, reports that he seems to get maximum output from his WRL Globe Chief 90 at 140 ma. of plate current.

John Aldrich, WINZZ, 103 North St., Lakeport, N. H., is open for Novice skeds if anyone needs that state. John is on all Novice bands.

Ed Dougil, Jr., KN20SC, 310 Ann St., Harrison, N. J. reports that he worked one of our DX reporters, Ivor Stafford, VK3XB, with a homebrew 6146 rig and an SX-99. The WAS total is 20 states.


Don Johnson, KN0QMU, 3527 Knox North, Minneapolis 12, Minnesota, has worked 7 states and 23 contacts in his first week of operation with a Globe Chief 90A and an S-40. He QSL's 100% and would like 80 and 40 meter skeds.

Charles F. Ackerman, WV2APX, 620 Fairview Avenue, New Market, N. J. operates on 80 meters with a DX-20 and SX-99 receiver. The antenna is an eight foot mobile whip. His first contact was with KN2RBI.

William Ziegenfus, WV2AXJ, 48 Madison Avenue, Lindenwold, N. J. got tired of waiting for his Novice, so he tackled the General and passed before the Novice ticket arrived! He is currently running a NC-109 and is planning on getting a Heath Apache.

Bob Saville, KN90KE, 6903 N. Kimberly Drive, Peoria, Illinois, uses a NQ-110 and a Globe Scout 680-A on the 40 and 15 meter bands. Bob thanks W9FM and K9EMJ for their code and theory classes that were held at the Peoria Area ARC.

*[Continued on page 118]*

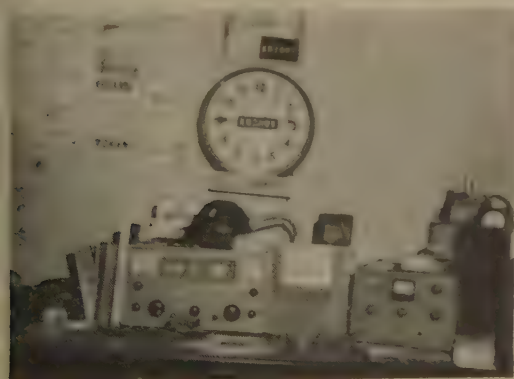

Bill Sharp, KN2HBV, 618 N. Salina St., Syracuse 8, N.Y. sends a "sharp" picture of his Knight 50 watt rig, and HQ-100. Bill has worked 500 QSO's and has most of them confirmed!



Ken Haswell, G2CWL, will be listening for Novices on the 15 meter band. Thanks to Hugh R. Paul, Jr., W8LMK, for supplying this picture.



# ham clinic

by **CHARLES J. SCHAUERS, W6QLV**

CQ Magazine, 300 West 43rd St., New York 36, N. Y.

**The best overall investment** an amateur can make is in good reliable test equipment. Why? Well, for one reason it seldom if ever becomes obsolete. Of course there are exceptions. But the ham who buys a good vacuum tube voltmeter today for example can look forward to it giving years of satisfactory service if handled properly.

Skimping on test gear is not understandable when one willingly pays \$500 or more for other equipment. Like insurance, test equipment when needed can sometimes approach "pricelessness"!

The selection of test equipment should be carefully done. It is better to pay an extra dollar or two for an accurate test unit than to hobble along with a real cheap device whose accuracy is always in doubt. Where money is a prime consideration, the do-it-yourself kits as offered by Allied Radio and the Heath Co. should be considered.

Recommended for the amateur just starting out as well as the firmly entrenched experienced ham are the following items of test gear: vacuum tube voltmeter; grid-dip meter; pocket volt ohmmeter with a sensitivity of at least 5000 ohms per volt and a good pair of high impedance headphones. With these items, nearly all modern circuits can be readily tested.

The ham who has invested \$1000 or more in equipment may be wise to buy a good tube tester too; but not one which tests for emission only. The set should be a mutual conductance (gm) tester and also contain provisions for indicating tube element shorts.

Many hams are not cognizant of what can really be done with the very popular grid-dip meter. This instrument, for my money, is worth more to me than any other test gadget I have. With it, frequency, rf loading, capacitance, inductance, parasitics and many other factors can be measured. By adding a 400 cycle modulator to it, it can be used for BC receiver alignment (if it is voltage stabilized and carefully calibrated).

To the serious ham an oscilloscope is a must. With it he can make very close measurements and analyze circuit performance with

very little difficulty. For the SSB enthusiast a scope often spells the difference between low and high efficiency.

If you like working with transistors, a vacuum tube voltmeter is quite essential because it takes very little power from a circuit and makes for accurate parameter measurement. Having high Z input, it will not disturb circuits whose circulating currents are minute—but important.

The lowly headphone can be used in a number of ways. In audio circuits, it can be used for signal tracing in conjunction with a blocking condenser. With a battery it can indicate open coils, shorted condensers, open resistors, poor relay contacts and many other things. Only in very high Z circuits does it fail to perform well.

Knowing how to use test equipment is another matter. More meters have "popped their innards" through operator carelessness than any other piece of electronic gear. A wise precaution on any ham's part is to buy a few *Littlefuses* made especially for test instruments. There is wisdom in burning out a few low priced fuses instead of an expensive microammeter.

Are you one of the many who forgot to switch from ohms to volts to suddenly find himself with a meter whose needle resembles a pretzel? Well, have courage—don't give up the ship! You are not alone. Experience still seems to be the best teacher.

Caring for test equipment properly is a very important matter. If you are like many of us, you'll never give much thought to cleanliness of switch contacts, loose knobs, old batteries, loose jacks or internal corrosion. But one day a particular instrument will stop working and you'll realize that a certain amount of instrument maintenance is necessary. A well maintained instrument is a safe instrument!

Prior to coming to Europe I happened in on a Novice who was testing an old surplus power transformer with a pair of test leads whose prods were badly insulated. Come to find out, 2000 volts were lurking in the wind-

[Continued on page 109]





# 1958

## RADIO-ELECTRONIC MASTER

(22nd edition)

biggest most authoritative buying  
guide ever published

### TV - RADIO - AUDIO - ELECTRONICS

Completely catalogs over 150,000 standard electronic parts and equipment necessary for amateur and industrial applications. It places at your fingertips 350 factory prepared catalogs in one bound volume.

only \$3<sup>50</sup>  
at your distributor

### 1584 pages

The world's largest and  
most referred to electronic  
buying guide contains...

direct-from-the-factory pro-  
duct information covering  
150,000 items produced by  
350 manufacturers

- ★ complete descriptions
- ★ specifications
- ★ prices
- ★ 11,500 illustrations

#### When you BUY... DESIGN... ASSEMBLE... REPAIR

You can immediately find out... What product best  
fills your needs? How does it compare with other  
models? What does it look like? What does it cost?  
...because the MASTER is systematically arranged  
in 18 product sections with all similar products  
grouped together.

Save time and money when you buy, design, repair or  
assemble, you'll save money and time by getting the right  
product to do the job because you are shopping in the  
electronic supermarket. The MASTER. Its product-packed  
pages give complete information on communications  
receivers, transmitters, hi-fi components, cabinets, racks,  
chassis, lenses, crystals, microphones, and many hard-to-  
locate items not usually shown in the smaller, incomplete  
catalogs.

Remember, no matter what product or component you  
require... **YOU FIND IT FASTER IN THE MASTER!**

Get your 1958 MASTER today at local parts distributor or order direct. Act now - the supply is limited.

The Radio-Electronic MASTER 60 Madison Avenue, Hempstead, New York

Here's my \$3.50. Please rush me the 1958 MASTER, Official  
Buying Guide of the Electronic Parts and Equipment Industry.


Name .....

Address .....

City ..... Zone ..... State .....

For further information, check number 22 on page 126.

# NOW *custom designed* CONSOLES

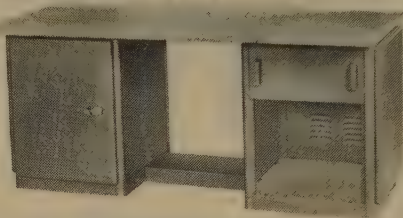

## AT MASS PRODUCTION PRICES

The new Bud Console Assembly is the modern concept in versatility and utility whereby a number of individual units may be quickly and easily combined to provide housings for electrical or electronic components or instruments.

Since all the components may be ordered separately and assembled on the site, substantial savings can be made in shipping and manufacturing costs.

The Bud Console Assembly consists of a number of units which are adaptable to control or testing centers of 3 standard sizes while a combination of these can provide practically unlimited expansion possibilities.

The components of the Bud Console Assembly comprise pedestals, ball cornered sides, ball cornered doors, panels, tops, drawers and other units, all beautifully finished, ready for assembly.

For your housing requirements involving consoles, see your nearest Bud distributor or write for Bulletin 4458 for complete description.




**BUD RADIO CORP.**  
2118 East 55th Street  
Cleveland 3, Ohio  
Dept. C
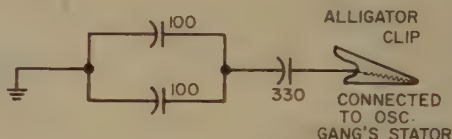
## BC and SPUTNIK, too

by Karl Thurber, Jr., K2IKZ  
247 Hamilton Road,  
West Englewood, N. J.

When it was first announced that the USSR had launched an artificial satellite, I, like thousands of other amateurs throughout the world, turned to the ham receiver to hear that latest choice DX item, Sputnik I. That is just fine, except that the receiver here at K2IKZ is the National Co.'s NC-300, covering only the ham bands; in addition, no spare receivers were to be had which would tune 20 megacycles. After a little experimentation, a simple condenser combination was devised to allow tuning 20.005 with the receiver set to the 15-meter band.



The "gizmo" is simply 2-100 mmfd silver mica condensers (parallel), connected in series with a 330-mmfd silver mica. The "gizmo" is clipped between the stator of the oscillator (first from front) gang of the large 3-gang variable, and ground.

Using a crystal calibrator and/or WWV's 20-mc signal, the operator should tune across the range until the 20-mc signal is heard; Sputnik's channel is 5 kc higher. Record the dial reading so that you will be ready for future "baby moons."

Using this easily-improvised set-up, excellent tape recordings of the satellite's signals were made.

For those of you who still listen to the standard broadcast band (you'll find DX there, too!) it was found that the same condenser combination would bring in the high-end of the broadcast band, 1430-1600 kc. Larger value condensers extended the receiver's tuning range lower in the band, but tracking and sensitivity was somewhat impaired as the frequency range was lowered.

It would seem reasonable to assume that other ham-bands-only receivers could be modified without "digging into" the receiver, with little difficulty.

It is probable that the Soviets will continue to use the 20-mc frequency for some time to come. The Soviet magazine "Radio" designated this range, along with the 40-mc channel, for future satellite launchings.

How about trying this modern version of SWL'ing?—Interplanetary style.



## BOOKSHOP

- 1 **Electronics & Radio Eng. by Terman**  
1378 entertaining educational pages, this one is a  
gotta-for every hambook, too bad it's so expensive \$13.50
- 2 **E. E. Handbook by McIlwain**  
1618 pages, a better buy than Terman, but  
it gives out formulas, tables & circuits, not so much  
explanation \$10.00
- 3 **Cybernetics by Weiner**  
No reason to buy this one except it is a classic & the  
title is visible from 10 feet. Confusing \$3.50
- 4 **Electronics Manual for Radio  
Engineers**  
You'll never find twice as much book for half the  
price, guaranteed rouser almost a corker \$14.00
- 5 **Antennas by Kraus (W8JK)**  
Handy if you ever plan to understand antennas \$10.00
- 7 **SOS At Midnight by K6ATX**  
Ham adventure book, dunno why we advertise it here  
\$2.75
- 9 **License Q & A Manual**  
Newest dope on commercial licenses, become a pro-  
fessional for \$6.00
- 11 **Radio Handbook by W6SAI**  
Another guaranteed rouser, great book, hundreds of  
bits, a hambook gotta this is the book \$7.50
- 13 **Reference Data, 4th Edition**  
1142 pages of pure data, data, data... facts \$6.00
- 16 **Ham Register by W3VKD**  
Hardest no shock is complete without this, real  
interesting \$5.00
- 20 **RTTY Handbook by W2JTP**  
A-Z of ham teletype, supply running out, very popular  
\$3.00
- 21 **VHF Handbook by W6QKI**  
Covers just about every aspect of VHF \$2.95
- 22 **Beam Antenna Handbook by W6SAI**  
Practical, includes both theory and construction \$2.70

- 23 **Novice Handbook by W6TNS**  
Receiver, transmitter and antenna theory and construction  
for the Novice and Technician. Terrific \$2.85
- 24 **Better Shortwave Reception by W6SAI**  
Fine handbook for SWL'ing, long needed \$2.85
- 25 **Mathematics for Electricians & Radio-  
men by Cooke**  
This is the standard text book in this field \$5.50
- 26 **Surplus Radio Conversion Manual I.**  
BC-221, 342, 312, 348, 412, 645, 946, 1068A, SCR-274,  
522 TBV, PE-103, etc. \$2.50
- 27 **Surplus Radio Conversion Manual II.**  
BC-454-459 Xmit-Rcvrs, AP5-13, ARC-5 VHF Xmit-Rcvrs;  
BC-357, 946B, 375, TA-12B, ART-13, AVT-112A, GO-9,  
LM, etc. \$2.50
- 28 **Television Interference by Rand**  
Latest complete dope on flicking TV! \$1.75
- 29 **QSL Album for WAS by Hanover  
Products**  
Mount your 48 cards for display \$3.50
- 30 **Miniature Call Letter License Plate**  
No \$ available, sorry 75c
- 32 **RCA Radiotron Designers Handbook**  
1500 pages—fabulous \$7.50

Permission granted to use separate paper if you want.  
OK fellas, send me postpaid the items circled, and get  
a move on.

1	2	3	4	5	9	7	11	13	15	20
21	22	23	24	25	26	27	28	29	30	32

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_  
Cash, check or money order enclosed, of course.  
N.Y.C.'ers add 3% Sales Tax.

### Radio Bookshop

1379 East 15th St., Brooklyn 30, N. Y.  
Patronize Ham Industry, bub.

# db's

Cloice W. Proctor, W8PMD

Staff Engineer (Philco)  
Engineering Division  
Product Division

The author wishes to make no claims as to the originality of the following, but has used it with considerable success while teaching basic electronics to Airmen of the United States Air Force.

The decibel and its relationship to power ratios, voltage gains or losses, etc., has always been a source of much confusion among students of electronics, hams and others, unless he was capable of handling logarithms, powers of tens and mathematics of considerable depth. Even then, it requires the use of a log table or slide rule to compute even the simplest problems involving the decibel.

Examination of the formula for decibels shows that db equals 10 log P1/P2 (when power ratios are known). Since the computation of decibels involving voltage or current ratios assumes a common impedance be at all

times considered, it is usually prudent to ignore all but power ratios until one becomes familiar with the mechanics involved. Consulting either a log table or a slide rule we can easily determine that 1 db is equal to a power ratio of 1.27:1. Further investigation would reveal that 2 db is equal to a power ratio of 1.6:1 (approximately). It is interesting to note that 1.6 is the result of raising 1.27 to the second power. (1.27<sup>2</sup> × 1.27 equals 1.6). As all amateurs know 3 db equals a power ratio of 2:1, which is the result of raising 1.27 to the third power. (1.27<sup>3</sup>). In short then to convert decibels into the equivalent power ratio, it would only be necessary to raise the figure 1.27 to the power equal to the number of decibels involved. Obviously this requires far too many separate steps and becomes hopelessly awkward when many db are considered. A greatly simplified method becomes apparent when the following table is considered.

1. db. equals a power ratio of	1.27 : 1
2. db. equals a power ratio of	1.6 : 1
3. db. equals a power ratio of	2.0 : 1
10. db. equals a power ratio of	10.0 : 1
20. db. equals a power ratio of	100.0 : 1
30. db. equals a power ratio of	1000.0 : 1 etc.

It is interesting to note that db's can be added



# EI

Presents . . .

# STEREO

... the fabulous new way to hear sound. In the November **ELECTRONICS ILLUSTRATED**, there's a *special* section on Stereo Hi-Fi that tells you all about: the latest in stereo components; how stereo records are made; how to build a complete stereo record player for \$25.00!; a free source of stereo music via FM-Multiplex; and many other features on bringing stereo into your home. In addition, the November **EI** brings you an inside story on the race into space, "Shooting for the Moon," and an informative piece on fixing your own TV set.

So don't miss the stereo-filled November issue of **ELECTRONICS ILLUSTRATED**.

In fact, don't miss any of the great issues of **EI** coming up. Get in on the new subscription offer right away. Just fill in the coupon below and enjoy receiving **EI** right at your door every month.

## SO DO IT NOW!

Please enter my subscription to

**ELECTRONICS ILLUSTRATED** for:

1 year: \$3.00 ☐

2 years: \$5.00 ☐

In U.S., possessions and Canada.  
All other countries, \$6.00 per year.

NAME.....

ADDRESS.....

CITY..... ZONE..... STATE.....

Mail to: **ELECTRONICS ILLUSTRATED**  
Circulation Dept.

**FAWCETT BUILDING, GREENWICH, CONNECTICUT**

arithmetically, while the ratios naturally multiply. Let us consider the problem of converting 16 decibels into its equivalent power ratio. 16 db equals 10 db plus 3 db plus 3 db. Converting to equivalent power ratios we can not  $10 \times 2 \times 2$  equals 40. Therefore 16 db represents a power ratio of 40 to 1. Since decibels represent ratios only, a positive 16 db would indicate a gain of 40 to one, while a negative 16 db would represent a value of  $1/40$  of the original value. By the same reasoning 37 db can be converted to its equivalent power ratio. 37 db equals 30 db plus 3 db plus 3 db plus 1 db. Converting to power ratios we find that  $1000 \times 2 \times 2 \times 1.27$  equals 5080. Consequently 37 db gain implies a power ratio of 5080 : 1.

From the foregoing it can be seen that any decibel to power ratio can be converted easily in a matter of seconds. Further it requires no reference tables or slide rules. It is necessary to commit to memory only the ratios equal to 1 db; 3 db; 10 db and so on. A few minutes practice with this system will permit anyone to equal the best slip stick artist in solving problems involving decibels and power ratios.

### HARMONICS [from page 46]

for low power using silver mica condensers. It is now possible to use disk ceramic 1200 ohm dc condensers enabling the filter to be used on kw rigs. The disk condensers, while they are not extremely accurate or stable, are good enough for this application. The actual cut-off frequencies of the filter is between the amateur bands. This was done to make the input and output impedance 50 ohms in the band pass of the filter. (See fig 1). If the filter was designed for a cut-off at the high end of the amateur band the impedance using this constant K filter would be high, increasing the SWR and pop the condensers. It would be necessary to go to a more complicated M derived filter to accomplish this. Long as we are only interested in cutting off before the second harmonics, this filter is satisfactory.

At the present no other solution presents itself to those who insist on using all-band antenna systems. There is less than 1 db loss in these filters. The entire price to construct all of these filters should not exceed the price of a regular low pass filter. Yet this filter has the advantage of preventing TVI, plus reducing QRM to your fellow amateurs on the higher bands.

### Theory

The action of the filter is based upon the fact an inductance represents a low impedance to low frequencies and a high impedance to high frequencies. Whereas the opposite conditions occurs with a capacitance. When inductance

[Continued on page 108]



# World Radio's Reconditioning Department



Leo I. Meyerson, W4GFQ, says, "Here's a part of our reconditioning department where five trained technicians are continually repairing and perfecting used equipment. As many as 500 new items go through here each month. But we need more. Over the years we have built such a tremendous market for used equipment, that sometimes we even have a waiting list for certain items. Because of this guaranteed market, we can offer you a better price on your trade-ins. We want them! We need them! We'll allow more for them! Let us give you our top quotation for your present gear when you buy your new NC-300."

Guarantees **YOU** THE BEST, HONEST  
TRADE-IN OFFER  
on National's exciting new



**NC-300**  
DREAM RECEIVER

Amateur Net:  
\$399.00

Only  
**\$22<sup>95</sup>** per mo.

your present equipment  
may be enough for down  
payment.

Stable! Sensitive! Features 10 dial scales for coverage of 160 to 1 1/4 meters with National's exclusive new converter provision with receiver scales calibrated for 6, 2 and 1/4 M, using a special 30-35 tunable IF band. Longest slide rule dial ever; more than 1 ft. Three position IF selector - .5kc, 3.5kc, 8kc - provides super selectivity. Separate linear detector for single sideband. Calibration reset adjustable from front panel to provide exact frequency setting. Dual conversion.

XCU 300 Plug-In Crystal Calibrator: \$23.95


**FREE — Limited Time Only!**

2400 Hour Clock with NC-300 Purchase

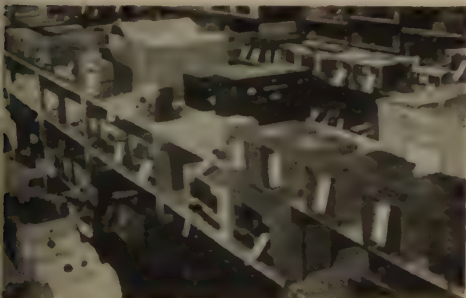**\$15<sup>00</sup>**

VALUE

Gives 2400-hour time every hour of the day in every time zone all over the world. Key cities shown clearly. Direct reading, no computing or calculation necessary. Order your NC-300 now while this offer lasts. Clock will be mailed to you and guaranteed by clock manufacturer.



Dear Leo: Please send your free 1959 Catalog, information on the National line, and quote your best trade offer on my present

for a new NC-300.

C-16

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

CITY & STATE: \_\_\_\_\_

WORLD'S MOST PERSONALIZED RADIO SUPPLY HOUSE



3415 W. BROADWAY, CO. BLUFFS, IA., Phone 2-0277

For further information, check number 23 on page 126.

**NOW**

**SHURE**

you can improve  
speech intelligibility  
and cut through QRM  
with the

*Ranger*

MODEL NO. 505T

CONTROLLED  
MAGNETIC  
MICROPHONE  
WITH  
TRANSISTOR  
AMPLIFIER



All the advantages of controlled magnetic microphone construction—ability to withstand hard usage and extremes of climate and weather conditions—are yours in this sturdy, reliable microphone. The Ranger 505T has a flat frequency response characteristic (200 to 4000 cps), controlled to provide maximum speech efficiency.

It is ideally suited for SSB-AM transmission. Fits naturally and comfortably in the palm of the hand . . . takes up minimum space in mobile or fixed-station equipment. Equipped with heavy-duty push-to-talk switch.

LIST PRICE \$48.50

**SHURE**

*The Mark of Quality*



SHURE BROTHERS, INCORPORATED  
222 HARTREY AVE., EVANSTON, ILL.

MICROPHONES, HIGH FIDELITY  
AND ELECTRONIC COMPONENTS

VHF [from page 82]

"July 23rd VE1HT was barreling in here about 5 and WIHOY was knocking him out (Sorry.) She right on his frequency and when she goes on, oh, oh, Funny, the way I heard it VE1QY was the one on Helen frequency, and the one who knocks her signal out.

**Grabill, Indiana** — Word about a couple of things from Bob Zimmerman (K9GXI):

"It might interest you to know that I worked 10 states on the 6th of this month, (July), to bring me total to 33 states. I run 50 watts to an 832A and use one of my S.E.I. beams about 40' up." Have heard from a number of the fellows concerning that opening. Sure was a honey.

**Wilmington, Delaware** — Dana Huft (W3HWQ) sez:

"Thought you would like to know there is a fair active station on in Delaware. I am on the following bands: 430, 11 elements, 70'; 220, 11 elements 70'; 144, 22 elements, 70' 6, 5 elements. Receiver is an NC300 with all converters. The Gonset on 2, the Globe 680 on 5. Homebrew on 430 and 220. I am working on a kw two meters with a pair of 4-125A's." A lot of the fellows will be looking for you on those VHF bands Dana. You can count on a busy time.

**Lewiston, Maine** — A few notes from Clem (K1GPJ).

"I got my license on May 18, 1958 and to August 1958 had made 821 contacts. On July 15th WIUAR Massachusetts, W1EXZ in Vermont and myself had three way contact with all parties hearing each other. Have hopes of having an all New England QSO on six meters in the near future"

"Have worked K2RRG in New Jersey and a number of New York stations. Have now worked 29 states and have 29 confirmed."

"I'm on every morning from 0700 to 0800 on 50.22 mc and usually on also from 2100 every evening. Anyone who wants the state of Maine give me a shout." As there are lots of them in there Clem, most everyone needs Maine.

**Meriden, Connecticut** — Doug (W1K1K) also comes up with a little about a lot.

"Main project here has been six meters. The 6s works fine. Receiver is a tetract-converter into a RME-45 which has double conversion to 85 kc added. Also noise clipper and audio filter. Present plans are for a coax tank circuit with 6BCY. The antenna on 6 is a 4 element beam on 12 foot boom. By the August contest it will be a 7 element on a 24 foot boom."

"Plans for two meters include a new beam (32 elements) and coax tank front end with 417A or 416B. I can swing it."

"W1OAX has taken his YX 150 final and Collins moved to New Mexico. He leaves his states work total for Connecticut at 22."

"KN1IHA, Al, is the latest addition to the Meriden 2 meter gang. He is also mobile with ARC-5 and Gonset receiver."

"K1AFR, John, has built himself a crystal converter and a pair of 6146's in push-pull for two meters. He uses an 8 element telrex from a fine VHF location Hamden, Connecticut."

"W1VSE, Mert, has been busy of late. He now has two rigs on 6 and two rigs on 2. One six meter rig is a converted ARC-5 where 8 mc VFO is used. On two he uses an 829B or YX150 rig. The antenna is a element beam but plans are for a 40 element array."

"W1PTG, Al, has been back on two meters from the WNHC-T.V. transmitter."

"K1AZG has an 829B rig modulated with a pair of 807's. He puts out a fine signal as long as his overloads relays don't kick out."

"K1CRQ, Stew, has been building long yagis. In September another get-together is planned at his QTH. Fine business, Doug, always good to get these bits of news.

73, Sam, W1F2

For further information, check number 24 on page 126.



# KEN-ELS *headquarters* for **EICO**




## 90-WATT CW TRANSMITTER

#720

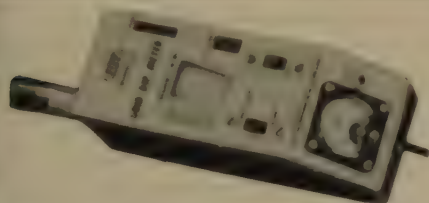**KIT \$79.95 WIRED \$119.95**

Conservative, highly efficient design plus stability, safety, and excellent parts quality. Covers 80 thru 40, 20, 15, 11, 10 meters (popular operating bands) with one knob band-switching. Finest quality, conservatively rated parts, copper-plated chassis, ceramic switch insulation. 5" H. 15" W, 9 1/2" D.




**NEW GRID DIP METER . . . . . #710**

KIT \$29.95 WIRED \$49.95 including complete set of coils for full band coverage.


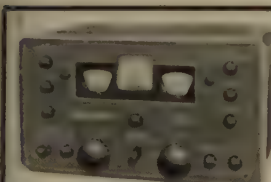
### EICO Deluxe PEAK- to-PEAK VTVM #249

with 7 1/2" meter and exclusive Uni-Probe (pat. pending). Kit only \$39.95; Factory Wired only. \$59.95



### HQ-160

GENERAL  
COVERAGE  
RECEIVER

**\$379.00**

\*Telechron automatic clock-timer \$10 extra.

WØZKD—Glen }  
WØZCN—Ken } Fort Dodge

428 Central Ave., Fort Dodge, Iowa  
Phone: 5-2451

WØCRP—Russ }  
KØABO—Rog } Cedar Rapids


37 16th Ave., S.W., Cedar Rapids, Iowa  
Phone: EM 4-1172

**KEN-ELS  
RADIO  
SUPPLY**


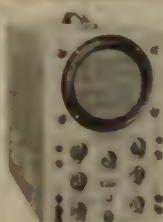
### NEW UNIVERSAL MODULATOR-DRIVER #730

KIT \$49.95 WIRED \$79.95 Cover E-5 \$4.50



### COLOR and Monochrome DC to 5 MC LAB & TV 5" OSCILLOSCOPE

#460

KIT  
\$79.95


WIRED  
\$129.50

• Features DC Amplifier

5" PUSH-PULL Oscilloscope #425: Kit \$44.95, Wired \$79.95

7" PUSH-PULL Oscilloscope #470: Kit \$79.95, Wired \$129.50

A Complete  
Line of

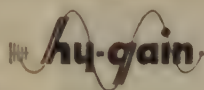

**6 METER  
5 ELEMENT  
\$12.95**

### 6 METER, 8 ELEMENT BEAM: \$24.95

The hy-gain 6-meter beams are adjustable for max. gain over the entire band, from our instructions. No further tuning necessary. Calibration Chart supplied with each instruction manual. Factory preassembled, these beams feature heavy wall 1/2" aluminum elements of 6061T6 alloy and 1 1/4" diameter aluminum booms. May be stacked for additional gain. Stacking Bars available at \$3.95 extra.

10% down — 24 months to pay. Your trade-in may cover down payment. Export business welcomed.


For further information, check number 25 on page 126.

For prompt, friendly service on

HY-GAIN

Talk to

Terry  
W9DIA

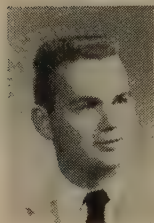

Steve  
W9EAN



*Perfect* 1:1 SWR  
with the NEW *Hy-gain*  
"monobanders"

### 10M - 3 ELEMENTS



18 lbs.  
Boom Length: 104"  
Longest Element: 17'10"

**\$24<sup>95</sup>**


### 15M - 3 ELEMENTS



30 lbs.  
Boom Length: 142"  
Longest Element: 23'10"

**\$34<sup>95</sup>**

### 20M - 3 ELEMENTS

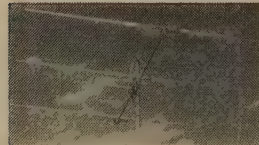

48 lbs.  
Boom Length: 212"  
Longest Element: 35'9"

**\$59<sup>95</sup>**

Average Gain: 8½ db. Average F/B Ratio: 24 db.

SEE THE COMPLETE HY-GAIN LINE . . .

See Terry Fri. eve 6 to 9 PM & Sat. 9 AM to 3 PM at

HARRIS RADIO CORP.

289 N. Main, Fond Du Lac, Wisc. Walnut 2-4670

Write for free used equipment listing—10% down—24 mos. to pay.

Wisconsin's Largest Ham Distributor

AMATEUR ELECTRONIC SUPPLY

3832 West Lisbon Ave., Milwaukee 8, Wisc.

WEST 3-3262

For further information, check number 26 on page 126.

100 • CQ • October, 1958

## CONTEST [from page 83]

envelope and sufficient new rate postage.

Look for OHØNB and OHØNC (Aland) during the Phone section. There is also a possibility of some CW activity. During the CW week-end we are promised some Luxembourg activity by DL7AH and DL9PF. They will be signing LX1RX and LX1KA. And there is still a possibility that PY2CK will be at Trinidad for the Phone section of the contest. Hope to have more for you next month.

## ARRL SS

A good opportunity to limber up your fist for the real contest that comes up at the end of the month.

## R5GB

The object of this contest is to work as many British Isles stations as possible on 21/22 mc Phone. (G, GC, GD, GI, GM and GW.)

Time—0700 GMT Saturday, November 23 to 1900 GMT Sunday, November 23.

Numbers—RS report followed by the usual progressive three figure serial, starting with 001, etc.

Points—Five points for each completed contact. A station may be worked only once on each band.

Bonus—A bonus of 50 points can be claimed for the first contact with each British Isles country/numeral prefix, e.i. G2, G3, GC2, GC3, etc. There are 36 combinations in all. A new bonus has been added this year. An additional 50 bonus points can be claimed for each ten G3 stations worked.

Scoring—Final score is obtained by adding the total contact points PLUS the total bonus points. There is no multiplier.

Awards—Certificates will be awarded to the leading station in each overseas country and each call area in VE, VK, W/K, ZL and ZS.

Send your logs to the R.S.G.B. Contest Committee, New Ruskin House, Little Russell Street, London W.C.1, England.

High man in the 1957 contest was G3DZ with 4140 points. The highest overseas entrant was VQ4RF with 2120 points. Certificate winners over here were: W8NWO 1540, W1F710, K2TCD/2 560, KØITF 515, W6AEI 445 and W3HQO 385. Winners across the border were: VE2YU 1405, VE3AIU 1095 and W2ZRX/VO1 680. Up in state 49 KL7PIV was top man with 1180 pts.

That's it for this month. Hope you sidebanders don't pass up the Phone section of the contest. The few SSB stations that were out last year were crying for lack of activity. Watch W3ASK's Propagation column for last minute forecast of what to expect in the way of conditions. Please George, make it another good year. Good luck, fellows.

73, Frank, W1WV



## BC-645 XMTR RECEIVER



### 15 Tubes 435 To 500 MC

Can be modified for 2 way communi-  
cation voice of code on both bands  
430-150 mc. citizens radio 400-430  
mc. Band and mobile 430-450 mc.  
television experimental 470-500 mc.  
15 tubes (tubes about worth more  
than \$20.00)  
2 6X5, 2 6A5 and 1  
6AV6. New covers 600 to 400 mc.  
New from BC-645 with tubes, less  
about \$10.00 in factory value

**\$29.50**

PE-120 DYNAMOTOR for BC-645, has 12-24V input, can  
to convert for 6V Battery operation. **\$7.95**

UMF ANTENNA ASSEMBLY for BC-645  
Complete set of 10 Poles. **\$5.50**

CONTROL BOX for phone **\$2.25**

SHOCK MOUNT for phone **\$2.25**

CONVERSION BOOKLET, Instructions for  
most useful surplus rigs. **\$2.50**

## SCR-274 COMMAND EQUIPMENT

### ALL COMPLETE WITH TUBES

Type	Description	Used	LIKE NEW
1	Complete set of 10 Poles	\$14.95	\$16.95
2	Control Box for phone	9.95	12.95
3	Shock Mount for phone	10.95	13.50
4	Conversion Booklet	1.49	1.95

### 110 VOLT AC POWER SUPPLY KIT

For All 274-N and ARC-5 Receivers **\$7.95**  
Factory wired, tested, ready to install. **\$11.50**

SPLINED TUNING KNOB for 274-N and ARC-5 RE-  
CEIVERS Fits BC-435 BC-434 and others. **49¢**

BC-437 TRANSMITTER-4 5.5 Mc. complete with  
all tubes and crystal. BRAND NEW **\$7.88**

BC-438 TRANSMITTER-5.5 to 7 Mc. complete  
with all tubes and crystal. BRAND NEW **\$7.88**

BC-439 TRANSMITTER-7.5 to 10 Mc. complete  
with all tubes and crystal. BRAND NEW **\$12.95**

ARC-5/T-19 TRANSMITTER-3 to 4 Mc. BRAND NEW  
complete with all tubes and crystal. **\$8.88**

BC-437 Transmitter Control Box **USED \$4.45 NEW \$4.95**  
BC-438 Transmitter Control Box **USED \$4.45 NEW \$4.95**

POWER SUPPLY KIT for 274-N and ARC-5 Transmitters, Input  
110 V, 60 cycles AC. Output 12-24V, 100 mA. **\$29.50**

BC-403 FM RECEIVER 88-108 Mc. complete with speaker. **\$10.95**

PE-120 DYNAMOTOR for BC-403, has 12-24V input, can  
to convert for 6V Battery operation. **\$7.95**

AC POWER SUPPLY for 274-N and ARC-5 Transmitters, Input  
110 V, 60 cycles AC. Output 12-24V, 100 mA. **\$10.50**

## SCR-522 2-METER RIG

Terrific! VHF Transmitter-receiver, 100-150 Mc. 4 chan-  
nel. Xtal. controlled. Amplitude modulated voice. Ther-  
mionic fast. Excellent control.

SCR-522 Transmitter-Receiver, complete with all 18 tubes,  
top rack and metal case. **Special \$33.33**

Receiver only, with all tubes. **\$19.50**  
Transmitter only, with all tubes. **\$22.25**  
Accessories for above available.

## WILLARD 6-VOLT MIDGET STORAGE BATTERY



3 Amp. Hour. BRAND NEW. 6" x 1 1/2" x 1 1/2"  
2 3/4". Uses Standard Electric. **Only \$2.69**

### 2 VOLT BATTERY "PACKAGE"


1-5V, 20 Amp. Hr. Willard Storage Battery **\$2.79**  
1-2V, 7 prong Synchronous Plug-in Dynamo **1.49**  
1-Quart Bottle Electrolyte (for 2 cells) **1.49**

ALL BRAND NEW! **\$5.45**


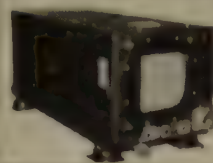
## BC-442 ANTENNA RELAY

Wonderful Value! Consists of 1/2 amp 2" RF  
Ammeter (no -0-0-0 current indicator), 0-10 scale  
Transmitter-Receiver Switching relay, in alumi-  
num case with associated compo-  
nents. BRAND NEW **\$2.49**



## ASB-5 'SCOPE INDICATOR

BRAND NEW, including all  
tubes, together with 500'1  
Range Tube. Originally used  
in Navy Aircraft RADAR  
equipment. Easily converted for  
AC operation.

VALUE \$250.00!

OUR LOW  
PRICE

**\$15.95**

## BC-659 TRANSMITTER & RECEIVER

100-150 Mc. FM. Two preselected channels crystal controlled.  
10 watts. Complete with speaker, tubes. Ex- **\$11.95**

Vibrator Supply for 6-12-24 Volts. New **\$11.95**

BC-659 FM TRANSCIEVER, 20-28 Mc. BRAND **\$9.95**  
NEW

PE-120 6-12V Power Supply, with Tubes and Vib. **\$11.95**  
NEW

Shock Mt. Rack, New **\$2.95**

## ARC-5/R28 RECEIVER

1 meter. Superhet, 100 to 150 Mc. in 4 crystal  
channels. Complete with 10 tubes. **\$24.45**

110 V AC Power Supply Kit for above **\$9.75**



## ARC-5/T-23 TRANSMITTER

100-150 Mc. Includes 2-821A, 2-1025 Tubes, **\$19.95**  
BRAND NEW

SPECIAL limited quantity ARC-5 T-23 transmitters **\$19.95**  
OFFER! BRAND NEW, less tubes..... **\$9.95**  
Excellent Used, less tubes..... **\$9.95**

## ARC-5 MARINE RECEIVER-TRANSMITTER

Navy Type Comm. Receiver 1.5 to 2 Mc. **\$16.95**  
BRAND NEW with 6 tubes

Navy Type Comm. Transmitter 2.1-3 Mc. **\$12.45**  
BRAND NEW with 4 tubes and Xtal.

MODULATOR for above, new, with tubes. **\$4.95**

## Hi-Fi DYNAMIC HEADSET with Cushions

Freq. Range: 40-14,000 CPS. No Distortion. **\$7.95**  
BRAND NEW

## MICROPHONES

Model	Description	Excellent BRAND Used NEW
T-17	Carbon Hand Mike	\$4.95 \$7.45
T-30	Carbon Throat Mike	.89 .79
T-45	Army and Navy Lip Mike	1.33
T-24	Carbon Mike	5.95
T-9	Headset	3.88
HS-38	Navy Type	2.79 4.95

## HEADPHONES

Model	Description	Excellent BRAND Used NEW
HS-23	High Impedance	\$2.25 \$4.75
HS-33	Low Impedance	2.79 4.75
HS-30	Low Imp. (leatherw.)	1.25 1.09
H-16/U	High Imp. (2 units)	3.75 7.95

TELEPHONICS 600 ohm HEADSETS BRAND NEW **\$3.45**  
PER PAIR

CD-307A Cords with PL55 plug and Jh26 Jack **.99**  
Earphone Cushions for above-pair **.50**

## MOBILE-MARINE DYNAMOTOR



12-24V DC Output 100 VDC 60  
Ma. for D.C. or A.C. operation.  
test operation. 110 V. 60 Hz.  
OUR LOW  
PRICE **\$9.95**

## SCHEMATIC DIAGRAMS for any equipment on this page each **65¢**

Please include 25% Deposit with order—Balance C.O.D. 50¢  
HANDLING CHARGE on Orders under \$5.00 MINIMUM. All  
Shipments F.O.B. Our Warehouse N.Y.C.

# G & G

## Radio Supply Co.

Telephone: CO 7-4605

53 Vesey St., New York 7, N. Y.

For further information, check number 27 on page 126

# GUARANTEED CRYSTALS!

**HERMETICALLY SEALED CRYSTALS**  $\frac{1}{2}$ " Spac  
.050 or .093

Amateur & Novice Fund. — .01% tol. ea. \$2.50  
Marine & Aircraft Fund. — .005 tol. ea. 4.10  
10 to 30 Meg. tol. .005% ea. \$3.75  
Overtones: 30 to 54 Meg. tol. .005% ea. 4.10  
54 to 75 Meg. tol. .005% ea. 4.25  
75 to 90 Meg. tol. .005% ea. 5.40

## Special! FT-243 Prec. Calib. to 1st Decimal

**2 Meters** { Exom: \*8010.6 x 18=144.190  
Exom: \*8010 x 18=144.180

Note—10 KC difference between the above

**6 Meters** { Exom: \*8340.6 x 6=50043.6  
Exom: \*8340 x 6=50040

Note—3.6 KC difference between the above

Calibrated FT-243 as exam. above\* spec. ....ea. \$1.19

Thin-Line FT-243—6 Meters,

50 meg. to 52.44 meg. ....ea. \$1.79

52.45 meg. to 54 meg. ....ea. \$2.39

2 Meters, 144 meg. to 148 meg. ....ea. \$1.79

Hermetically Sealed Fund. .01 Tol. ....ea. \$2.50

## NOVICE BAND FT-243 Fund. or DC-34 Freq. \$1.19

80 Met. 3701-3748—Steps of 1 KC. FT-243 or DC-34

40 Met. 7150-7198—Steps of 1 KC. FT-243 only

Dbl. to 40 Met. 3576-3599. Steps of 1 KC. FT-243 or DC-34

15 Met. 5276-5312—Steps of 1 KC. FT-243

4035	4995	5880	6362	6815	7316	7558	7710	7875	8066	7283	8575
4045	5030	5895	6373	6825	7325	7560	7716	7880	8073	8290	8580
4090	5035	5900	6375	6840	7340	7585	7720	7885	8075	8291	8583
4095	5090	5906	6400	6850	7350	7593	7725	7890	8090	8300	8590
4110	5127	5925	6405	6873	7358	7595	7730	7895	8091	8306	8591
4135	5185	5940	6406	6875	7360	7597	7733	7900	8100	8308	8600
4165	5205	5950	6425	6900	7373	7583	7740	7906	8106	8310	8608
4175	5235	5955	6440	6906	7375	7590	7741	7906	8108	8316	8610
4190	5245	5973	6450	6925	7400	7591	7750	7910	8115	8320	8615
4215	5327	5975	6473	6940	7406	7600	7760	7916	8120	8325	8620
4220	5385	5985	6475	6950	7408	7606	7766	7920	8125	8330	8625
4255	5397	6000	6500	6973	7416	7608	7770	7925	8130	8340	8630
4280	5435	6006	6506	6975	7425	7610	7773	7930	8133	8350	8633
4295	5437	6025	6525	7000	7433	7618	7775	7933	8140	8355	8640
4300	5485	6040	6540	7006	7440	7620	7780	7940	8141	8360	8641
4330	5500	6042	6550	7025	7441	7625	7783	7941	8150	8368	8650
4395	5545	6050							8154	8375	8654
4395	5585	6075							8160	8430	8660
4397	5587	6075							8166	8440	8670
4445	5645	6106							8170	8441	8675
4500	5660	6106							8173	8450	8680
4595	5675	6125							8175	8458	8683
4595	5700	6142							8180	8460	8680
4595	5687	6140							8183	8470	8690
4610	5706	6150							8190	8475	8700
4620	5735	6173							8197	8480	8708
4625	5740	6185	6575	7050	7458	7633	7791	7958	8206	8490	8716
4635	5750	6200	6600	7073	7466	7640	7800	7967	8208	8491	8717
4695	5760	6206	6606	7075	7473	7641	7806	7964	8210	8500	8725
4710	5773	6225	6625	7100	7475	7650	7808	7970	8216	8506	8730
4735	5775	6235	6640	7106	7483	7658	7813	7973	8220	8513	8733
4780	5800	6240	6650	7125	7500	7660	7820	7975	8225	8518	8740
4785	5825	6250	6673	7140	7506	7666	7825	7980	8233	8520	8741
4815	5800	6273	6675	7150	7508	7670	7830	7983	8234	8525	
4820	5860	6273	6700	7200	7510	7673	7833	7990	8241	8530	
4840	5820	6275	6706	7206	7516	7675	7840	7991	8257	8531	
4845	5825	6300	6725	7225	7520	7680	7841	7995	8258	8540	
4850	5830	6306	6740	7240	7525	7683	7850	8005	8265	8541	
4880	5850	6315	6750	7250	7530	7690	7858	8030	8266	8550	
4900	5855	6325	6773	7273	7533	7691	7860	8033	8270	8553	
4930	5860	6335	6775	7280	7540	7700	7866	8040	8273	8560	
4950	5875	6340	6800	7300	7541	7706	7870	8041	8275	8564	
4980	5875	6350	6806	7306	7550	7708	7873	8050	8280	8570	

**1000 KC-DC9-LM-BC 221 Sid. ....\$6.25**

**Fi-243—From 1005-2999. Steps of 5 KC ea. ....\$2.39**

### SPECIAL ITEMS—

FT-241 5SB. Matched Pairs..... pr. \$1.95  
FT-241 Single Side Band low frequency Crystals —  
370 KC to 540 KC.....ea. 59c  
AN/TRC-1 FT-241 holders from 729 to 1040 KC —  
1000 KC excluded.....ea. 75c  
FT-241 200 KC or 500 KC.....ea. \$1.00  
DC-34/35—1690 to 4440 KC. Steps of 10 KC...ea. 79c

**Marine & C.A.P.—All Freq. Available**  
2009—2182—2637 etc. Tol. .005% ....ea. \$2.99

## SEND FOR CATALOG — SE HABLA ESPAÑOL

Include 5c per crystal for postage. Calif. add.  
4% Tax. No. C.O.D.'S. Prices subject to change. Ind. 2nd  
choice, substitution may be necessary. Min. Order \$2.50.

**J. S. CRYSTALS, INC.**

1342 So. La Brea Ave., Los Angeles 19, Calif.

**SURPLUS** [from page 88]

second. Should the tone continue with the signal generator off, you have an oscillation and this will require detuning or anyone of dozen procedures to eliminate. If you have followed the directions carefully you will find that the set may oscillate while you are aligning it, but that the backing off of the slug adjustments will eliminate the oscillations. In severe cases you will have to increase the size of the plate decoupling resistor (that's the 1000 ohms resistor at the bottom end of the i-f return for B-plus) and also increase the size of the by-pass condenser associated with the resistor. Front end alignment was described last month, so we won't go into that except to say that the rf gets aligned at the low end of the band with the slugs and at the high end of the band by means of the trimmer condensers.

It is a usual practice to disable the avc when aligning a set by shorting it, but since this is not always advisable especially when the i-f gets a large portion of its bias from the avc line, we found that the alignment can be accomplished by the monitoring of the avc voltage (about 8 to 10 volts) with a vtvm.

## MAIL

It is gratifying to get as much mail about the simple feature of handbooks. It seems that the surplus hound is far from down and out and that surplus is still a big business. As you will see next month, this column is now devoted only to the conversion of military surplus, but that from time to time we will spend a little effort bringing an older piece of equipment to a new life having reached the status of surplus or junk in the light of present equipments. Of course everybody likes to have new gear, but a lot of us cannot afford to go out and buy all of the new stuff that is on the market. So bringing the older gear to life again will in a sense be using surplus.

We recently got a request from Harvey House of 2022 Bentley Ave., Orlando, Florida for a BC-652-A handbook. A day later we got a second request from another ham about the same gear. Strangely enough it isn't listed in any of the listings of available field manuals published by the Signal Corps, so if anyone has any data on this, please contact both Harvey and myself on this gear. In case you have a copy of the BC-654-A handbook, get in touch with K3BVV. That long awaited TCS conversion is not in my hands any more. It has been months since it was submitted for publication (and I'll bet the author forgot about it), but the backlog of articles is what has held it up. It will be in soon, but just in case KX6AF is looking for a conversion or a

[Continued on page 104]



# WALKIE-TALKIE RADIOPHONES

General specifications applying to all models:

Highest quality workmanship and materials, silver plated coils, ceramic capacitors and advanced design assures maximum performance with the longest battery life. Sensitive receivers can detect signals as small as one microvolt and feature automatic volume control and noise clipping. Transmitters use high level amplitude modulation, have a power input of one watt to the R.F. stage and will radiate a signal for 1 to 3 miles (depending on obstructions) using antennas supplied. Up to 40 miles have been reported by some of our customers when communicating with stations having directional beam antennas. Radiophones can be used singularly to communicate with fixed stations or two or more to communicate with each other providing they are for the same frequency band. Fully portable, no external connections needed. Uses standard radio and flashlight batteries available at your local store. Total weight of completed unit including all accessories is less than 5 1/2 lbs.

**Model TC-144.** Meets FCC requirements for general class amateur license. No minimum age requirement. Variable frequency transceiver circuit. Tunes from 144 to 148 mc. Wired, tested and guaranteed electronic chassis complete with two high frequency triodes. 3A5's ..... \$7.98

**Model TR-144.** Similar to above but with independently tuned receiver and transmitter circuits, using 4 high frequency triodes (2 3A5's). Permits receiving frequency to be changed without affecting transmitting frequency. \$11.98

**Model TRX-50.** Crystal controlled transmitter and variable frequency receiver with R.F. stage. Tunable from 50 to 54 mc. Meets FCC requirements for general and technician class amateur licenses as well as for civil defense and other special services. Wired, tested and guaranteed electronic chassis complete with six high frequency triodes. (3 3A5's) ..... \$16.98

**Model TRX-50-A.** Similar to above but with transistorized audio booster stage for extra loud reception ..... \$18.98



for as little as

**\$7.98**

plus accessories

**NOW 4 MODELS TO CHOOSE FROM  
IMPROVED CIRCUITS  
GREATER POWER  
TRANSISTORIZED**

The following accessories are required to complete the walkie-talkie as illustrated:

Strong 16 gauge 8" x 3" x 3" aluminum case satin etched and anodized with all holes punched for quick assembly. Heavy duty battery holders with phosphor bronze contacts, battery switch, telephone handset cradle, retractable coiled cord, adjustable shoulder strap, 18" or 24" antenna with loading coil (depending on frequency) and necessary hardware. All for only ..... \$9.98

Western Electric telephone handset with push-to-talk switch ..... \$6.98

Input and output impedance matching transformers for the above handset. Both for ..... \$1.98

Very active quartz transmitting crystal for models TRX-50 and TRX-50-A ground to .01% of your desired frequency and hermetically sealed ..... \$3.98

**How to Order:** If your dealer cannot supply you with our products you may order direct from our factory by checking each item desired and ADD 5% of total for postage and insurance. Orders not paid in full will be sent COD for the balance due. COD orders must include \$3.00 deposit. All orders immediately acknowledged.

Dealer inquiries invited.

FREE power output indicator kit with each order over \$20.00.

Manufacturing division

## SPRINGFIELD ENTERPRISES

Box 54-C-10, Springfield Gardens 13, N. Y.

For further information, check number 29 on page 126.

### ANTENNA MATCHER—At Left

Variable Inductance Tuner with Calibrated Vernier Lock Dial. 2 1/2" x 6" RF Meter mounted on Panel. Size 4 1/2" x 5 1/2" x 1 1/2" ..... \$9.95

### TRANSMITTING VARIABLE CAPACITORS

100 Watts:

22 MMF to 110 MMF	1 33 MMF to 440 MMF
..... \$1.95	..... \$1.95
19 MMF to 116 MMF	1 20 MMF to 135 MMF
..... 1.95	..... 1.95

Dial 210 MMF each section—SPLIT STATOR \$2.95

**PHONE PATCH TRANS.**  
No. C-161  
**\$1.95**



### RANGE BEAM FILTER

1020 Cycle Acceptance or Rejection with PL-55 Plug & Cord, two output jacks. New \$1.95. Similar to PL-55. 2 output jacks, less plug & cord \$1.80

**SIDE BAND LOADING COIL**  
No. C-114  
**\$1.95**

### PHONE PATCH CONVERSION UNIT

REMOTE CONTROL RM 52—Can be used with RM 53 or used as a separate telephone system. Uses 4 flashlight batteries. Also can be used as a direct remote control for radio equipment. Provides bias for Mic. & Siletoone to headset. High or low imp. Mic. & Phone Jacks. Easily converted to Phone Patch. See det. on CQ. Prices: Used: \$1.95; New: \$2.95

### MARS • CD • MARINE

RECEIVER-TRANSMITTER BC 1300—3000 to 6500 KC. Voice 15 Mils. CW 20 Mils. MO or Crystal Control. Crystal Calib. & Not Controls. Used: \$29.95

PE-237 Power Supply 1/BC-1300—4/12/ or 24 V. Used: \$14.95

Large Plug to 81 BC-1300 or PE-237 Each: \$1.95

SCR-521 RECEIVER-TRANS.—100 to 156 MC. Used: 29.95

RT-18/ARC-1 RECEIVER TRANS.—100 to 156 MC. Used: 89.50

BC-1335 FM RECEIVER-TRANS.—27 to 38 MC. Used: 24.85

BC-650 FM RECEIVER TRANS.—27 to 38 MC. Used: 14.65

BC-620 FM RECEIVER-TRANS.—21 to 28 MC. New: 14.95

MISC.: Magnets, Rams Horn, 5200 Gauss \$12.95

Magnets, Horseshoe: 75 lb. lift \$4.95—25 lb. \$2.95

I-208 Signal Generator—Used: \$59.50

Cole Tapes—15 Rolls to a Set—New: \$18.95

**THE WORLD'S FINEST SURPLUS BUYS!**

Send today for copy or our new

**FREE CATALOG**

### RECEIVERS

R AX-1 Four Band, 4 1/2" Dial, AVC. CW. MW. Phone Jack. Volume Control. Voltage required 24 VDC & 200 V 80 MA. Complete with 7 tubes, less top cover. Good condition. Size: 16 x 7 1/2 x 7 1/2"—as illustrated.  
Unit #1 200-1500 KC ..... \$18.95  
Unit #2 1500-3000 KC ..... \$18.95  
Unit #3 7000-27000 KC ..... \$18.95

R-26 ARC 5 Receiver 3 to 6 MC. Used: \$7.95  
R-28/ARC 5 Receiver 100 to 156 MC. Used: 14.95  
ARB Receiver 100 to 9050 KC. Used: 18.95

For details, send for our Free Catalog.

BC-652 Receiver—2 to 6 MC. Used: 24.85  
BC-112 342 Receiver—1.5 to 18 MC. Used: 79.50  
BC-734 Receiver—108 to 119 MC.—Paid: \$9.95—No

BC-603 FM Receiver—20 to 28 MC. New: 19.95  
BC-683 FM Receiver—27 to 38 MC. Used: 24.95  
BC-3050 FM Receiver—30 to 50 (10 MC Spread) New: 29.95

BC-1026 Receiver—200 to 400 KC.—Used: \$4.95 New: 9.95

### DYNAMOTORS:

1 VDC @ 350 MA. Starting Relay & Filtered. HD-70 1 V input—Used: \$9.95 New: \$14.95 PE-73 28 V input—Used: \$8.95 New: \$12.95 PL-50 10 MA Voltage P. \$1.00 PL-61 1 V Control Plug \$1.00 30 VDC @ 260 MA & 150 VDC @ 10 MA Starting Relay. Voltage Regulator. Filtered PE-98 14 V input—Used: \$12.95 New: \$19.95 PE-94 28 V input—Used: \$4.95 New: \$9.95 Input Plug \$4.00 Output Plug \$1.00 UNIVERSAL 13M TYPE-6 Volt 8 A. Input, output 12 V 18 A. 200 V 80 MA 12 Volt 4 A input, output 24 V 18 A. 500 V 50 MA Will operate BC-400 683 3050 ARC from 6 Volts No. 0515 ..... New \$4.95

	NEW	USED
1 VDC 220 VDC 80 MA	DM-34 \$4.95	\$2.85
1 VDC 625 VDC 225 MA	DM-35 14.85	11.95
1 VDC 375 VDC 150 MA	HD-83 6.95	4.95
1 VDC 540 VDC 450 MA	DA-12 9.95	6.95
1 VDC 425 VDC 103 MA	WE-377 12.95	9.95
1 VDC 225 VDC 100 MA	D-402 8.95	5.95
1 VDC 250 VDC 60 MA	DM-32 12 V 4.85	.....
2 VDC 275 VDC 150 MA	DM-64 8.95	.....
12 VDC 185 VDC 210 MA	DM-40 4.95	2.95
6 VDC 640 VDC 260 MA	Recond't. by G.E. 12.95	.....
6 VDC 450 VDC 260 MA	Recond't. by G.E. 9.95	.....
6 VDC 275 VDC 60 MA	DM-9450 6.95	4.95

ADDRESS DEPT. CQ • MINIMUM ORDER \$5.00 • PRICES F.O.B. LIMA, OHIO • 2% ON C.O.D. ORDERS

# FAIR RADIO SALES 132 SOUTH MAIN ST. LIMA, OHIO

For further information, check number 30 on page 126.

# YOUR mailing strip is IMPORTANT

4- 80 123 c DEC 60

SUSAN B QUICK-W2SLA  
139 BCH 112TH ST  
ROCKAWAY PARK N Y

This is a typical mailing strip

Whenever you write to CQ concerning your subscription, change of address, or renewal, cut your mailing strip from the wrapper of your latest copy and attach it to your letter.

This will help us to find your stencil in our files which is the first step in faster, more accurate service to our readers.

**CQ Magazine**

300 West 43 St., New York 36, N. Y.



## NEW FREE 1959 CATALOG

Here it is—the "bible" for the amateur radio industry, containing thousands of bargains from the Nation's greatest manufacturers. You'll find everything you want in amateur radio, hi-fi, the industrial and experimental fields... parts, tubes, tools, equipment... the works. Over 200 pages.

**Hurry! Send for Yours Today!**

**World Radio Laboratories** c-10

3415 W. Broadway • Council Bluffs, Iowa

"The World's Largest Distributor of Amateur Radio Equipment"

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

CITY & STATE: \_\_\_\_\_

For further information, check number 31 on page 126.

## SURPLUS [from page 102]

handbook as is Harold Cutshall, WØQPQ/ currently at East 9905 4th Avenue, Spokane 63, Washington. Received a letter from Mr. G. J. Meyers, Jr., Executive Vice Pres. of the Reading Tube Corporation, Box 126, Reading Penna. for conversion data and coil information (including where to purchase coils) for the BC-AR-429 receiving set. If anyone has any data on this please contact him directly.

K8IMR came up with a Bendix Communications system model 3801, with a model 3103 receiver and a 3006 transmitter. We give up except to say that it is probably airline surplus... can anyone help? K8JBE points out that the ARR-1 makes a good pre-amp for 10, 6 or 2 meters—just tune the coils for the band you want. Archie Love W4TCM is looking for a TBX-8 as well as a handbook for it. He claims he has used a Heath Battery Eliminator for the transmitter filaments while using a motor to drive the hand generator.

W3HSL wants conversion info on the ASI scope as well as the schematic for same. Has anyone a BC-1066 conversion for John Giddings PO box 3931, Bay Pines, Florida? Fred Lampell, K2OMY needs the AN/VRC-4 handbooks as well as the BC-609D interphone schematic. The BC-348-0 is still a hot receiver and Hugh Richards Jr., Box 631, Ft. Myers, Florida has one and is looking for the handbook that goes with it. 73, Ken W2HDM

## 6AU8 [from page 49]

pentode sections. Although not too important this is actually opposite to what might be desired. Driving a 6146 or a 2E26 is marginal.

Fig. 2 shows the same type of circuit using a 6AU8 which has a triode rating of 9 ma. and a pentode rating of 15 ma. This is the way we want it and we can run both sections cold for long life. Of particular interest (except for the first grid resistor) is the complete difference in values of resistance, capacitance, voltage and current. In studying the two schematics you will note that not only is more desirable operation of the crystal obtained but the large output of the pentode section with only 150 microamps of grid drive is extremely attractive and we still have 5 ma. of pentode plate current in reserve. We all know that 95 volts on the 2E26 grid is more than enough, thereby making tubes, components, crystals, and adjustments less critical. A potentiometer or variable resistor in place of the 51 K in the pentode screen will control your drive to the final stage. The use of the 6AU8 is not limited to only 50 mc so why not give it a try?

NOTE:

The 6U8 and 6AU8 do not have the same socket connections.



# THE HAM SHOP


## GLOBE

We can't see how you can get along without this beautiful 19-inch, 8 color World Globe. It can be yours, including a one-year subscription to CQ for lighted model W bulb \$24.95; unlighted model \$19.95.

Log Sheets of the most astounding modern design. Infinitely superior to any others on the market. And they are only \$1 for a pad of 100 sheets. Specify Regular or SSB type.
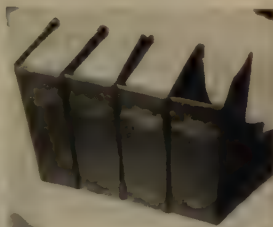
## BINDER

There is no other good way to keep your back issues. Make 'em neat. We supply the binder, with the year embossed in gold, not merely a sticker which will come off later. Specify what year you want stamped on your binder. \$3.50 each



## ATLAS

Come on, get with it. Don't pull a blank when some one asks you for the capital of Honduras. For only \$12.50 you can own 7 lbs. of full-color maps and a complete gazetteer. Send for this Hammond Atlas. PLUS a one year subscription to CQ.

only \$12.50



## MOBILE HANDBOOK

This new Mobile Handbook by Bill Orr, W6SAI, has been getting raves from all of the experienced mobile operators. There is all sorts of information in here that cannot be found anywhere else. This is NOT a collection of reprints. \$2.95 postpaid.

## COMMAND SETS

This IS a collection of reprints, containing all of the available information on the conversion of the popular "Command" transmitters and receivers into good ham transmitters and receivers. Invaluable for Novice, Technician, General, Advanced and Extra class operators. 136 fabulous amazing terrific pages for only \$1.50 PPD.

## COMMAND SETS



## HAM'S INTERPRETER

Now you can talk in broken French, Spanish, Italian, German, Swedish and Finnish. This handy little book gives all the popular ham conversation in seven languages, including letters and numbers. Only \$1.50 postpaid.



## CODE RECORD

Learning code is a snap with this record. Speeds from 3 to 16 WPM, depending upon turntable speed. This 12" LP record has on it all you need to learn the code for both the Novice and General license. \$3.50 each.

CQ Magazine  
300 West 43rd St.  
New York 36, N.Y.

SIRS, My check (money order for \$ \_\_\_\_\_) is enclosed. Please send the following items to: ☐ Lighted Globe ☐ Unlighted Globe  
☐ Log Sheets ☐ Binder—Year Wanted ☐ Atlas ☐ Mobile Handbook  
☐ Command Sets ☐ Ham's Interpreter ☐ Code Record

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

New York City residents add 3% Sales Tax

C-10

## QUALITY CUT QUARTZ FOR EVERY SERVICE



All crystals made from Grade "A" imported quartz — ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders	MC-7 holders
pin spacing 1/2"	pin spacing 3/4"
pin diameter .093	pin diameter .125
DC-34 holders	FT-171 holders
pin spacing 3/4"	pin spacing 3/4"
pin diameter .156	banana pins

### MADE TO ORDER CRYSTALS

1001 KC to 2500 KC:	
.01% Tolerance	\$2.00
.005% Tolerance	\$2.75
2501 KC to 9000 KC:	
.01% Tolerance	\$1.50
.005% Tolerance	\$2.50
9001 KC to 12,000 KC:	
.005% Tolerance	\$3.00
Specify holder wanted.	
3500KC hermetically sealed frequency marker crystal	
.005% tolerance fits octal tube socket	\$1.75

### ANY AMATEUR BAND CRYSTAL

.01% Tolerance

### NOVICE BAND CRYSTALS

80 meters 3701-3749 KC

40 meters 7152-7198 KC

15 meters 7034-7082 KC

### 6 METER TECHNICIAN BAND CRYSTALS

**\$1.50 ea.**

ASK YOUR LOCAL PARTS DISTRIBUTOR FOR TEXAS CRYSTALS . . . LOOK FOR THE YELLOW AND RED DISPLAY BOARD.

SEALED OVERTONE CRYSTALS supplied in metal HC/6U holders—pin spacing .486, diameter .050.

10 to 30 MC .005 tolerance	\$3.85 ea.
30 to 54 MC .005 tolerance	\$4.10 ea.
55 to 75 MC .005 tolerance	\$4.25 ea.

### TEXAS CRYSTALS' TRANSISTORIZED

#### 100 KC MARKER OSCILLATOR

Compact, portable, in attractive carrying case with handle. Size: 4" H x 3" W x 6" D. Connects to any receiver to get 100 KC markers from 100 KC to 50 MC. Factory wired with two transistors, one 100 KC crystal, self-contained battery. Shipping weight, 10 oz. Add 50¢ for prepaid parcel post.

**Net \$17.95**

MARINE FREQUENCY CRYSTALS • All marine frequencies from 2000-3200 KC .005 tolerance . . . \$2.50 (Supplied in either FT-243, MC-7, or FT-171 holders.)

RADIO CONTROL CRYSTALS • 27.255 MC sealed crystals (1/2" pin spacing . . . specify pin diameter . . . .093 or .050) . . . \$2.50 ea.

Stock crystals in FT-243 holders from 5675 KC to 8650 KC in 25 KC steps . . . 3 for \$2.00 or **75c**

FT-241 lattice crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC.) . . . **50c**  
Matched pairs ± 15 cycles \$2.50 per pair.

### WRITE FOR CATALOG AND QUANTITY PRICES

200 KC Crystals, \$2.00; 455 KC Crystals, \$1.25; 500 KC Crystals, \$1.25; 1000 KC Frequency Standard Crystals, \$3.50; Dual Socket for FT-243 Crystals, 15¢; Ceramic socket HC/6U Crystals, 15¢.

## Texas Crystals

The Biggest Buy in the U.S.

8538 W. GRAND AVENUE • RIVER GROVE, ILL.

ALL PHONES — GLADSTONE 3-3335

Terms: All items subject to prior sale and change of price without notice. All crystal orders MUST be accompanied by check, cash or M.O. WITH PAYMENT IN FULL. No C.O.D.s. Postpaid shipments made in U.S. and possessions only. Add 5¢ per crystal for postage and handling charge.

## VOX-BREAK [from page 47]

The keying relay selected follows straight or automatic keying perfectly from a few words to over fifty words per minute and contacts are used to actuate the transmitter keying circuit. For those transmitters in which grid-block or cathode keying is employed this relay may be eliminated from the circuit altogether along with its series connected 750 ohm resistor. In this case the connections to the transmitter keyed circuit are made directly across the contacts of the Vox-Break keying jack.

The plate relay contacts are heavy duty and are used to operate the transmitter controls desired. For well shielded transmitter installations good quality connectors such as Amphenol type 91MC or MP should be installed for cable entrance at the transmitter. It is also suggested that a small line filter be inserted in each line at the back of this connector inside the transmitter. A 3.9 microhenry choke in series with each line and a small .01 mfd ceramic button capacitor connected from each connector contact to ground serve the purpose perfectly. It is up to the individual reader to decide how the relay contacts are to be employed. In the author's Vox-Break the relay contacts go directly across the dpst plate voltage switch in the Viking II which in turn controls the antenna relay and receiver muting. Any combination to accomplish the same purposes will be satisfactory.

### Parts List

Transformer —Stancor PS8416  
Rectifiers —Federal 1002A  
Rotary Switch—Mallory 3115J  
Plate Relay —Potter & Bromfield LM-11  
Keying Relay —Sigma 41 DC Keying Relay  
Any low voltage 50 to 200 ohm keying relay may be used. Several available surplus.

All other parts as shown on schematic diagram.

For adjusting the plate circuit relay "on" time a shorting type five-position switch is attached to the output tube grid. After some experimentation it was determined that delays of 0, 1/4, 1/2, 1 and 1 1/2 seconds were all desirable and these have been included in the design. The cw man will find the 1/4 and second delays most applicable to traffic in operation with the 1 and 1 1/2 second delay more suited to the usual cw ragchew. The phone man will find the 1/4 second delay best for chatting with the SSB stations, the 1/2 and 1 second delays best for AM phone net use and the 1 1/2 second delay most suitable for the ordinary AM phone conversations. In the event that automatic VOX operation is not desired during a voice contact it is only necessary

[Continued on page 108]

For further information, check number 32 on page 126.





NEW 100V EXCITER-TRANSMITTER

NO TUNING except VFO. Uses famous CE BROADBAND system. PRECISION LINEAR VFO. 1AC Constantizer. Single Knob Bandwidth 80 thru 10. SSB-DSB-AM-PM-CW and PSK. RF Output adjustable 10 to 100 Watts PEP. Meter reads Watts Input, Amps Output and Carrier Suppression. 2 RF Scope. Speech Level and Load Mismatch Indicators. Audio Filter - Inverse Feedback - 50 db Carrier and Sideband Suppression.

IN PRODUCTION SOON..... PRICE \$595.00

## SUPERIOR SSB GEAR




MODEL 600L BROADBAND LINEAR

NO TUNING CONTROLS - CE BROADBAND Couplers in HIGH EFFICIENCY CLASS AB<sup>2</sup> using single 813. Easily driven to 600 Watts PEP Input 160 thru 10 by a 20A or 100V. Built in HEAVY DUTY POWER SUPPLY - 45 MFD PAPER Capacitor. Meter reads WATTS INPUT, GRID DRIVE, RF AMPS, and SWR. Completely shielded - TVI suppressed - parasitic free. REMEMBER there is LESS than ONE 5 UNIT difference between the 600L and a 2 KW PEP job.....PRICE \$495.00

MODEL 20A

### THESE MULTIPHASE EXCITERS PIONEERED AMATEUR SSB

MODEL 10B

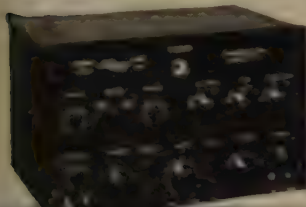

MODEL 10B - 10 watts PEP. Plug-in coils 160 thru 10 meters. Perfect voice control on SSB-DSB-AM and PM - CW break-in. Carrier and calibrate level controls. 40 DB suppression.

Wired.....\$179.50 Kit.....\$139.50

MODEL 20A - 20 watts PEP. Bandswitched 160 thru 10 meters. SSR-DSB-AM-PM and CW. Magic eye monitors carrier null and peak modulation. Ideal for driving AB1, AB<sup>2</sup>, and most Class B linears.

Wired.....\$279.50 Kit.....\$219.50



*Central Electronics, Inc.*

1247 W. Belmont Ave.

Chicago 13, Illinois

For further information, check number 83 on page 126.

# Hint: November 1st New Rates

We're not trying to be difficult or anything... it's just that postal rates are going up in 20% leaps and we have to raise the subscription rates if we are to stay in business. The present rate runs \$4 per year, \$7 for two and \$10 for three years. This will go up to \$5 for one, \$9 for two and \$13 for three. Some economies can be realized if you subscribe through your club at our club rates (have

your club secretary write for info) or if you buttonhole the editor at a convention or ham-fest. All of these arrangements are quite an improvement over the newsstand rate of a flat \$6.50 per year. It is therefore highly recommended that you get your subscription in soon, or extend your present subscription at the present rates.

THIS COUPON VOID AFTER OCT. 31, 1958

CQ Magazine  
300 West 43rd St.  
New York 36, N.Y.

One year, \$4 Two years, \$7 Three years, \$10 C10

in U.S. Possessions, APO & FPO, Canada & Mexico

Enclosed is \$..... for a..... year ☐ new ☐ renewal subscription to CQ, to be sent to:

Name..... Call.....

Address.....

City.....

Zone.....

State.....

Pan-America and all other foreign: 1 yr. \$6; 2 yrs. \$11; 3 yrs. \$16

## ANNOUNCEMENT

Again in this issue a new section appears in CQ where distributors may advertise trade-in and reconditioned equipment. This section, called the TRADING POST will be confined only to legitimate ham distributors as a means of announcing the many excellent used items available.



**TRADING  
POST**

**BARGAINS:** Send for list of reconditioned receivers and transmitters with new guarantee. 10% down with up to 24 months to pay. In stock new Collins, Johnson, Hallicrafters, WRL, National, Hammarlund, Gonset, Elmac, Drake, Central Electronics, B & W, Hy-Gain Mosley, Gotham beams. Shipped on approval. Write en, W0ZCN, or Glen, W0ZKD for your best deal. **KEN-ELS RADIO SUPPLY CO., 428 Central Ave., Fort Dodge, Iowa.**

**RECONDITIONED and GUARANTEED TO SATISFY:** Hallicrafters S40B \$65.00, S85 \$89.00, SX42 \$139.00, SX43 \$89.00, SX99 \$109.00, SX101 Mark III \$309.00, National NC98 \$109.00, NC188 \$119.00, NC109 \$169.00, NC183D \$275.00, NC300 \$289.00, Johnson Viking II \$189.00, Ranger \$199.00, "500" Like new \$649.00. Collins 75A1, 75A2, 75A3, 32V2, 32V3, BW 5100, 5100B/51SB-B. Many others. Write "Vince" W0NTA, **RADIO TRADE SUPPLY CO., 1224 Grand Ave., Des Moines, Iowa.**

**RECONDITIONED and GUARANTEED.** Satisfaction guaranteed. Terms financed by us. Hallicrafters S38 \$29.00; S85 \$89.00; SX99 \$119.00; SX96; SX100; SX101; HQ100 \$139.00; HQ110 \$189.00; HQ140 HQ150; National NC98 \$99.00; NC125 \$129.00; NC300 \$279.00; HRO50T; HRO60; NC183D; Central B slicer \$39.00; Globe Scout \$69.00; Viking II; Ranger; Valiant; Pacemaker; Thunderbolt; Heath DX35; DX100; Collins 32V; 75A2; 75A3; 75A4; etc. Many other items. Write for free list. **HENRY RADIO, BUTLER, MO.**

sary to switch the device over to the cw mode and depress the telegraph key for "press-to-talk."

No TVI has resulted from the installation and use of the Vox-Break and it has been found that usual receiver speaker volume insufficient to trigger the unit with the microphone a couple of feet away from the speaker at the operating position.

## HARMONICS [from page 96]

ances are connected in series on a line and capacitors in shunt, then dc will flow in one position and the ac of low frequencies are subject to only a small impedance. As the frequencies increase the series impedance and shunt circuit decreases. If the inductances and capacitances are correct with low rf leakage then the frequencies above a critical frequency will be attenuated and the network forms a low pass filter. Because the cut off frequency is much higher than the amateur band to secure a 50 ohm match the disk ceramic condensers may be used. Ceramic condensers are stable enough for this application and 10% deviation may be tolerated securing standard types to work in the filter, as the impedance curve rises slowly toward the cut off frequency.

*Technical Information:* For one section of filter

*Example:* Using values for 80 meters.  
800 mmfids and 2.3  $\mu$ hs.

$$1 \text{ Section: } f_c = \frac{1}{\pi \sqrt{LC}}$$

$$\text{Where } f_c \text{ Cut Off Frequency.}$$

$$= \frac{1}{\pi \sqrt{2.3 \cdot 1600 \cdot 10^{-18}}} = 5.23 \text{ mc.}$$

Using this value of 5.23 mc we can find the impedance of the filter at the operating frequency. (See Fig. 1)

$$Z_o = \sqrt{\frac{L}{C}} - \sqrt{\frac{2.3 \cdot 10^{-6}}{1600 \cdot 10^{-12}}} = 38 \Omega \text{ at zero frequency.}$$

$$Z_o = \sqrt{\frac{1 - f_1^2}{f_o^2}} \quad \begin{matrix} 38 \text{ where } f_1^2 = \text{operating frequency} \\ f_o^2 = \text{cut off frequency.} \end{matrix}$$

Impedance:

zero frequency	38 ohms.
1.0 mcs.	38 ohms.
2.0 mcs.	41 ohms.
3.0 mcs.	47 ohms.
3.5 mcs.	51 ohms.
3.8 mcs.	55 ohms.
4.0 mcs.	58.5 ohms.
5.2 mcs.	Infinity.

These are theoretical calculations. Extra capacity due to feed line etc. may add some error. The original article states the input and output impedance is not too critical.



ings ready to snuff out a young life! Do not be foolish and depend on old worn test leads and prods. Remember: the ordinary test prod is not built for high voltage!

One common mistake made by amateurs when testing commercial gear is to use a voltmeter whose sensitivity is low (1000 ohms per volt). Most manufacturers use meters having a sensitivity of 20,000 or more ohms per volt. If you follow their voltage charts reproduced in their instruction books using a low sensitivity VM you'll wind up with wrong voltage readings. In some circuits a difference of 3 or 4 volts is very important.

Yes, the day of the "hit and miss" era has since long passed. But as long as we have ham radio we'll have those with us who say: "heck, I've been on the air 20 years and never needed anything 'fancy' to do my testing. Only thing I need usually, is a good half watt neon bulb!" Hmmm! I wonder!

### OBSERVATION

In thumbing through various technical periodicals containing transistor circuitry, it is quite evident that one needs a "universal" manufacturers guide if he is to find out who makes what transistor. For example, few technicians or engineers could tell you who makes the "2N638" without charts such as those reproduced in SEMI-CONDUCTOR PRODUCTS (published by the publishers of our own CQ), or charts from the specific manufacturer.

At the present time there are so many transistors on the market that it is hard to keep track of them—let alone know their characteristics. Some companies like General Transistor, General Electric, Sylvania, GE, Texas Instruments etc., to name a few, publish very useable characteristic charts and handbooks on their semi-conductor products.

Observed: the numbering system for semi-conductor products is pretty sad. We hope that the time will come when transistors having the same characteristics but made by different manufacturers will bear the same number, just as most tubes do today. We know of the work involved in standardization and sincerely hope those connected with it realize that they have most hams who do a lot of their own design and construction on their "side of the fence." Authors of articles containing transistors should include a few of the most important parameters for the transistors they use and let the reader know WHO makes them!

### QUESTIONS

#### Bad Connection

I have a homebuilt transmitter using an 829B in the final. Lately I have noticed that my final current seems to vary without modulation, that is, on standby. I've checked the final tube, the meter and the power supply.



Balun  
Model 725  
\$19.50

**you'll want this**  
**Universal 1KW Balun**

... Because it's the answer to feeding either a single or folded type dipole or, the driven element in a beam antenna.

The Model 725 Balun also solves the problem of impedance matching. It is particularly effective on any multiband antenna with a 300 ohm feed point.

Frequency: 1.5 to 30 MC. Impedance: 75 ohms unbalanced to 300 ohms balanced. Max. Power Rating 1 KW on CW and AM (100% modulated), 4 KW P.E.P. on SSB.

See this rugged universal model at your favorite dealer, or write B&W direct.



**Barker & Williamson, Inc.**  
Canal Street & Beaver Dam Road  
Bristol, Penna.

For further information, check number 34 on page 126.

WATCH FOR THE GIGANTIC  
NOVEMBER ISSUE



### ARE YOU MOVING?

If you expect to move, and IF you know your new address now, and IF you don't want to miss any issue of CQ here are three things you can do right now!

1. Tear your name and address label off the wrapper of this issue and paste it in this box right over these words, or make a complete and accurate copy of your old address label.
2. Print your name and NEW post office address in the lines below:

(Name) \_\_\_\_\_

(Number and street—or Route) \_\_\_\_\_

(City) \_\_\_\_\_ (Zone) \_\_\_\_\_ (State) \_\_\_\_\_

3. Cut out this whole box and mail it to: CQ Magazine, 300 W. 43 St., New York 36, N. Y.

## KEEP CANDEE HANDY!

- ★ Count on J. J. CANDEE for reliable
  - ★ new and used surplus communication
- The Receiver buys of the year!**

### AN/APR-1 RECEIVER

Input 110 V. 60 cyc. Fresh from aircraft — so you know it's good! Includes receiver and two tuning units: TN-1: 38—90 MC; TN-2: 80—300 MC **\$29.95**

### BC-683 FM RECEIVER

27-38.9 MC. 10 push-buttons for channel selection. Continuous tuning. Squelch circuit. Complete with tubes, speaker, (less dynamotor). Excel. cond. Only **\$14.95**

### BC-603 FM RECEIVER

Same as above except freq. is 20-27.9 MC. Excellent condition **\$6.95**  
12 V. DM-34D DYNAMOTOR: for above. Excel. **\$3.95**  
110 VAC POWER SUPPLY: for above. Just plug in. No conversion needed.

Brand New . . . \$11.95

In Kit Form . . . \$7.95

### ARC-5 COMMAND EQUIPMENT

T-19 TRANSMITTER: 3-4 MC. Excel. cond. . . . .	\$5.95
T-20 TRANSMITTER: 4.5-8 MC. Excel. cond. . . . .	3.95
T-21 TRANSMITTER: 5.3-7 MC. Excel. cond. . . . .	3.95
R-25 MARINE RECVR.: 1.5-3 MC. Excel. cond. . . . .	8.95
R-26 RECEIVER: 3-6 MC. Excellent cond. . . . .	5.95
MD-7 MODULATOR: Excel. . . . .	8.95

Write us for your ARC-5 Equip't. needs.

### BC-1335 TRANSCEIVER

Two-channel, crystal controlled, FM. 18 tubes! Output: 1.5 W. For fixed or mobile installation. Range: 5-10 miles. Built in vibrator type power supply operates from 6 or 12 VDC. New in original carton. **\$29.95**  
In Like New Condition, only **\$24.95**

### ★ ★ HEADSET SPECIALS! ★ ★

HS-23: HI impedance. Leather covered headband. New, with cushions. **\$4.95**  
Get two for only \$8.49 Ea.  
HS-33: Low impedance. With extension cord. Brand new. **\$4.49**  
2 for \$9.95 Each only

### HI FI HEADSETS

15,000 cyc. NEW with cushions **\$8.95**

### SCR-625 MINE DETECTOR

Tone signals the location of metal objects buried 2 ft. or more. Excel. cond. Depot re-pack. Never sold at this fantastically low price! Only **\$24.95**

All items FOB, Burbank, Calif., subject to prior sale. In Calif. add 4%. Min. order \$3.95.

## J. J. CANDEE CO. Dept. C.Q.

509 No. Victory Blvd., Burbank, Calif.

Phone: Victoria 9-2411

For further information, check number 35 on page 126.

## CALLING ALL HAMS . . .

Lapel Pins and Tie Bars that will cause comment by Hams and non-hams alike! Heavy silver plating, personalized with your call sign. \$4.95 per set or \$2.50 each tax & postage included. Print Name, Address and Call Sign legibly with your order.

Do Your Xmas Shopping Early—ORDER NOW!

**HEWLETT SALES CO.** 1199 E. BROADWAY  
HEWLETT, N. Y.

## TELETYPE PRINTERS

Models #14, #15, #19, #26. Telewriter Receiving Converter. Perforators, D.C. Power Supplies. Transmitter-Distributors. Polar Relays.

### ALLTRONICS-HOWARD CO.

Box 19, Boston 1, Mass. (Richmond 2-0048)

## USA MIL TECH MANUALS

AN, TS, UPM, PRC, SCR, R, PE, PH, PW, TG, CF, OA, O, EE, RT, SG, TC, VRC, Etc.

Catalog upon request. Large stock!

**JAPAN ELECTRONIC TRADING CO.**

CPO Box 1556, Tokyo, Japan

Now what do I do?

How about checking your antenna relay contacts? Also look into transmission line continuity and connection. Sure you don't have something arcing over in the set? How about cold soldered joint in your power supply bleeder system? Loose tank connections? How about a resistor changing value? Check for loose filament connection on final tube. Hope you find your trouble.

## No High Frequency

I have a real old RCA receiver which used to work fine on 10 and 20 meters; now I hear nothing at all on these bands. All tubes tested o.k. Voltages seem to be fine too. The trouble started when I put my transmitter on the two mentioned bands. Any tips?

Yes! First of all, check your antenna connection in the receiver—but they're open due to RF. If they are not, check your band switch contacts and clean them carefully. When an oscillator receiver stops operating on one or more bands, suspect switch contacts first. If you had given us the type number of the receiver we might have been able to offer you a few more specific hints as to probable trouble.

## WRL SM-90

Will the screen modulator SM90 made by World Radio Labs. work with a Heath DX 2 transmitter and what do you think of it?

Yes. I think it is well worth the money.

## 2E26

Can Is use 2E26s in place of the 1625s in the linear described on page 317 of the current ARRL Radio Handbook?

No.

## Theory

Is there any objection to asking questions relative to radio-electronic theory? Sometimes outside clarification is needed to help in understanding a technical point or two.

No, in fact we have answered many theoretical questions. However, not always to the satisfaction of the correspondent. For example, one ham wrote in wanting to know "where the other sideband went" in SSB. We carefully explained balanced modulator cancellation to him but he said he couldn't see through our explanation. We tried again—but still no luck in getting the point across. By the way, anyone know where that other sideband really did go?

## R.F. Resistance

Here's a question on theory received recently. What actually is RF resistance? How can it be minimized?

Actually, it applies to the resistance of a conductor plus any additional resistance due to skin effect present at higher frequencies. It can be minimized by silver plating conductors to "current traveling depth" or the utilization of Litz wire or flat copper stripping.



## Transistor Course

Where can I get a homestudy course in transistor-electronics without having to take a lot of radio theory etc.?

CBS Hytron Sales Corp. of Danvers, Mass. offers a course in transistors. Contact your local CBS tube distributor for details. Also, the Philco Technological Center, 22nd and Lehigh Ave. Phil. 32, Pa. puts out a fine course too—complete with training kit.

## Tech Twists

If you have to ship a piece of delicate electronic gear, you can make sure it will arrive at its destination in good shape if you incase it first in a plastic clothes cover (obtainable at most dry cleaning establishments), and then surround it in a heavy cardboard carton with very cheap sponges obtainable at the five and dime store. Rubberized horsehair is even better if you can obtain some in block form from a local supplier. A KE-93 receiver shipped this way 6000 miles arrived in France without a scratch.

Temporary test prods can be made from old ballpoint ink fillers which have a recessed insulated point. Merely snap out the point and run a wire through the plastic ink container and solder the end to the tip, which is then snapped back in place after the wire has been pulled back to allow this to be done. But for goodness sake, don't use a metal filler! If you use a plastic filler without a recessed point it would be wise to wind enough plastic tape above the tip to prevent accidental contact with the point when using the prod.

## CORRESPONDENCE

We have been receiving many letters which do not include self-addressed and STAMPED envelopes. Fellows, we do not mind digging for the extra 3 or 4 cents, but with the number of letters we receive this mounts up. For quick replies use airmail (7¢) on inner and outer envelope. Thank you!

Please confine one question to one letter. Before you write HAM CLINIC check through CQ to find out if the information you are seeking is covered in some other department. When seeking information on current or recent articles drop a line to the author, that is why his address is included under the article title.

## QUESTION OF THE MONTH

Being too lazy to write for an index for past issues of CQ I thought I would write to you to find out the following: in what issues can I find information on the GDO (grid-dip oscillator)?

We receive many questions like this one. Readers are reminded that the CQ 11 Year Index is obtainable from the editorial office (address at the head of this column). Now back to the question of the month.

## QUARTZ CRYSTALS IN THE AMATEUR BANDS ONLY \$1.50 (with this advertisement)



Here's your opportunity to buy a quality crystal for your rig. These are not surplus crystals, but are newly manufactured to the highest standards. Mounted in hermetic sealed HC6/U holders. Special prices when this ad accompanies your order. Order will be mailed the same day it is received.

Meters	Frequency Range	Crystal Modes	Price
80	3500 to 4000 KC	Fundamentals	\$1.50
40	7000 to 7300 KC	Fundamentals	1.50
20	14000 to 14350 KC	Fundamentals	1.50
15	21 to 21.45 MC	Third Mode	1.50
10	28 to 29.7 MC	Third Mode	1.50
6	50 to 54.0 MC	Third Mode	4.50
2	144 to 148 MC	8000 to 8222 KC by 18 times 9000 to 9250 KC by 16 times	1.50
Citizen Band Crystals 27.255 MC			1.85

## TWO-WAY COMMUNICATION CRYSTALS

We specialize in the two-way communication field. We have two-way frequency correlation for G.E. Motorola, R.C.A. and others. One day service.

FREQUENCY RANGE	CALIBRATION TOLERANCE	PRICE
1000 KC to 2000 KC	.002%	\$6.00
2001 KC to 2500 KC	.002%	\$4.00
2501 KC to 9999 KC	.002%	\$3.00
10 MC to 15 MC	.002%	\$4.00
15 MC to 30 MC	.0025%	\$3.00
30 MC to 50 MC	.0025%	\$4.00
50 MC to 80 MC	.0025%	\$5.00

## ALL CRYSTALS GUARANTEED

## AMERICAN CRYSTAL CO.

821 E. 5th St.

Kansas City 6, Mo.

For further information, check number 36 on page 126.

## TUBE LINE UP

**SSB**

12AX7 Speech & 9 Mc XTAL OSC  
12AU7 Speech  
12AT7 Mod  
2—6AL5 Balanced Mod.

6CL6 9 Mc Amp  
6CL6 Mixer  
1626 VFO  
2—1623 R.F. Amp

Push To Talk 120 watts P.E.P. 40 watts A.M. Using the famous IM-458 cabinet and VFO, we are able to bring to Main Radio at a ridiculously low price SSB for everyone. Mobile or fixed. Upper lower sideband. Foolproof. 2 bands 14 & 3.5. Not a kit. By building your own power supply

1000 AMP

ALIGNED. COMPLETE WITH TUBES & XTAL.

Prices subject to change without notice. **\$160** Less Pwr. Supply

**GULF COAST PRODUCTS CO.**  
4720 Ave. R 1/2, Galveston, Tex.

## WANTED


TUBES—all types—Klystrons, Magentrons, Miniatures, Subminiatures, Transistors, Diodes, Etc.

HIGHEST PRICES PAID—IMMEDIATE CASH

J. S. H. ELECTRONICS CO.

P.O. Box 15654, 1108 Venice Blvd., Los Angeles 15, Calif.  
Richmond 9-7644

# New ROHN "FOLD-OVER" TOWER

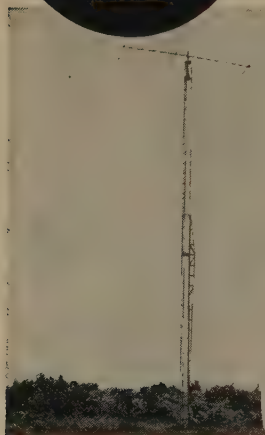

the *BEST* in  
antenna  
towers ...  
now  
*EVEN*  
*BETTER!*

DO YOUR WORK ON  
THE GROUND WITH  
ROHN FOLD-OVER"

- Hot-dipped galvanized after fabrication
- Structurally sturdy enough for all sizes and types antennae
- Excellent workmanship — superior design — yet economical in cost
- A complete tower made especially for amateur use
- FREE literature and nearest source of supply gladly sent on request

**ROHN** Manufacturing Company  
116 Limestone, Bellevue, Peoria, Ill.  
"Largest Exclusive Manufacturer of  
TV-Communications Towers"

For further information, check numbr 37 on page 126.

FOR THE FINEST IN AMATEUR PHONE PATCHES ITS ...

**K'WickPatch** The high speed  
high quality patch  
AM Models \$14.95. Dual  
by-bird Sideband models  
\$24.95. No switching...

No disconnecting ... Models for single or double connector  
microphones. See them at your distributor. For literature  
write to

KWickPatch, P. O. Box 612, Redwood City, California

**NEW!**

1 INCH

PANEL METERS

Self-shielded

**ALCO** Moving coil  
MINIATURES

**D.C. MICROAMMETERS**  
0-300 ..... 5.95 0-500 ..... 5.75

**D.C. MILLIAMMETERS**  
0-1 ..... 4.95 0-100 ..... 4.95  
0-5 ..... 4.95 0-200 ..... 4.95  
0-10 ..... 4.95 0-300 ..... 4.95  
0-50 ..... 4.95 0-500 ..... 4.95

**D.C. VOLTMETERS**  
1000 Ohms Per Volt  
0-3 ..... 4.95 0-50 ..... 4.  
0-10 ..... 4.95 0-150 ..... 4.  
0-300 ..... 4.95

**A.C. Rect. Type—1K  $\Omega$  per V**  
0-15 ..... 5.25 0-150 ..... 5.  
0-300 ..... 5.25

**ALCO** ELECTRONICS MFG. CO. Lawrence, Mass.

May 1947; Jan. 1949; Feb. 1949; Jan. 1951;  
March 1951; April 1950; and Jan. 1953,  
contain info on GDOs.

(Most back issues are obtainable for  
from CQ.)

## THIRTY

So far, we have given you the service you  
have a right to expect from a magazine that  
is still growing. When we have not had  
could not get the information you request  
we told you so. We are not infallible and can  
make mistakes just like anyone else. Taking  
care of this column and its resultant correspondence  
in our sparetime leaves us little time for  
the latter. But even if you do not have a question  
to ask we would like to hear from you.  
While in Europe I plan to visit most large  
cities in most countries over here, so if you  
have some special ham friend you want looked  
up, drop us a line, we'll add "visiting service"  
to other services now being rendered.

73, Chuck, W6QI

## PATCH [from page 44]

power level into the line. Why all this concern  
Crosstalk.

The telephone line which runs between your  
home and the local telephone office almost always  
physically parallels dozens, or even hundreds,  
of other lines. This physical proximity leads to  
inductive coupling which is not a factor with  
normal, i.e., zero level, audio on the line, but  
which will actually result in your receiver's  
signal being heard in neighboring lines if you  
use higher line level. Earlier, it was said that  
the surer road to Ma Bell's disfavor existed than  
the dc load on her lines. This is absolutely true,  
but excessive line levels run a darned close  
second. If you don't have an ac voltmeter handy,  
use this rule of thumb: THE AUDIO FROM YOUR  
RECEIVER, AS HEARD IN YOUR TELEPHONE, MUST  
NEVER BE AS LOUD AS YOUR OWN VOICE HEARD IN  
THE PHONE WHEN YOU SPEAK NORMALLY. Actually,  
keeping the audio in the line low also serves the  
advantage of making the party at the other end  
sound off. One of the most common problems in  
running patches, particularly with the ladies, is  
that the party at the far end of the wire seems  
reluctant to talk directly into the telephone  
microphone and at better-than-normal voice levels.  
As a result, the usable audio-to telephone-line-noise  
ratio (signal to noise) is usually pretty low and  
the overall system intelligibility far lower than either  
the phone or radio-link intelligibility takes



alone. If people have just a little difficulty in hearing the party at the other end of the line, they naturally tend to talk more loudly. Don't believe it? Make a long-distance call sometime and note how much louder *you talk!* All told, it is distinctly advantageous to keep under the zero VU limit for psychological reasons as well as for the dictates of good engineering practice.

Now, to the final hook-up. Your patch is completed so all you have to do is make the connecting cords and plug 'em in. The connection to the receiver speaker voice coil is made with a piece of lamp-cord terminated in a PL-68 plug. The cord to the transmitter speech must be of shielded wire (RG-58 U is FB) and terminated at one end with a PL-55 and at the other with a connector suitable for your rig. The line to your telephone may be of lamp cord, twin lead or what-have-you. Connect it from the binding posts on the rear of the patch to the two fuses in your telephone terminal box or to the red and green wires where the cord on your phone terminates at a block. Be sure these connections are made neatly so that they cannot short circuit—remember what was said about dc loads!

Ready to try it? Let's go. Contact some patient local ham buddy and get him on the air. Your PATCH-MIC switch will be in MIC position while you gab on the air. Now phone him. After you have him on the horn, flip the switch to PATCH. While he transmits on the air, increase your receiver gain control until you have a .75 volt maximum signal on the line or until you hear him clearly in your telephone receiver. Now you transmit while he talks to you on the telephone. Adjust your transmitter gain control (or PATCH GAIN CONTROL, if you built one in) until you have normal modulation as indicated by your normal modulation checking method. A word of caution: This particular method of checking is loaded with feedback possibilities that will give you embarrassingly high line levels unless your buddy keeps his telephone well separated from his speaker and his speaker volume low. At the first sign of feedback, flip the switch back to MIC.

In normal patching, remember just four things and all will be well. First, watch your line level; second, keep an eye on modulation, riding gain if necessary; third, never transmit either dial pulses or telephone operator's voices over the air; and fourth, always keep one hand on the patch switch—YOU and you alone are responsible for anything said over your station and not a few words frowned on by the FCC are wending their way into everyday conversation.

You now have a Macy's Special patch which will cut the mustard with the best of them. Good luck... and the author needs patches into Detroit, Gages Lake, Illinois, Lake Geneva, Wisconsin... Please hurry if you live in these areas!

## GOOD BUYS — ALL NEW

TRANSFORMERS		all have 115-volt, 60-cycle primaries
Reyno, 2000 v/3 mls & 3.5 v/175 a	5 lbs.	\$1.95
Staco, 6.5/1.80, 6.5/0.90, 700 v/30, 700 v/1.75, 6.5/0.6, 2 and 3 KV lns, upright shielded	5 lbs.	\$3.45
Power, Marconi B mount, upright shielded shell, 500 v/175 mls, 5 v/3 a, 6.5/0.6, 6.5/0.3 and 2 v/1.75 a, lns. var.	10 lbs.	\$5.95
Power, 700 v/120 mls, 5 v/3 a, 1.1, 6.5/0.6, HS 102	10 lbs.	\$2.95
Power, 500 v/240 mls, 5/3, 6.5/11.1, 17/1.2, HS 148	10 lbs.	\$3.45
Power, 100 v/60 mls, 5 v/3 a, 1.1, HS	10 lbs.	\$2.29
Pilament, 6.5/22, 6.5 v/2.4, 6.5/2.25, 6.5 v/0.6, 92	10 lbs.	\$3.29
CATHODE RAY TUBES		
6EP1	\$1.75	6EP2 \$3.45 6EP10 \$1.00 6EP11 \$1.29 6EP12 \$2.45

CHOKES		all are pot-core, hermetically sealed
18 h/500 mls, 100 ohm, 2000 r RMM test	30 lbs.	\$6.95
10 h/100 mls, 100 ohm, 2000 r RMM test	5 lbs.	\$1.89
4 h/50 mls, 11 ohm, 1000 volt test	1 lb.	59c 2 95c

MISCELLANEOUS VALUES		read carefully, some will go fast
Meter, 0-50 microamps, 2 1/2" round	1 lb.	\$4.95
25K ohm, 150 watt bleeder resistor	1 lb.	88c
100 watt wire-wound resistor for 24 v/100 mls	2 lbs.	\$2.59
100 v/100 mls, 200 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls	8 lbs.	2 95c
100 v/100 mls, 200 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls	10 lbs.	\$2.95
100 v/100 mls, 200 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls	10 lbs.	79c
455 KC IFs, very nice with schematic	8 lbs.	3 45c
TR-13 handset with plug, complete	3 lbs.	\$3.95
100 v/100 mls, 200 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls	2 lbs.	\$1.95
BC-610 RF coils, 2 lbs., complete set	2 lbs.	\$10.95
100 v/100 mls, 200 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls, 1000 v/100 mls	14 lbs.	\$6.95
Belina, Delco type II-A, C-56701 motor-respeaker	13 lbs.	each \$9.95 2 \$17.95

VACUUM TUBES		
701-A	\$3.95 pair	3B24 \$4.95/box
717-A, 2X2, 1642, 958-A	\$2.05/box	80Y, HY-615 \$19.95/box


### WRITE FOR FREE GOVERNMENT SURPLUS BARGAIN BULLETIN

Send adequate postage with orders. We refund any overage. All prices are FOB Sacramento.

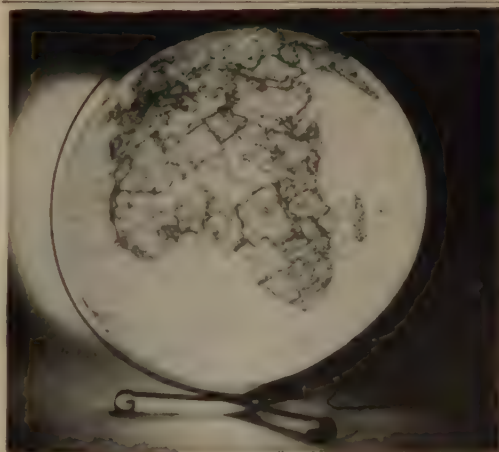**JOE PALMER**

PO BOX 6188 CCC, SACRAMENTO, CALIF.

For further information, check number 38 on page 126.



## Lighted Globe

When we first introduced the world globe some two years ago we found that there were a few malcontents who wanted to know if they could put a light in it. Ridiculous, said we, how do you expect to put a light bulb in a plastic globe? So, now we have it. \$24.95, including the light bulb and a year's subscription to CQ. A bargain! They sell for up to \$25.00 in the stores without CQ. And they are guaranteed, man.


Use order coupon on page 105

**DOW-KEY**

**Silent**
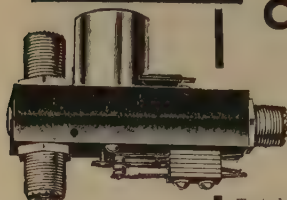
# COAXIAL RELAY

**GUARANTEED  
FREE OF HUM  
OR CHATTER**




**DKC-GE**

Power consumption, AC models Approx. 4 watts, DC models 3 watts. V. S.W.R. at 150 mc 1.1 and 1.2 at 300 mc. Coil voltages: AC 6, 12, 24, 115, 220; DC 6, 12, 24, 48, 110, 220. Special coil voltages available.

Tested and proven by amateurs and industrials. High contact pressures now made possible with new Dow-Key magnet principle, a new concept of low resistance contact, a new high standard for coaxial relays. Exclusive, patented receiver protecting connector, and heavy duty SPDT or DPDT switches are optional.

**PRICES** .....10.90 to \$14.20

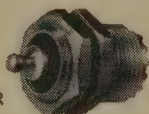**DKC-P  
PANEL  
MOUNT  
UHF  
CONNECTOR**



Needs only one 5/8" hole, no screws. Precision made, durable. Each .....70¢  
See your electronics dealer, or write for specifications.

**DKF-2  
DOUBLE-  
MALE  
UHF  
CONNECTOR**




A favorite for relays, antenna switches, cables. Durable, silver-plated, locking type. Each .....1.45  
Traditional factory warranty for unit replacements.

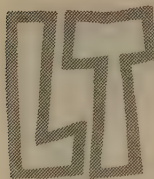**DOW-KEY CO. INC.**

THIEF RIVER FALLS, MINNESOTA

For further information, check number 39 on page 126.



**FIRST NEW PUNCH  
DEVELOPMENT IN 20 YEARS ...  
OBSOLETES EVERY OTHER  
PUNCH NOW ON THE MARKET**



**WALSCO**

**"L.T." LOW TORQUE  
CHASSIS PUNCH**

**CUTS a cleaner hole  
with 50% less effort!**



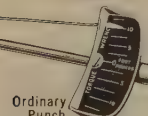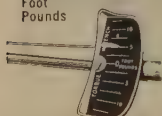Walsco  
"L.T." Punch  
Torque in  
Foot  
Pounds



Ordinary  
Punch  
Torque in  
Foot  
Pounds

A brand new electro-coating process (which can't wear off) reduces friction, thus lowers torque. You get a much cleaner hole with much less effort. The Walsco "L.T." Chassis Punch requires no lubrication of any kind and will give perfect service almost indefinitely. Available in a wide variety of sizes, round, square, key and D shapes.

Full information on these extra-easy to use "L.T." punches is available from your Walsco distributor or by writing direct to Walsco.

**WALSCO ELECTRONICS MFG. CO.**

A Division of Tectron Inc. • West Coast Plant: Los Angeles 18, Calif.  
Main Plant: 112 W. GREEN ST., ROCKFORD, ILL., U.S.A.  
For further information, check number 40 on page 126.

**YL [from page 85]**

How about it, gals? As part of Chapter 3 "History of the YLRL," the calls of all the YLs who joined YLRL in the first year of its existence, 1939-40, are listed as they appeared each month in "YL Harmonics." Let's hear from you and see what's happened in nearly 20 years! Also included in this chapter is a reproduction of the ad for the book "200 Meters and Down" which appeared in QST for May, 1939, together with the letter written in response to it by W7FWB, Ethel Smith (now K4LMB) which sparked YLRL into being. A couple of pages from the original story, "The YL's Unite!" by Nita Bien, W8TAY (now W4JCR) which appeared in QST for May, 1940 are included, also the W8 YLs at Cleveland, the YLARC of Greater St. Louis and the N.Y.C. YLRL, oldest of the YL clubs still in existence. Many photos of the early members, words of the YLRL song by W8UDA, and numerous other details are given. This is only one chapter in "CQ YL." There are 17 other chapters in the book covering every facet of the YLs' participation in Ham radio. Order your copy from your column editor, Louisa Sando, W5RZJ, 212 Sombrio Dr., Santa Fe, N.M., \$3.50 postpaid. Please indicate if you wish it autographed.

33, Louisa, W5RZJ

**AF-67 [from page 38]**

## Coil Data

**Coil L-a:** 20T. #30 scramble-wound on a 3/8 slug for m. (8 mc)  
**Coil L-b:** 22T. #22 close-wound on a high value 1-watt res. (25 mc)  
**Coil L-d:** 2T. #16 1/2 inch 3/8 inch, wound on former coil L-41 form (50 mc)  
**Coil L-d:** 2T. #16 1/2 inch 1D, spaced to 3/4 inches. (50 mc)  
**Condenser C-a:** 7-40 mmfd ceramic trimmer

to terminal 6 on switch SW-51C.

This completes the conversion. Place an 8334 (and up) mc crystal in socket "X2". If a grid dip meter is available, check all the new coils to be sure that they are near resonance. Turn the rig on, with the high voltage off the final (switch SW-52 in extreme counter-clockwise position) and adjust coils L-a, L-b, and L-c for maximum grid drive, which should be about three mils.

Assuming all is satisfactory, put high voltage on the final and check for resonance. The tank circuit is resonant with the tank condenser near minimum capacity.

This transmitter should give you very satisfactory service on six meters. It will load to just about anything you could think of using for an antenna. I would like to thank Michael Axman, W4VOZ, who assisted with the "brain work" in this conversion.



CITATIONS [from page 35]

On the other hand, the increase in violations may have resulted, also, from the increase in the number of licensed amateur stations. An analysis of station and operator licenses, however, doesn't help much. The ratio of increased violations in 1956 over 1953 does not bear a close correlation to the increase in number of licenses. The annual reports of the Federal Communications Commission show that as of June 30, 1952, there were 110,968 amateur operator licenses in effect, 12,827 of which were Novice licenses and 3,615 of which were Technician licenses. The following table shows the new licenses issued in each year of the survey period.

Year	Novice	Technician	Other Classes	Total
1953	9386	3652	4844	17882
1954	12044	3253	3723	19020
1955	18882	2314	4144	25928
1956	16819	3322	5199	25340

Apparently only a relatively small percentage of Novices secure a General license as can be seen from the small number of "other class" licenses issued in any year as compared to the total Novice licenses issued in the previous year.

As of June 30, 1955, the Federal Communications Commission reported that there were 139,993 licensed amateur stations, and as of June 30, 1956, the amateur stations licensed had increased to 150,549. The net increase in amateur station licenses for the year was 10,556 or approximately 7% more than the previous year. The violations reported, however, showed an increase of approximately 260% for the same year. The violations, therefore, increased far more rapidly than could be explained by the normal increase in station licenses.

One further possible explanation of the sharp increase in observed violations is the development of the Novice classification. Between June 30, 1955, and June 30, 1956, some 16,819 Novice licenses were issued and 3322 Technicians were licensed. Statistics of Novice licenses issued in previous years mean very little in connection with this study since Novice licenses are valid for only one year. It is safe to assume that persons receiving Novice licenses in previous years have either dropped out of the hobby or are now numbered as General licenses. Although exact figures are not available, Novice class licensees have received the highest percentage of citations.

If Novice licensees as a class do receive more citations than amateurs with General class licenses, then it may be desirable for some appropriate body to re-evaluate the licensing requirements for Novice licenses. A disproportionate ratio of violations committed by Novice ticket holders especially in the field of



wire this balun coil kit  
to suit yourself  
...It's easy!



Balun Coil Kit  
Model 3976  
\$8.95

A brand new balun coil kit with exclusive B&W design features. Model 3976 has sturdy, air-wound bifilar inductors for multiband impedance matching. Kit has full wiring instructions showing how to connect 75 ohms unbalanced to 300 ohms balanced, or 75 ohms unbalanced to 75 ohms balanced. Balun operates on 80 through 10 meter bands without tuning or changing coils. Rated at 250 watts maximum AM phone, 500 watts CW and 1 KW on SSB. Coils and space-saving mounting bracket also available separately. Available at better dealers now, or write to B&W direct.

 **Barker & Williamson, Inc.**  
Canal Street & Beaver Dam Road  
Bristol, Penna.

For further information, check number 34 on page 126.

# FREE

## GIANT NEW 1959 B-A CATALOG



180 KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR 1st TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

**BURSTEIN-APPLEBEE CO.**

Dept. CQ, 1012 McGee St., Kansas City 6, Mo.

☐ Send Free 1959 B-A Catalog No. 591.

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_

**SEND FOR IT TODAY**

For further information, check number 41 on page 126.
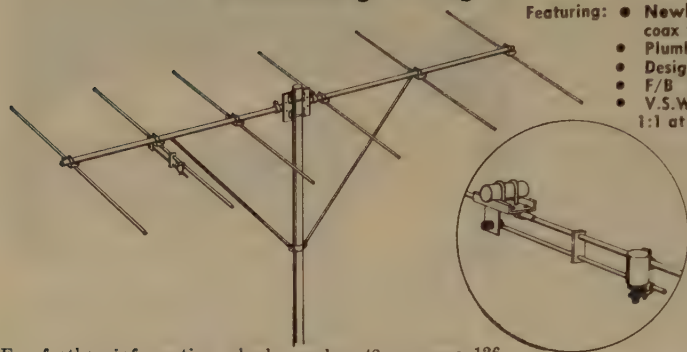
## The "Lunenburg" Long John Antenna for 6 Meters

- Featuring: • Newly Designed Gamma Match, complete with coax fitting  
• Plumber's Delight—finest aluminum ..... 50.5 Mo  
• Design Center ..... 23 D  
• F/B Ratio .....  
• V.S.W.R. ....  
1:1 at design center. Less than 1.5:1 within 2 Mc



- Horz. Beam Width  
45° (1/2 power points)
- Impedance..... Adjustable for any standard coaxial cable
- Overall length ..... 21'6"
- Net Weight ..... 15 lbs
- Shipping Weight ..... 20 lbs

HI-PAR PRODUCTS COMPANY  
FITCHBURG, MASS.

For further information, check number 42 on page 126.

### CRYSTALS inc.

ACCURACY DEPENDABILITY QUALITY  
and ONE DAY SERVICE

#### AMATEUR BAND CRYSTALS

Not surplus! New quartz ground and etched to your exact specified frequency. Checked on HP cycle counters.

1500 KC to 2000 KC.....\$2.00 ea. postpaid.

2001 KC to 8995 KC.....\$1.50 ea. postpaid.

8996 KC to 11000 KC.....\$2.50 ea. postpaid.

#### SSB FILTER CRYSTALS

Plated type in FT241A holders. All channels 370 to 534 KC (except 500 KC) \$1.00 ea. postpaid. 500 KC \$1.75 ea. postpaid.

Channel Groups Accurately Matched, No Extra Charge.

#### MARINE FREQUENCIES

All channels. Guaranteed accuracy. Supplied in MC7 or FT243 holders (specify which type) \$3.75 ea. postpaid.

#### VERY THIN CRYSTALS

Supplied in very thin FT243 holders. Order by fundamental frequency. \$2.00 ea. postpaid.

Minimum Order \$2.00

No CODs.

Satisfaction Guaranteed or Your Money Back!

ILLINOIS ORDERS . . . Please Include Sales Tax

### CRYSTALS inc.

ODELL, ILLINOIS

For further information, check number 43 on page 126.

## 47 RADIO PROJECTS 75¢ Plus "White's Radio Log"



Think of it... 47 electronics projects you can build... explained with diagrams, photographs and step-by-step instructions, plus "White's Radio Log," a directory listing U.S. and Canadian AM, FM and TV stations by call letters, locations, kilocycles and power and over 1,000 world-wide short-wave stations. Terrific value! Get this 192-page handbook, RADIO-TV EXPERIMENTER, No. 555, at newsstands 75¢; or direct from:

SCIENCE & MECHANICS

450 E. Ohio St., Dept. 792, Chicago 11

radiation harmonics might indicate that more technical information should be required as a condition to issuance of a Novice license, thereby insuring some preliminary study in connection with suppression of harmonics.

While the issuance of a citation by the Federal Communications Commission does not ordinarily involve any penalty except the preparation of a reply and an explanation including details of corrective action which has been taken, repeated violations have resulted in suspensions or revocations of the amateur license. Suspensions and revocations are likewise on the increase. For the fiscal year ended June 30, 1953, four license suspensions occurred. For the fiscal year ended June 30, 1954, ten license suspensions occurred. For the fiscal year ended June 30, 1955, five suspensions occurred. For the fiscal year ended June 30, 1956, seventeen suspensions occurred, and thirteen orders to show cause why disciplinary action should not be taken against amateurs were issued by the Commission. Suspensions increased three-fold in 1956 over 1955.

Although the Radio Act of 1934 provides for criminal penalties for violation of the Federal Communications Commission regulations, no criminal proceedings were instituted against licensed amateurs by the Federal Communications Commission during the four-year period involved in this study. Several criminal convictions were obtained against persons who operated radio transmitters on amateur frequencies without having been issued a license.

Although the number of violation citations might not be considered as a large number considering the number of amateurs licensed during that period of time, nevertheless, two matters should cause the serious amateur to reflect upon the effectiveness of self-regulating activities. The first is the fact that officially observed violations in 1956 were almost five times the number of observed violations during the same period of time the year before. The second aspect is the fact that the officially observed violations do not necessarily represent all of the violations which actually may have occurred.

During the year 1956, 236 amateur ob-



servers participating in the ARRL official observer program observed and sent out 10,348 co-operative report notices of regulation violations. While these notices do not carry with them the legal injunction of an official F.C.C. notice, they do nevertheless represent observed violation of amateur regulations. It is, of course, impossible to tell how many of the 10,348 official observer notices were in fact duplications of the 5,248 official citations issued by the Federal Communications Commission for the same period, but it is safe to assume that in some cases at least the two sets of notices did not relate to the same occurrences nor duplicate each other.

While it is undoubtedly true that the issuance of informal official observer notices undoubtedly gave many amateurs an opportunity to correct their illegal practices before being observed by an F.C.C. monitoring station, it does not answer a fundamental question which must be asked; that is, why did this number of observed violations occur in the first instance? As a hobby-saving precaution, it is not sufficient that amateur violations be detected by fellow amateurs before they are observed by an official monitoring station. The violations simply cannot be permitted to occur in the first instance regardless of who observes them first. The fact that the F.C.C. observed only 5,248 amateur violations in 1956 should not lull the amateur into any sense of false security. Given a higher monitoring priority, more and more violations would be officially observed. A hard look at the practical effectiveness of the amateurs' self-regulating activities is timely. Careful attention to the regulations and an active campaign on the part of the amateurs to live with the regulations and reduce the number of violation citations can be an important factor in maintaining the status of the hobby. Too many violations could easily cause the F.C.C. to question seriously if the amateur service is really entitled to the consideration it has received.

It is hoped that analysis of the available statistics might prove valuable in charting a course of more complete amateur compliance with regulations. The necessity of amateurs' voluntary compliance with the regulations should be obvious to all. With limited budgets available for communication commission personnel and monitoring services, any substantial increase in time or personnel required for regulating the amateur services will inevitably raise questions as to whether or not the amateur services justify such required increase of personnel. It is a vulnerable point that powerful grabbers would delight to emphasize. It might, therefore, be time well-spent to analyze the type of violations which have been observed and reported by the Federal Communications Commission and to take a good hard look at the effectiveness of amateurs' self-regulating activities.

## pi-network coils provide complete line



Model 851  
\$16.50

Model 850A  
\$35.00

Model 852  
\$39.50

Now—Pi-Network inductors specially tailored for your needs. Here are highly-efficient, super compact tank coils incorporating the unique feature of integral band switching.

Model 850A and Model 852, now complement the famous B&W Model 851. All are designed for single or parallel tube operation on 80, 40, 20, 15, 11 or 10 meters, with top efficiency in Class "C" or linear operation. Windings give ample current carrying capacity with optimum "Q" over the entire operating range.


See these superior B&W inductors at your dealers now, or write B&W direct for detailed information.



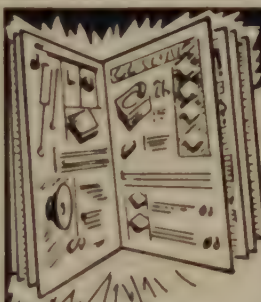**Barker & Williamson, Inc.**

Canal Street & Beaver Dam Road  
Bristol, Penna.

For further information, check number 34 on page 126.



# FREE!

**CATALOG**  
4,872 SQ. IN.  
OF BARGAINS!

IT'S TRUE! Olson's Catalog has 4,872 sq. inches of Gigantic Bargains at prices that defy comparison—and it's FREE for the asking! Tremendous savings on Name Brand merchandise—Tape Recorders, Hi-Fi's, Radios, Record Changers, Speakers, Amplifiers, Intercoms, Mikes, Kits, Cabinets, Testers, Antennas, Tools—and on and on. You name it, Olson can put it in your hands—and you keep the change. Don't delay, send for your free copy NOW!

MAIL THIS COUPON TO:

## OLSON RADIO WAREHOUSE

C-108 FORGE ST., AKRON 9, OHIO

Rush me your FREE Olson Catalog without obligation Today!

Name.....

Address.....

City..... Zone..... State.....

For further information, check number 44 on page 126.

**FOR THE BIGGEST BATCH . . .**

**of blockbusting buys in electronics**

**get our new, free, 32-page**

**CATALOGUE NO. 117! It's terrific!**

## **ARROW SALES, INC.**

Sales-Showrooms:

Western: 7035 Laurel Canyon Blvd., North Hollywood, California.

Central: 2534 S. Michigan Ave., Chicago 16, Ill.  
Mailing Address: Box 3007, No. Hollywood, Calif.

# W2HSU

### **CALL PLATES—CUSTOM MADE TO YOUR ORDER**

Show your Call Letters proudly in a bold new, distinctive style plate. Silver anodized aluminum cast letters—Giant size  $3\frac{1}{2}$ " high—Three dimensional effect. Permanently mounted on jet black enamelled background. Overall size  $4\frac{1}{2}$ " x 16". Hang in your shack or mount on your car. Immediate delivery. Only \$5.95 ppd. Satisfaction guaranteed.

**CRAFTSMAN, 287 Jay Street, Brooklyn 1, N. Y.**  
MA 5-3344

### **CANADIAN AMATEURS**

We are now manufacturing Amateur and Commercial antennas—write for free brochure describing our new Beam Antenna series.

**LINDSAY ANTENNA & SPECIALTY PRODUCTS LTD.**  
DEPT. C-A LINDSAY, ONT., CANADA


# BANG

**go prices in our  
newest catalog!**

**Get YOUR  
free copy today!**

**COLUMBIA ELECTRONICS**  
2251 W. Washington Blvd.  
Los Angeles 18, Calif.

TELL THEM  
You SAW IT  
IN CQ

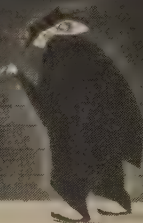

## **NOVICE [from page 91]**

Todd Fonstad, KN9LWU, 316 Jefferson Waupaca, Wis. is interested in two me walkie talkies. Look for him on 40 if you have any info.

Jim Johnson, KN7CNT, 209 Karr Aver Hoquiam, Washington, has been on for about 5 months haunting the 80, 40, and 15 meter bands with his Adventurer. He will sked anyone needing a Washington contact.

John Stone, KN4VUR, P. O. Box 3 Leaksville, N. C. is active on 21.150 and would like skeds with 7's and 0's. John QSL's 100 when he picks 'em off with his Globe Scout 680-A and S-85. By the way, he is looking for an SX-71 or SX-76.

Don Evans, WV6AWR, 241 W. Ave. Lancaster, California, makes them sit up and take notice with a Viking Adventurer and SX-99. Don would like 40 meter skeds with all states except Calif. and Arizona.

Jim Charipar, 701 7th Ave., Iowa City, Iowa is an expectant Novice. He plans on running DX-20 and an SX-99. Give a listen for him.

John Schroeder, WN6UFJ, 5735 Jefferson Avenue, Hollydale, California, just passed his General test. While a Novice, he worked states and some impressive DX, with a AT long wire ant., and a HQ-100 receiver.

Peter Henderson, WV2APZ, 36 Woodhull Pl., Northport, L. I., N. Y. is using a Heath AR-3 and a DX-40. He has two antennas including a Demi-Quad (PE-Jan-58). Pete would like to see more information on operating technique.

Jerry Janka, KN9JHY, 141 Andy Drive Melrose Park, Illinois, wrote an interesting letter suggesting that we drop the DX report Help Wanted and Letters. Jerry had some good arguments, too, but he didn't say what to put in their place. This constitutes almost the entire column—hi.

Dell Keene, KN6EOK, 1853 East Gage Avenue, Los Angeles 1, California, slugs away on the 40 and 80 meter bands with an AT and a brand new HQ-110. The antenna is Hy-Gain 14AV. He will sked for any reason or if anyone wants nomination to RCC.

Bill Crook, KN6GNO, 997 Capri Drive Campbell, California, runs a "baby 7 watt rig and a S-38-C. He has totaled 216 QSO with 160 QSL's for confirmation. Bill would like to work a Texas station. How about it?

George Kracke, WV2AGR, Shewenken Avenue, Millvale, N. J. is having trouble getting out on the 40 meter band. Can anyone help him?

Paul Nugent, W1NJX, and Howard Gould, KN1HHN, 29 Eire St., Dorchester 24, Mass. would like to start a radio club and would like interested hams in the area to contact them.

Toby Rayer, 1516 N. Ridge Dr., Cincinnati 31, Ohio, writes to say he is starting an SW



QSL bureau.

Al Bogdonoff, KN2HIR, 1716 Avenue "T," Brooklyn 29, N. Y. is on 40 meters with a DX-20 and an S-38-D and is rockbound on 7155. To date he has worked 187 contacts in 18 states. Nice going, Al.

Tim Morrell, KN1GBI/1, Box 413, York Harbor, Maine, is very active on 15 with a Globe Scout 680-A and a S-85 feeding a homebrew single element "beam." He needs skeds with Okla., Ark., La., Miss., Ariz., N. & S. Dakota and Alaska. He will sked anyone needing N. H. or Maine.

Mike Broga, K1DQG/DL4, 586 C&G Sqdn., APO 109, N. Y., N. Y. has been too busy to send in DX reports but will resume shortly. He is expecting the DL4 calls to arrive soon. Mike would like a teen-agers contest—everybody else has them—hi.

Late Late letters for the 807 arrived from: C. E. Corbin, WV6AWH, R@, Box 313, Merced, California

George Hall, WV6AGH, 1750 E. Westward Avenue, Banning, Calif.

John Palesch, R6, Oswego, N. Y., WV2AND

Joe Allison, WV2AYV, 49 Orlando Avenue, Albany 3, N. Y.

73, Don, W6TNS

**SCRATCHI** [from page 12]

they saying he reel 1/c thinker.

I'm surely you reelizing reel problem here. Not having to having lisenese to operating on ESP. Not needing to taking FCC eggssaminayshun. Anybuddies can be ESP amchoor, even if they not knowing di-dah from dah-dah-dit-dit.

Thinking of fun amchoors having in dee-x contest. Have to ESP'ing in foren language. It would be like kibitzing at United Nayshuns, only worse.

Maybe worst thing would be your Hon. Mag. Yes indeedy, Hon. Ed., thinking or artickles you having to printing. Maybe one on How to Increasing Your Signal 6 DB by Eating Alaska Salmon. Or maybe one on Lat-est Style in Operating Chairs.


Or how about How a Sponge Rubber Cushion Helped Me Work For More States. Maybe even Get Your Feet Up in the Air for Reel Dee-X. Possibly you having artickle called Ware the Right Clothing and Work the World. Hon. Ed., you might even having to sponsor a stile show!!

It's not too late. Tell everybuddies they can avoiding this fate. Telling all amchoors not to thinking. No thinking allowed. Just pounding good old key or using good old mike. Remember—no thinking.

Eggscuse me Hon. Ed., I seem to be heering something in my mind. Quiet! CUL, Hon. Ed., I thinking somebuddy calling me mentally.

Respectively yours,  
Hashafisti Scratchi

## AMAZING NEW VIBROPLEX

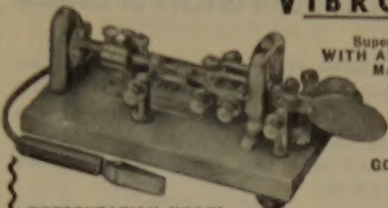

Super DeLuxe  
WITH ADJUSTABLE  
MAIN SPRING  
AND OTHER  
GREAT  
FEATURES

24-K  
GOLD-PLATED  
BASE TOP

### PRESENTATION MODEL

\$29.95

Vibroplex presents the first really speed control key. An adjustable main spring permits operator to send slower or faster as desired. No more muddy signals. . . no sacrifice of signal quality. Suits any hand or any style of sending. Free of arm tension. Sends easily as pressing a button. Praised by operators and beginners alike. Try this new Vibroplex key! You'll be delighted. Other new popular Vibroplex keys from \$15.95 up. At your dealer or  
THE VIBROPLEX CO., INC. 833 Broadway, N. Y. 3, N. Y.

2, 6, 10 — Meter

### MOBILE EQUIPMENT

MOTOROLA, R.C.A., G.E., LINK, etc. 30-50 Mc., 152-172 Mc. Used Commercial F.M. Communications Equipment Bought & Sold. Complete two-way sets meeting F.C.C. Licensing Requirements for taxicabs, Police, Fire, etc. \$169.00 and up.

Motorola F.M. Receivers, Double

Conversion ..... \$55.00 each

Motorola F.M. Transmitters ..... 45.00 each

### COMMUNICATIONS ASSOCIATES INC.

165 Norfolk Street  
Dorchester, Mass.

## EASY TO LEARN CODE

It's easy and pleasant to learn or increase speed the modern way — with an **Instructograph Code Teacher**. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready, no QRM, beats having someone send to you.



### ENDORSED BY THOUSANDS!

The **Instructograph Code Teacher** literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the **Instructograph System**. Write today for full particulars and convenient rental plans.

## INSTRUCTOGRAPH COMPANY

Dept. C, 4701 SHERIDAN RD., CHICAGO 40, ILL.

### DON'T BE A BULB SNATCHER

Check your rig properly with a non-radiating dummy load using this **SPECIAL Global Ceramic non-Inductive Resistor**, rated 600 ohms @ 118 watts. Standard fuse clip mounting. Parallel 3 for 300 ohms @ 236 w. 8 for 75 ohms @ 944 w. 12 for 50 ohms @ 148KW, etc. Write for free info. Also perfect for Ithomia & T2FD antennas.

Govt. cost over \$5.00—NOW ONLY \$1.10 ea.

12 FOR \$12.00—POSTPAID USA

### ARKAY ELECTRONICS

Ft. George Sta., P.O. Box 23, New York 40, N. Y.

### PERFECT CHRISTMAS GIFT

**CQ YL**

The only book about the YLs. 18 chapters, 500 photographs, covers all phases of YL participation in Ham radio. Autographed copy \$3.50, postpaid. Order from:

LOUISA B. SANDO, W5RZJ

212 Sombrio Dr.

Santa Fe, N. Mex.



## EQUIPMENT & COMPONENT SPECIALS

- **General-Radio Variac Type 200 CUH**—The original continuously adjustable autotransformer—Input voltage: 115 volts at output voltage of 0 to 270 volts @ 2 amps. Also will operate from 230 volts and deliver from 0 to 270 volts @ 2 amps. Brand new sealed in original cartons—only \$11.95 less knob & dial.  
With knob and dial..... only \$12.95
- **Millen 2" Magnetic Shield with 2 3/8" x 2 3/8" Bezel** with green-tinted face. Made of NICOLOL.  
Brand new—Millen #80042..... \$2.50
- **Marion 2 1/2" Round Hermetically-Sealed 36-Volt D.C. Voltmeter.** Has expanded 18 to 36-volt scale in Half-volt steps.  
Clean, removed from equipment ..... \$2.95
- **Cornell-Dubilier Heavy-Duty 12-Volt Power Supply.** C.D. Model No. 3414 Heavy-Duty 300 Volt D.C. Output at 335 MA. Vibrator Supply Units are made with the finest of components and best construction for long trouble-free use. All units are brand new, packed in original Cartons. Units come complete with two CK-1006 Rectifier Tubes and C.D. Vibrator Type 12VF10. Input: 12.6 VDS. Output: 300 Volts D.C. at 335 Milliampers. Size: 8 1/2" High x 13 1/4" Wide x 7 1/4" Deep. Weight: 28 lbs. Sale Price ..... \$19.50
- **500 Watt Tra-1 UHF Xmtr RF Amplifier & Power Supply.** Perfect for 6 meters . . . requires 3 Watts drive—P.P. 4E27's. 115 Volts 60 Cy companion power supply uses pair of 3B28's. All units are unused in mint condition . . .  
\$165.00 the pair, F.O.B. N.Y.C.
- **Carter Duovolt Dynamotors**—operates from 6 or 12 Volts D.C. type A puts out 400 VDC @ 375 Ma..... \$15.95  
Type B (also operates from 6 or 12 Volts D.C.) puts out 620 VDC @ 280 Ma..... \$19.95  
All units are brand new, genuine Carter Dynamotors with mtg. brackets.
- **Kilowatt Antenna Change-Over Relay.** Specs: 115 VAC 60 CPS coil. Contacts: DPDT w/all ceramic insulation—compact. Quiet. Units are new. Special..... \$3.95
- **Scintillation Counter Gramscint Model 1002.** Self-contained portable Scintillation type Gamma-Ray Detector designed for prospecting, radiation monitoring, etc. Contains a nine-stage photo multiplier tube coupled to Gamma sensitive plastic phosphor which makes this instrument a real buy. Regular Price \$245.00 complete with Trimm headphone, leather strap, batteries, ready-to-operate. Sale Price \$49.95

Continued Next Page

# BARRY ELECTRONICS CORP.

512 Broadway, Dept. 10-C, N.Y. 12, N.Y.

Phone: Walker 5-7000

## The Ham Shop

RATES: 25¢ per word per insertion for commercial business organizations.  
10¢ per word per insertion for individuals on non-commercial basis.

**MINIMUM CHARGE: \$1.00**

**CLOSING DATE:** 20th of the 2nd month preceding date of issue.

**MAIL:** Your typewritten copy with full remittance should be sent to CQ Magazine, 300 West 43 St., New York 36, N. Y.

Attention: Classified Ad Dept.

**NOTE:** The products and services advertised in this section are not guaranteed by the publisher or CQ.

Telephone orders not accepted.

Call letters only are undesirable. Please include name and address in all advertisements submitted.

### FOR SALE

**V.H.F. ROUND UP:** Don't forget October 11. That's the date of the Syracuse VHF Round-Up. All the DX men will be there, so don't stay home and listen to a dead band. Contact Bob Mele, W2EMW, 18 Howland Dr., N. Syracuse, N.Y.

**ATTENTION MOBILEERS!!** Leece Neville 6 volt amp. system alternator, regulator and rectifier, \$45.00. Also Leece Neville 12 volt 100 amp. system, alternator, regulator & rectifier \$85.00. Perfect condition. Herb A. Zimmerman, Jr., 115 Willow St., Brooklyn 1, N.Y. K2PAT, ULster 2-3472.

**DRAKE 1A RECEIVER:** in excellent condition, real great receiver, but I need money desperately. First \$100 gets it. Box 12, CQ Magazine, 300 W. 43 St., NY 36.

**PRESERVE YOUR HAM TICKET,** Social Security Card, small photo, passes and anything else of value that's wallet size. We will laminate it in clear plastic, guaranteed for life. Lamination will prevent it from getting torn, soiled or frayed. Send your ticket or anything of value with \$1. in stamps or cash for each item that you want preserved. 24 hour service. Send to Dept. HW, Magazine, 300 West 43rd St., N.Y. 36, N.Y.

**CALL PLATES:** Deluxe 8" x 1 1/4" black phenolic laminate with engraved white letters. Only \$1.00 pp. Polished plexiglass base \$1.00 extra. L. and J. PRODUCTS Co., P. O. Box 122, Downers Grove, Ill.

**THIS HALO ANTENNA** makes VHF mobile operation worthwhile. Folded dipole elements. 2 meter Model H-comes with fitting for standard mounts and 20 feet coax. Portable Model H-144P mounts directly on your Gonset. Either model only \$13—\$13.50 west of Denver, L. and J. Products Co., Box 122, Downers Grove, Illinois.

**BARGAINS:** Send for list of reconditioned receivers and transmitters with new guarantee. 10% down with up to 24 months to pay. In stock new Collins, Johns Hallcrafters, WRL, National, Hammarlund, Gonset, Elmac, Drake, Central Electronics, B&W, Hy-Gonset, Mosley, Gotham beams. Shipped on approval. Write K1W0ZCN, or Glen, W0ZKD for your best deal. Ken-Radio Supply Co., 428 Central Ave., Fort Dodge, Iowa.

**FOR SALE:** Still waiting for WAS, WAZ confirmation! Send Reply-Paid QSL's! 5, 25¢; 25, \$1.00. Hart, Park, Birmingham, Michigan.

**WORKED ALL STATES?** Mount your QSLs neatly in first QSL Album designed specially to hold your W.A. cards. Heavy leather-textured covers, sturdy wire binding, individual spaces for all 48 states. Cards can be inspected, removed, replaced. \$3.50 postpaid. Call let in gold for affixing to cover \$1 extra. Hanover Electronics, 126 East 37th Street, N.Y.C., or your dealer.

**FOR SALE:** Schematics, radio or T.V. 59¢. Send me and model number. Call Book \$5.00. Ham receiver \$5.00. T.V.I. \$1.75, 100 QSO file cards \$1.00, DX QSL forwarded 2¢ each after membership. Free flyer. "radio coop" Box 5938 Kansas City 11, Missouri.



## MOBILING [from page 31]

mobile work. Unless the mobile is equipped with some sort of special voltage-generating system, it is best to mount a trickle charger in the car and plug it in every night. Another possibility is to connect the output of the battery charger to a plug which fits in the cigarette lighter socket.

A word of caution to mobilers that attend drive-in theaters. Do not operate your transmitter the next time the movie is dull. Those drive-in PA systems soak up rf like West Texas soaks up water. Some people get downright indignant at hearing "CQ 40" come over their speaker instead of the movie's sound track, as dull as it may be.

As I have been mistaken for a policeman, I have also been mistaken for just the opposite. On one occasion while chasing DX from a high hill with an engine-generator for power, I found myself suddenly surrounded by squad cars with drawn arms pointing my way—ordering me to come out with my hands up. It took a lot of convincing that I was an amateur radio operator and not a spy operating a short-wave radio station.

Now, in order to be mobile, it is necessary to be prepared to answer many questions about your hobby. The following are the most common, there are many more. Prepare at least one answer for each of the following:

- Are you a policeman?
- What's that big aerial for?
- Have you got television in there?
- Is that thing there for a telephone?
- Who can you talk to with that thing?
- Can you get police calls?
- How far can you talk?
- What do you talk about?
- Are you one of those people who interferes with TV?
- Do you ever talk with \_\_\_\_\_? (Any name or QTH may be inserted here.)
- What kind of license plates are those?
- Are they legal?
- Since when did \_\_\_\_\_ (insert the name of your state here) quit putting numbers on license plates?

So, this is mobiling. It's a great sport! ■

## AUSTIN PASS [from page 34]

time keeping little kids out of the gear and trying to explain why we were there, that there was no time to ham. Ever try to DX-Pedoperate with about a hundred people looking over your shoulder, tripping over power cables, and stepping on test gear.

The car did start ok and we didn't have to coast down the hill. Both of us were tired, hungry, but ready for another expedition when the time is right. What member of the great amateur radio fraternity doesn't love a DX-Pedition any place and any time? ■

## HAMS—HOBBYISTS—DEALERS! Here's a DEPENDABLE SOURCE of SUPPLY for RECEIVING TUBES



Nationally sold ZALYTRON Tubes are BRAND NEW Quality Tubes, guaranteed to perform as well and as long as tubes much higher priced. Why pay more? Try them once, you'll buy them always. Every tube we ship is covered by our Full Refund Guarantee . . . YOU be the judge! Send today for new Price List "Q".

**ZALYTRON**

**TUBE CORP.**  
220 West 42nd St.,  
New York 36, N. Y.



## RADIO AMATEUR CERAMIC SPECIALTIES ONLY \$2.75

#M1. Approx. 20 ounce mug, embossed with colorful amateur figures. (For a "YL" figure, order Item #M3), and amateur's individual call sign made with one-inch black characters.

**MILLWOOD STUDIO**  
Box 223, Rowley, Mass.



**\$2.98** postpaid

Send for Gift Catalog

**THE KREBS**

Westerly 3, Rhode Island

## SOLDER-ETTE

Calling all radio "hams" and handy men! You can't afford to pass by this all-purpose soldering iron. Small, rugged, really "heats up"; has fine tip for hard - to - get - at places. Repairs radios, TV sets, and many items about the house.

25W, 110-120V, AC/DC  
Complete with cord.

## RADIO ZONE MAP GET YOUR FREE COPY. . .

OF THE UNITED STATES

REQUEST IT WITH YOUR NEXT  
ORDER OR INQUIRY TO:—

**LADD ELECTRONICS**

111 No. 41 ST., OMAHA 31, NEBR.



## WANTED

Special Purpose Vacuum Tubes; Klystrons, Magnetrons, Power Tubes; Lab Test Equipment; X, S, K, bands, Signal Generator, Slotted Lines; Aircraft Communication Equip't.

We pay top prices fast! REpublic 5-0215

**V. & H. RADIO-ELECTRONICS**  
2053 W. Venice Blvd., Los Angeles 6, Calif.



# Advertising Index

Alco Electronics Mfg. Co.	112	Instructograph Company	119
Allied Radio Corp.	128	International Crystal Mfg. Co.	19
Alltronics-Howard Co.	110	JSH Electronics Co.	111
Amateur Electronic Supply	100	Japan Electronic Trading Co.	110
American Crystal Co.	111	Johnson, E. F. Company	27
Arkay Electronic Sales Co.	119	Ken-Els Radio Supply	99 & 108
Arrow Sales, Inc.	118	Krebs, The	125
Barker & Williamson	109, 115 & 117	Kwick Patch	112
Barry Electronics Corp.	120 & 121	Ladd Electronics	125
Bud Radio, Inc.	94	Lakeshore Industries	12
Burstein-Applebee Co.	115	Lindsay Antenna & Specialty Products Ltd.	118
Candee, J. J. Co.	110	Master Mobile Mounts, Inc.	26
Central Electronics, Inc.	107	Millen, James Mfg. Co., Inc.	2
Centralab	22	Millwood Studio	125
Cleveland Institute of Radio Electronics	14	Morrow Radio Mfg. Co.	20 & 21
Collins Radio Corp.	Cover II	Mosley Electronics, Inc.	25
Columbia Electronics Sales	118	National Company, Inc.	Cover III
Communications Associates	119	Olson Radio Warehouse	117
Craftsman	118	Palmer, Joe	113
Crystals, Inc.	116	Petersen Radio Co., Inc.	1
CQ Back Issues	122	RCA Electron Tube Div.	Cover IV
CQ Ham Shack	105	Radio Bookshop	95
CQ Subscription Ad.	107	Radio Shack Corp.	123
CQ World Globe	113	Radio Trade Supply Co.	108
CQ YL Book	119	Regency Div., I.D.E.A. Inc.	18
Dow-Key Company, Inc.	114	Rohn Mfg. Co.	112
East Meadow Surplus Co.	124	Science & Mechanics	116
EICO	23	Shure Brothers, Inc.	98
Eitel-McCollough, Inc.	13	Springfield Enterprises	103
Eldico Electronics	17	TAB	127
Electronics Illustrated	96	Texas Crystals	106
Fair Radio Sales	103	Trading Post	108
G & G Radio Supply Co.	101	U.S. Crystals, Inc.	102
General Electric Co.	24	United Catalog Publishers	93
Gonset Company	16	V & H Radio Electronics	125
Gulf Coast Products Co.	111	Vibroplex Company, Inc.	119
Hallicrafters Company	10 & 11	Walsco Electronics Mfg. Co.	114
Hammarlund Mfg. Co., Inc.	15	World Radio Laboratories, Inc.	97 & 104
Heath Company	4, 5, 6, 7 & 8	Zalytron Tube Corp.	125
Henry Radio Stores	108		
Hewlett Sales Company	110		
Hi-Par Products Co.	116		

# Reader Service

## CQ Magazine, Dept. RS

300 West 43rd Street  
New York 36, New York

Reader Service Coupon J  
Void after Oct. 25, 1958

Please send me information on your ads in the October 1958 CQ keyed as follows:

1	2	3	4	5	6	7	8	9	10	11	12
13	14	15	16	17	18	19	20	21	22	23	24
25	26	27	28	29	30	31	32	33	34	35	36
37	38	39	40	41	42	43	44	45	46	48	49
50	51										

Name \_\_\_\_\_ Call \_\_\_\_\_ Engineer ☐

(Please Print)

Address \_\_\_\_\_ Type of work (specify) \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_